

Friday March 17, 2017

Last time:

- RC circuits (charging/discharging capacitors)
- RC time constant and its meaning
- Early and late time behaviour of RC circuits



Today:

- RC circuits example
- Power in circuits
- Group activity

Charging/Discharging Capacitors



Charging: $q(t) = Q_f \left(1 - e^{-\frac{t}{RC}} \right)$

$$i(t) = i_0 e^{-\frac{t}{RC}}$$

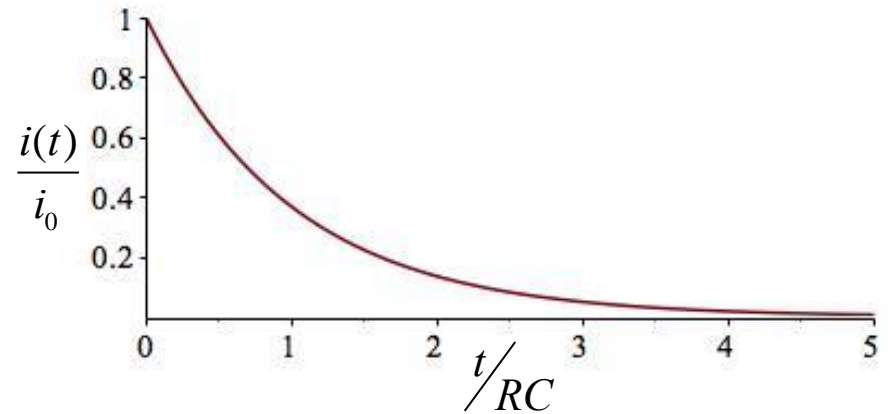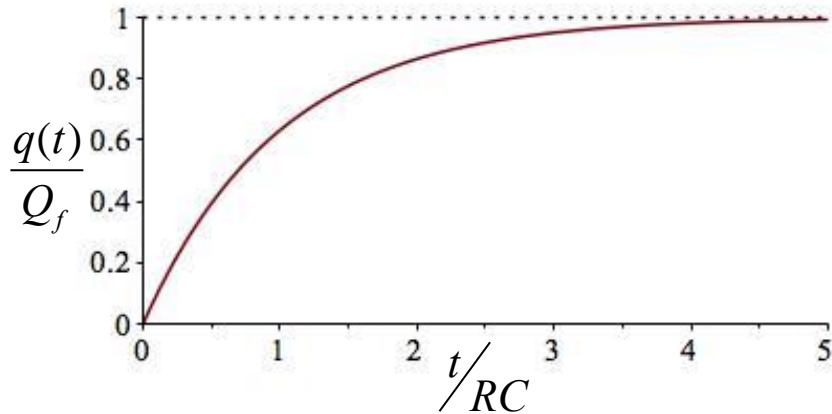

Discharging: $q(t) = Q_0 e^{-\frac{t}{RC}}$

$$i(t) = i_0 e^{-\frac{t}{RC}}$$

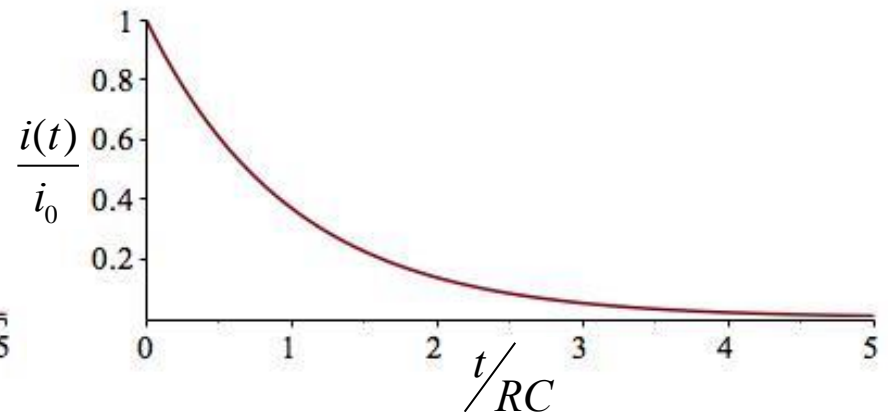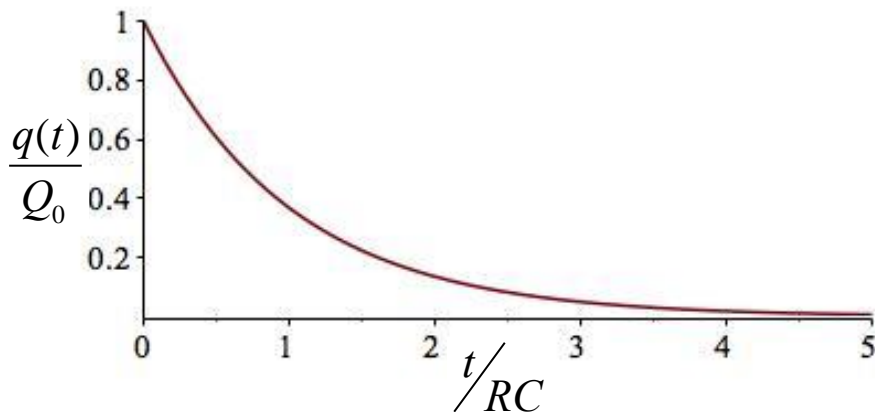

The RC time constant

The constant RC pops up in the exponential factor for both charging and discharging capacitors. What does it represent?

The units of RC is seconds: $[RC] = \frac{V}{A} \frac{C}{V} = \frac{C}{C/s} = s$

We call RC the “RC time constant” and it tells us how quickly a capacitor can charge or discharge.

$$RC \equiv \tau$$


After a time τ , the charge on a discharging capacitor is reduced by a factor of $1/e$. After a time $N\tau$, it is reduced by a factor of $1/e^N$

$$q(t) = Q_0 e^{-\frac{t}{\tau}}$$

Document Camera Calculation

An RC circuit is shown below. Initially the switch is open and the capacitor is uncharged. At time $t = 0$ s, the switch is thrown to the left, connecting the capacitor to the battery. At time $t = 15$ ms the switch is thrown to the right, connecting the capacitor to the resistor.

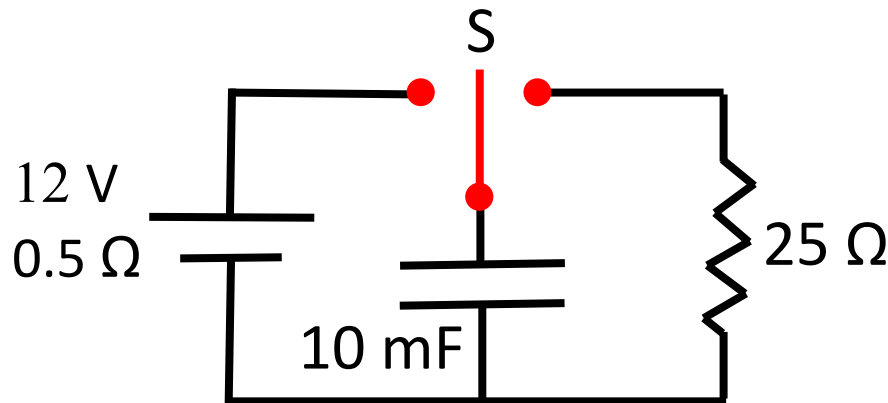- 1) How much charge builds up on the capacitor while it is connected to the battery?
- 2) What is the voltage across the resistor as a function of time as the capacitor discharges?
- 3) What is the ratio of the charging time to discharging time?



Power in circuits

Recall that **POWER** is the **rate at which work is done**.

$$P = \frac{W}{\Delta t}$$

A battery with voltage ΔV raises the **potential energy** of a single charge q by an amount $q\Delta V$. This is the **work done** by the battery. For N charges


$$P = \frac{Nq}{t} V = \left(\frac{Nq}{t} \right) V$$

$Nq/\Delta t$ is the number of **charges passing through the battery** in time Δt , i.e. it is the **current**

$$P = I \Delta V$$

Power Non-ideal Batteries

$$I = \frac{e}{(r + R)}$$

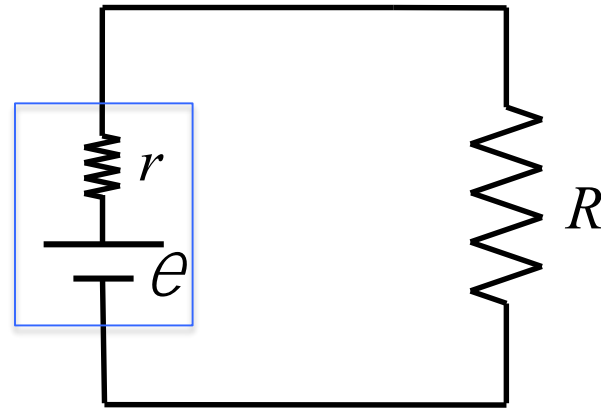


$$P_e = Ie = \frac{e^2}{R + r}$$

Power output required
by the emf source

$$P_R = I^2 R = \frac{e^2 R}{(R + r)^2}$$

Power dissipated by the
resistive load

Non-ideal Batteries: internal resistance

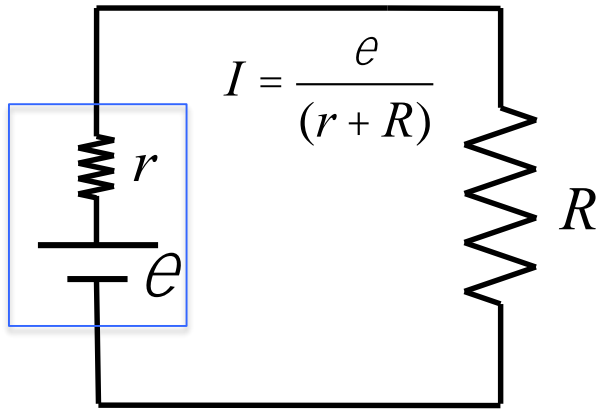

Conservation of energy requires power in must be equal to power out, but power by emf is not power dissipated by R .

$$P_e = Ie = \frac{e^2}{R + r} \quad P_r = I^2 R = \frac{e^2 R}{(R + r)^2}$$

Resolution: power dissipated by emf

$$P_r = I^2 r = \frac{e^2 r}{(R + r)^2} \quad \text{The emf must do more work because it fights against its own internal resistance}$$

Now we can verify that power in = power out

$$P_e = P_r + P_R = \frac{e^2 r}{(R + r)^2} + \frac{e^2 R}{(R + r)^2} = \frac{e^2 (R + r)}{(R + r)^2} = \frac{e^2}{R + r}$$