

①) charging the capacitor

$$t = 0 \rightarrow t = 15ms$$

Final $\tau = RC$ $R = r$ (internal resistance of battery)

$$\tau = rC \quad \tau = 0.5\Omega \cdot 10mF = 5ms$$

Total charging time $t = 15s$
 $t = 3\tau$

Calculating charge on capacitor after a very long time - maximum possible charge Q_f ($t \rightarrow \infty$)

$$Q_f = C \cdot \mathcal{E}$$

$$Q_f = 10mF \cdot 12V = 120mC$$

Calculating charge on capacitor after $t = 15ms$ (3τ) time.

$$q(t) = Q_f (1 - e^{-t/RC}) = Q_f (1 - e^{-t/\tau})$$

$$q(3\tau) = 120mC \cdot (1 - e^{-3\tau/\tau})$$

$$q(3\tau) = 120mC \cdot (1 - \underbrace{e^{-3}}_{0.049})$$

$$q(3\tau) = 114mC$$

Capacitor is not fully charged after 15ms.

①

2) What is the voltage?

We start at $Q_0 = 114 \text{ mC}$

→ this is the charge on capacitor after charging for 15 ms (see part 1)

$$q(t) = Q_0 e^{-t/RC}$$

$$i(t) = -\frac{dq}{dt} = -\left(\frac{Q_0}{-RC}\right) e^{-t/RC}$$

discharging current flows in opposite direction

$$i(t) = \frac{Q_0}{RC} e^{-t/RC}$$

$$V(t) = R \cdot i(t)$$

$$V(t) = \cancel{R} \cdot \frac{Q_0}{\cancel{RC}} e^{-t/RC}$$

$$V(t) = \frac{Q_0}{C} e^{-t/RC}$$

$$RC = 25 \Omega \cdot 10 \text{ mF} = 250 \text{ ms} = 0.25 \text{ s}$$

$$Q_0 = 114 \text{ mC}$$

$$C = 10 \text{ mF}$$


$$V(t) = \frac{114 \text{ mC}}{10 \text{ mF}} \cdot e^{-t/0.25 \text{ s}}$$

$$V(t) = 11.4 \text{ V} e^{-t/0.25 \text{ s}}$$

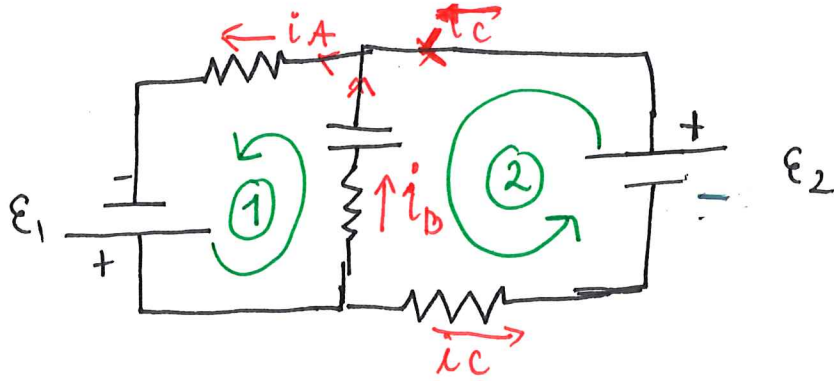3) Calculating the ratio of charging to discharging time

$$\frac{\tau_{\text{change}}}{\tau_{\text{discharge}}} = \frac{r \cdot \cancel{C}}{R \cdot \cancel{C}} = \frac{0.5 \Omega}{2.5 \Omega} = \frac{1}{5}$$

$$\text{or: } \frac{\tau_{\text{change}}}{\tau_{\text{discharge}}} = \frac{5 \text{ ms}}{250 \text{ ms}} = \frac{1}{50}$$



$$\varepsilon_1 > \varepsilon_2$$

$$i_A - i_C = i_B$$

$$\frac{dq}{dt} = i_B = i_A - i_C$$

$$(1) \quad \varepsilon_1 - i_B R - \frac{q(t)}{C} - i_A R = 0$$

$$(2) \quad \varepsilon_2 + \frac{q(t)}{C} + i_B R + i_C R = 0 \quad / \ominus$$

$$\varepsilon_1 - \varepsilon_2 - i_B R - \frac{q(t)}{C} - i_A R - \frac{q(t)}{C} - i_B R + i_C R = 0$$

$$\varepsilon_1 - \varepsilon_2 = 2i_B R + 2 \frac{q(t)}{C} + \underbrace{R(i_A - i_C)}_{R \cdot i_B}$$

$$\varepsilon_1 - \varepsilon_2 = 3i_B R + 2 \frac{q(t)}{C}$$

$$\varepsilon_1 - \varepsilon_2 = 3 \frac{dq}{dt} + 2 \frac{q(t)}{C} \quad / : 2$$

$$\frac{\varepsilon_1 - \varepsilon_2}{2} = \frac{3}{2} \frac{dq}{dt} + \frac{q(t)}{C}$$