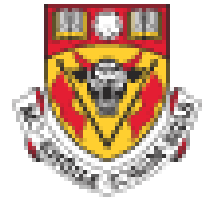


Electricity and Magnetism

- Physics 259 – L02
 - Lecture 35



UNIVERSITY OF
CALGARY

Chapter 27



Last time

- Chapters 26 and 27

This time




- Solve some examples


27 Circuits: continue of last section




Resistivity and temperature

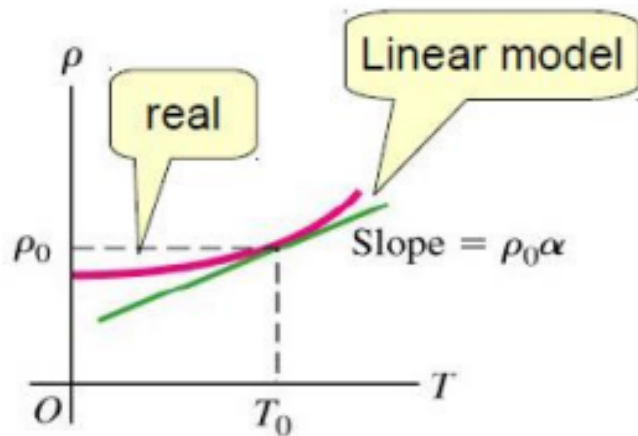

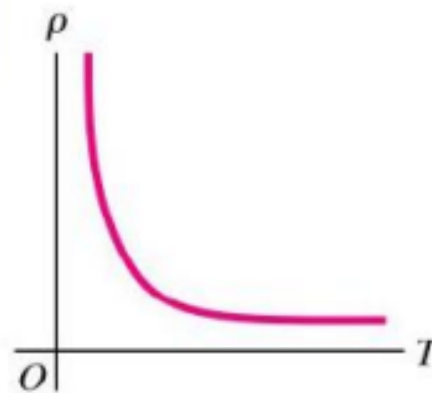(a) Metal:
 ρ increases
with increasing T



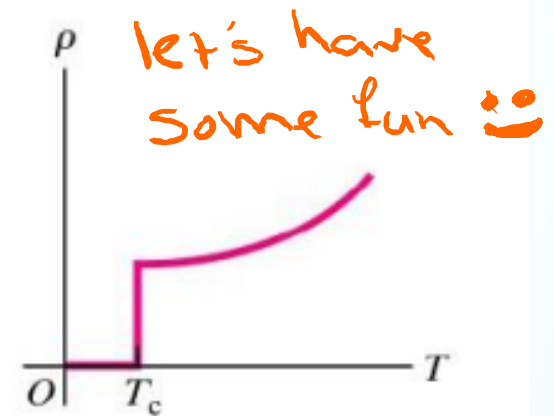(b) Semiconductor:
 ρ decreases
with increasing T



(c) Superconductor:
 $\rho = 0$ for $T < T_c$


<https://www.youtube.com/watch?v=hTT6nktJQBE>

Case 1: Charging a capacitor




$$i = i_0 e^{-t/RC}$$
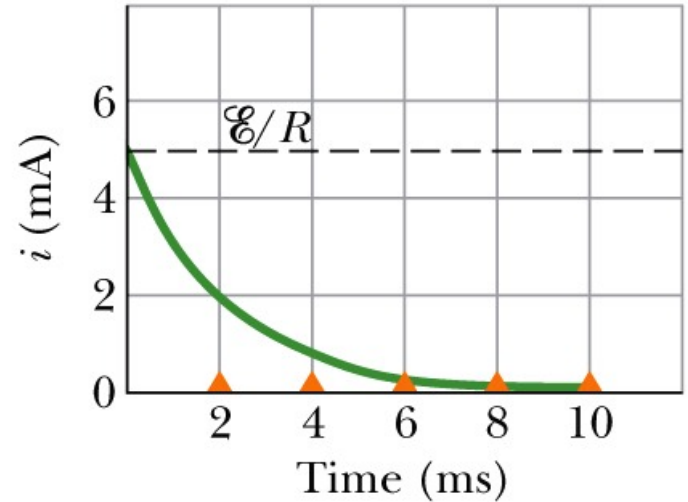
$$q = \varepsilon C (1 - e^{-t/RC}) = Q_f (1 - e^{-t/RC})$$



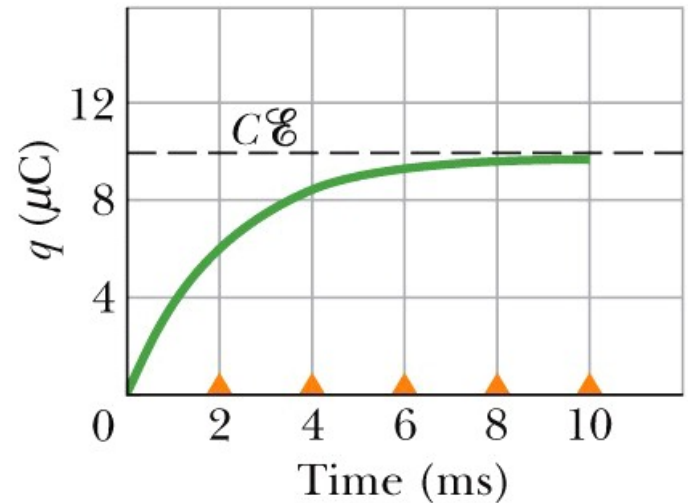
Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.


Case 2: Discharging a capacitor

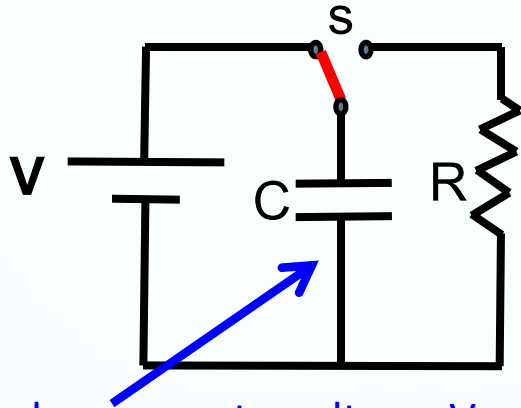Switch is connected to the left for a long time until $t=0^-$



Capacitor charges up to voltage V

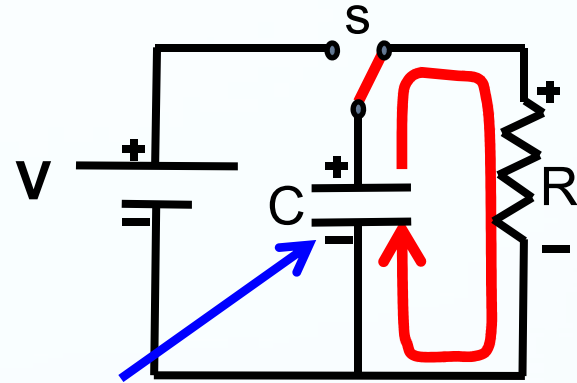Switch is suddenly flipped to the right at $t=0^+$




Capacitor discharges

$$q(t) = q_0 e^{-t/RC}$$

$$i(t) = i_0 e^{-t/RC}$$

$$q_0 = CV$$


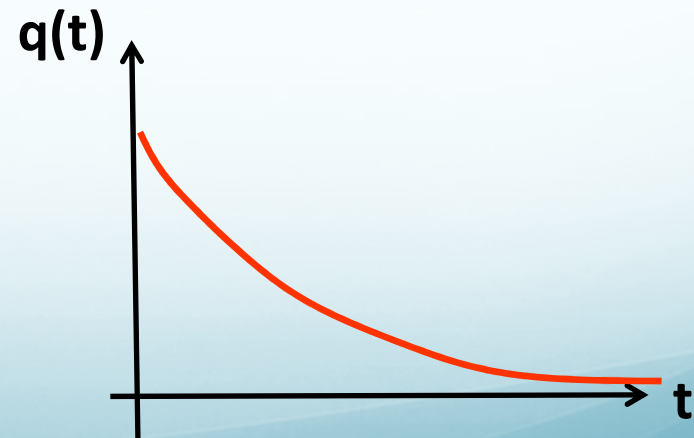


Charging/Discharging Capacitors

Charging:

$$q(t) = Q_f \left(1 - e^{-\frac{t}{RC}} \right)$$



$$i(t) = i_0 e^{-\frac{t}{RC}}$$

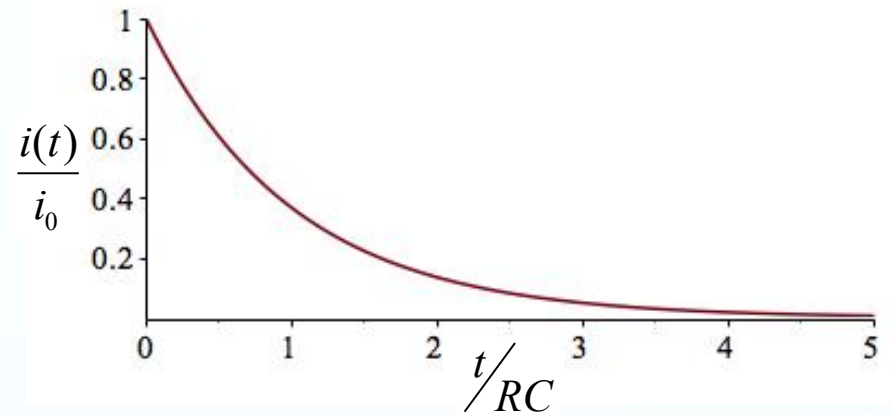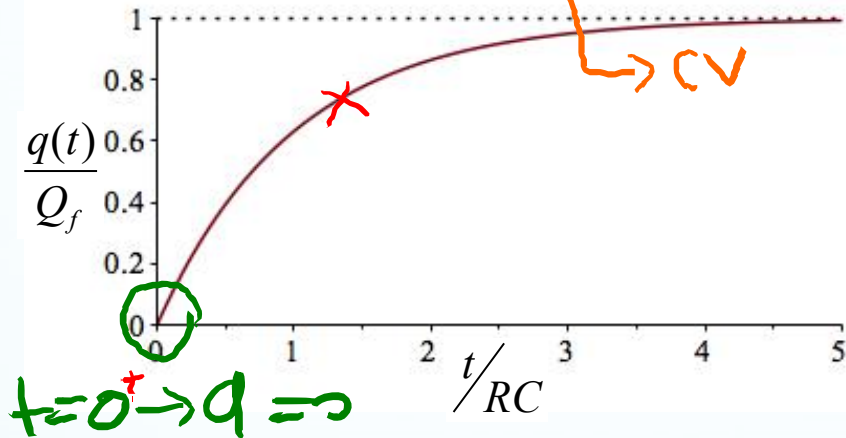

Discharging:

$$q(t) = Q_0 e^{-\frac{t}{RC}}$$

$$i(t) = i_0 e^{-\frac{t}{RC}}$$

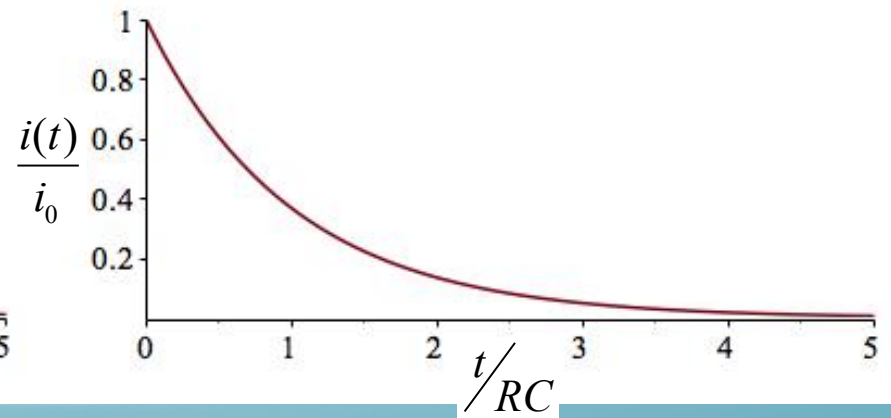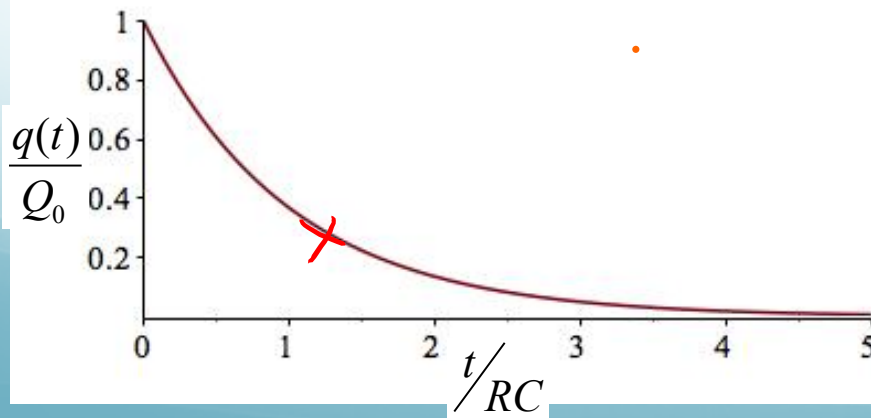


Top Hat Question

An RC circuit is shown below. Initially the switch is open and the capacitor is uncharged. At time $t=0$, the switch is closed. What is the voltage across the capacitor **immediately** after the switch is closed (time = $0+$)?

$$\text{at } t=0+ \rightarrow q=0 \rightarrow V = \frac{q}{C} \rightarrow V=0 \quad \text{😊}$$

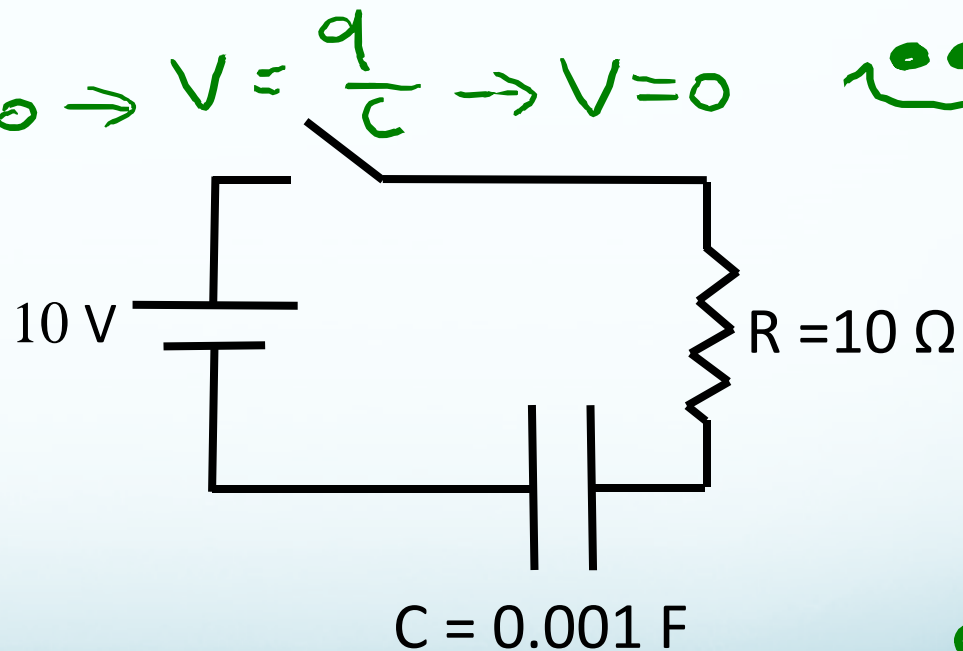- ✓ A. 0.0 V
- B. 10 V
- C. 5.0 V
- D. 1.0 V



Hint $\rightarrow C = \frac{q}{V} \rightarrow V = \frac{q}{C} \rightarrow \text{what is } q \text{ at } t=0+?$ 😊

The RC time constant

The constant RC pops up in the exponential factor for both charging and discharging capacitors. What does it represent?

The units of RC is seconds: $[RC] = \frac{V}{A} \frac{C}{V} = \frac{C}{C/s} = s$

We call RC the “**RC time constant**” and it tells us how quickly a capacitor can charge or discharge.

$$RC \equiv \tau \rightarrow \text{RC time constant}$$

After a time τ , the charge on a discharging capacitor is reduced by a factor of $1/e$. After a time $N\tau$, it is reduced by a factor of $1/e^N$




$$q(t) = Q_0 e^{-\frac{t}{\tau}}$$

$$q(t) = Q_0 e^{-t/\tau}$$

Sample question

An RC circuit is shown below. Initially the switch is open and the capacitor is uncharged. At time $t = 0$ s, the switch is thrown to the left, connecting the capacitor to the battery. At time $t = 15$ ms the switch is thrown to the right, connecting the capacitor to the resistor.

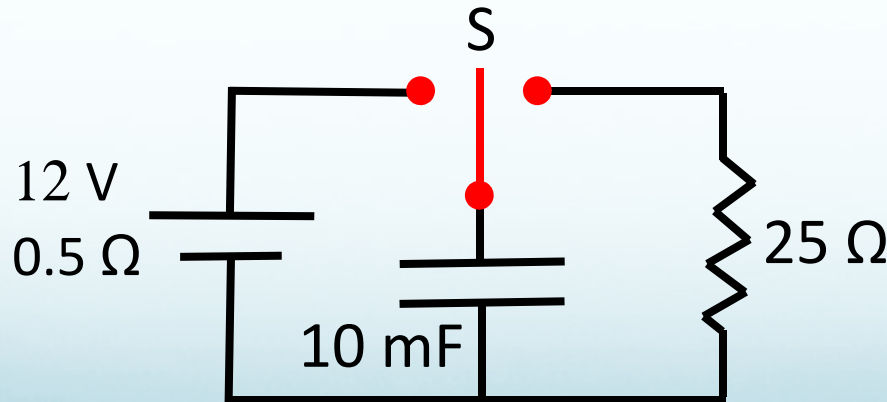- 1) How much charge builds up on the capacitor while it is connected to the battery?
- 2) What is the voltage across the resistor as a function of time as the capacitor discharges?
- 3) What is the ratio of the charging time to discharging time?




$$q(t) = Q_f(1 - e^{-t/\tau})$$

↙

$$Q_f = CV$$

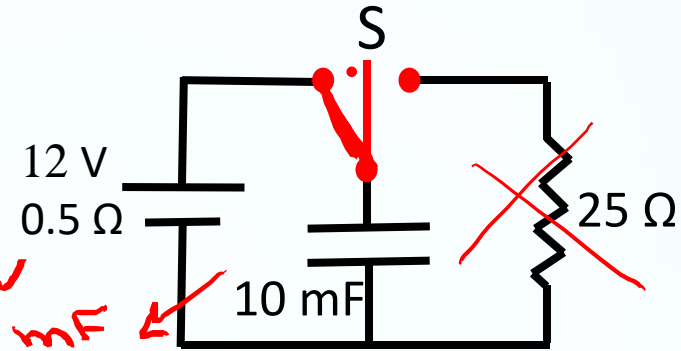Initially the switch is open and the capacitor is uncharged. At time $t = 0$ s, the switch is thrown to the left, connecting the capacitor to the battery. At time $t = 15$ ms the switch is thrown to the right, connecting the capacitor to the resistor.



$$V = 12 \text{ V}$$

$$C = 10 \text{ mF}$$

$$R = 0.5 \Omega$$

- 1) How much charge builds up on the capacitor while it is connected to the battery?

charging capacitor $\rightarrow q(t) = Q_f (1 - e^{-t/\tau})$

$Q_f \rightarrow$ fully charged capacitor $\rightarrow Q_f = CV = 10 \text{ mF} \times 12$

120 mC


$\tau = RC = 0.5 \Omega \times 10 \text{ mF} = 5 \text{ ms}$

\rightarrow at time $t = 15 \text{ ms} \rightarrow q(15 \text{ ms}) = Q_f (1 - e^{-t/\tau})$

$\rightarrow q(t) = 120 \text{ mC} (1 - e^{-15/5}) = 114 \text{ mC}$

$\rightarrow q(15 \text{ Sec}) = 114 \text{ mC}$ 12

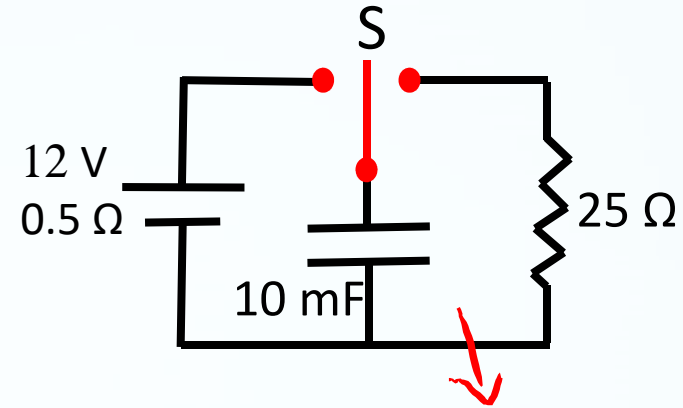Initially the switch is open and the capacitor is uncharged. At time $t = 0$ s, the switch is thrown to the left, connecting the capacitor to the battery. At time $t = 15$ ms the switch is thrown to the right, connecting the capacitor to the resistor.



2) What is the voltage across the resistor as a function of time as the capacitor discharges?

$$q_0 = 114 \text{ mC}$$

$$R = 25 \Omega$$

$$C = 10 \text{ mF}$$

discharging capacitor \Rightarrow

$$V = R I(t) = R I_0 e^{-t/RC} \quad I_0 = \frac{q_0}{RC}$$

$$I(t) = -\frac{d}{dt} q(t) = -\frac{d}{dt} q_0 e^{-t/RC} \rightarrow I(t) = \frac{q_0}{RC} e^{-t/RC}$$


$$\rightarrow I(t) = \frac{q_0}{RC} e^{-t/RC} = I_0 e^{-t/RC} \Rightarrow I_0 = \frac{q_0}{RC}$$

$$\rightarrow V = R I_0 e^{-t/RC} = \frac{q_0}{C} e^{-t/RC}$$

$$\rightarrow V = (11.4 \text{ V}) e^{-t/0.25}$$

$$RC = 25 \times 10 \text{ mF} = 250 \text{ ms}$$

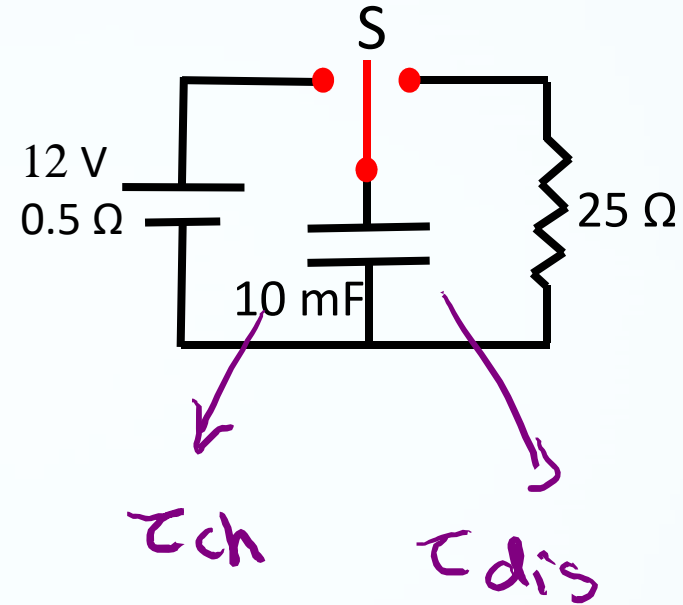Initially the switch is open and the capacitor is uncharged. At time $t = 0$ s, the switch is thrown to the left, connecting the capacitor to the battery. At time $t = 15$ ms the switch is thrown to the right, connecting the capacitor to the resistor.



3) What is the ratio of the charging time to discharging time?

$$\tau_{\text{charging}} = rC$$

\Rightarrow

$$\tau_{\text{discharging}} = RC$$

$$\frac{\tau_{ch}}{\tau_{dis}} = \frac{rC}{RC} = \frac{r}{R} = \frac{0.5}{25}$$


$$\rightarrow \frac{\tau_{\text{charging}}}{\tau_{\text{discharging}}} = \frac{1}{50}$$

Top Hat Question

An RC circuit is shown below. Initially the switch is open and the capacitor is fully charged. At time $t = 0$, the switch is closed.

How much charge is left on the capacitor plates after $t = 10$ ms?

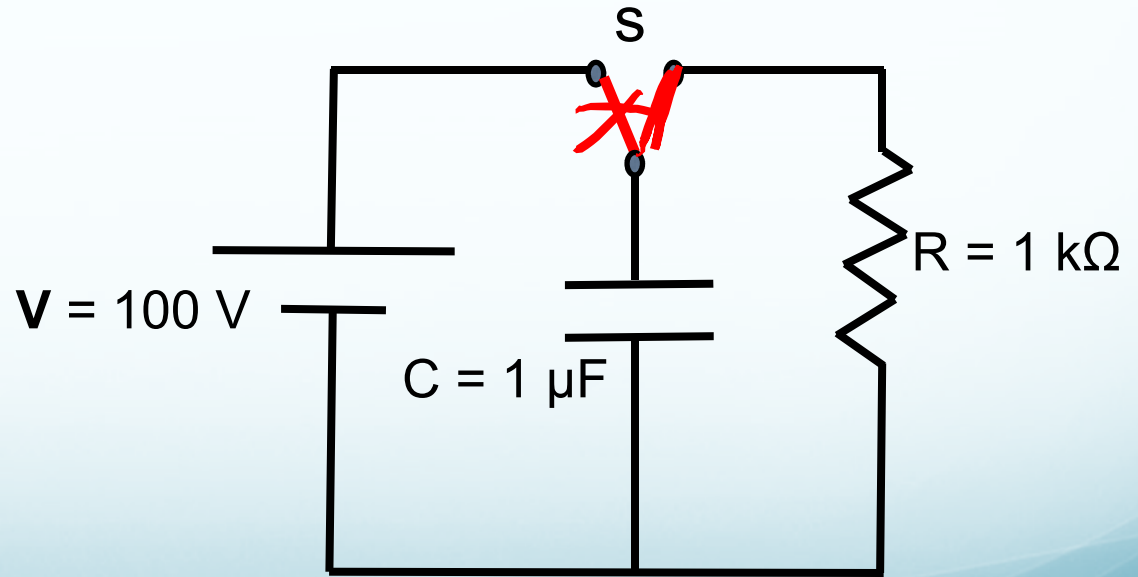- A. 0.67 nC
- B. 14 μC
- C. 37 μC
- D. 4.5 nC




Top Hat Question

An RC circuit is shown below. Initially the switch is open and the capacitor is fully charged. At time $t = 0$, the switch is closed.

How much charge is left on the capacitor plates after $t = 10$ ms?

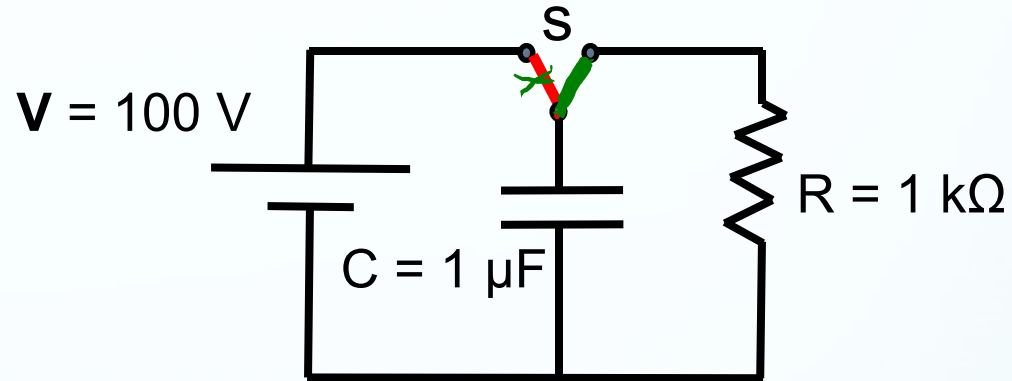- A. 0.67 nC
- B. 14 μC
- C. 37 μC
- D. 4.5 nC



discharging $\rightarrow q(t) = q_0 e^{-t/RC}$

$q_0 \rightarrow q_f$ of charging $\Rightarrow q_0 = CV =$

$$\begin{aligned} V &= 100 \text{ V} \\ R &= 1 \text{ k}\Omega \\ C &= 1 \mu\text{F} \end{aligned}$$

$$\rightarrow q(t) = (100 \mu\text{C}) e^{-\frac{10}{1 \text{ ms}}} = 4.54 \text{ nC}$$

This section we talked about:

Chapter 27

See you on Friday

