

Electricity and Magnetism

- Physics 259 – L02
- Lecture 34



UNIVERSITY OF
CALGARY

Chapters 26 & 27



Last time


- Chapter 25- Capacitance

This time




- Chapters 26 and 27

26-4 Ohm's Law

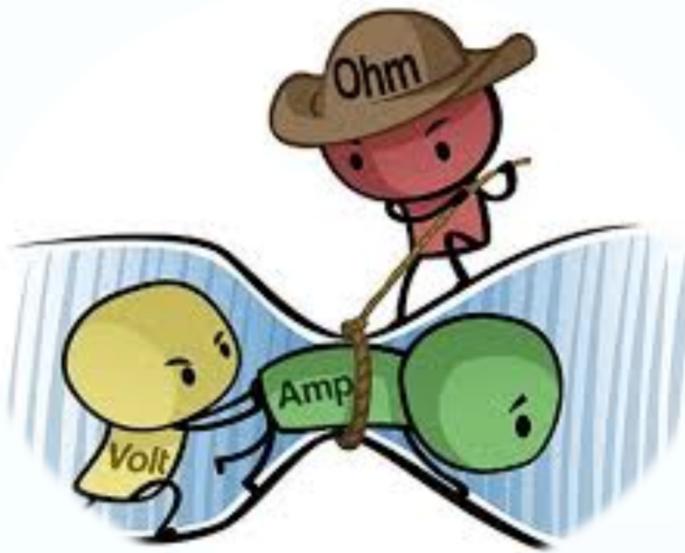

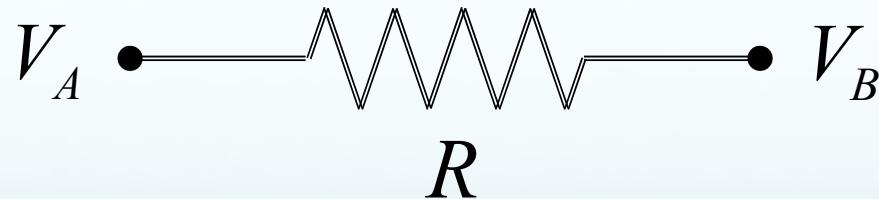
When a voltage difference ΔV is applied across a resistor R , the voltage difference causes electrons to flow through the resistor




This flow of electrons is the electric current I . These quantities are related by Ohm's Law:

$$\Delta V = IR$$

Ohmic vs non-Ohmic devices

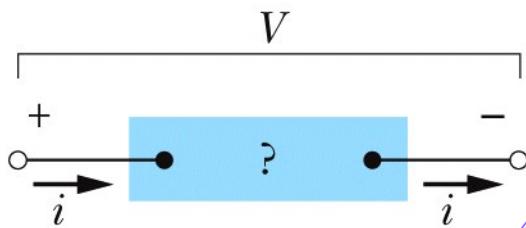


$$V = R I \rightarrow R = \frac{V}{I}$$

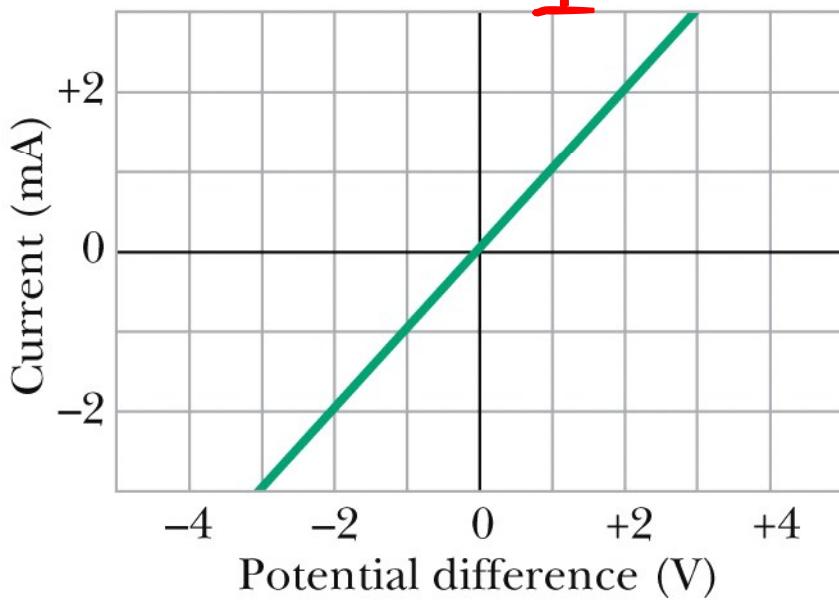

(b)

Materials with isotropic electrical properties

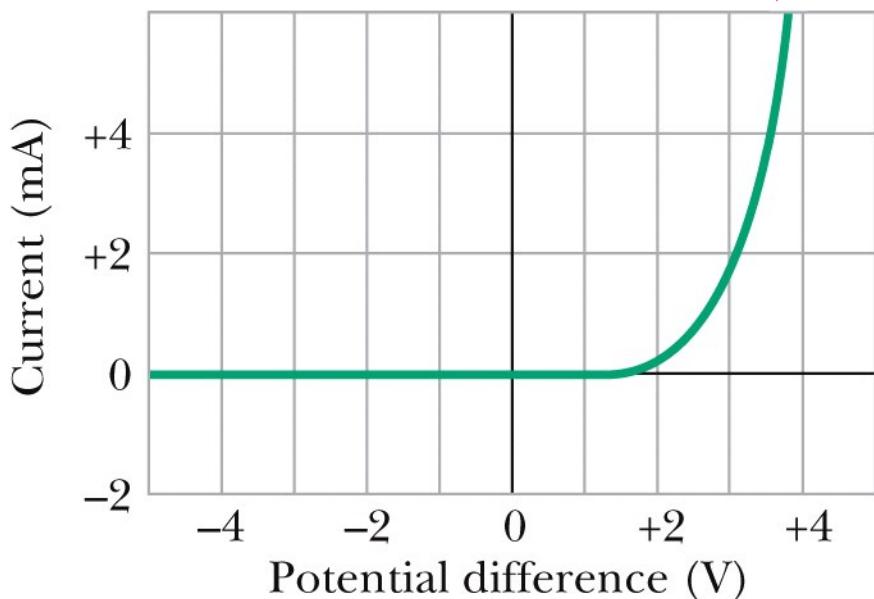Materials with anisotropic electrical properties (pn junction diode)




(c)

TopHat Question

A cylindrical resistor is composed of 1/3 copper and 2/3 Tungsten as shown ($\rho_{Cu} = 1.69 \times 10^{-8} \Omega m$, and $\rho_W = 5.25 \times 10^{-8} \Omega m$). The radius of the cylinder is $R = 0.105 \text{ mm}$, and it is $L = 5.26 \text{ cm}$ long.

Each piece has a resistance. Are these resistors in series or in parallel?

- A. Series
- B. Parallel
- C. Neither

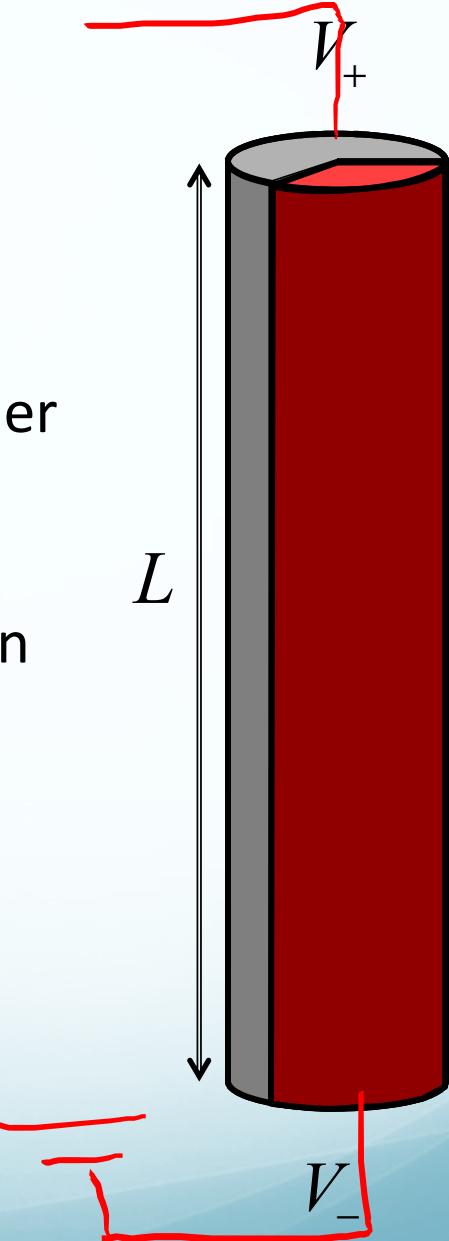

TopHat Question



A cylindrical resistor is composed of 1/3 copper and 2/3 Tungsten as shown ($\rho_{Cu} = 1.69 \times 10^{-8} \Omega m$, and $\rho_W = 5.25 \times 10^{-8} \Omega m$). The radius of the cylinder is $R = 0.105 \text{ mm}$, and it is $L = 5.26 \text{ cm}$ long.

Each piece has a resistance. Are these resistors in series or in parallel?


A. Series

B. Parallel

C. Neither

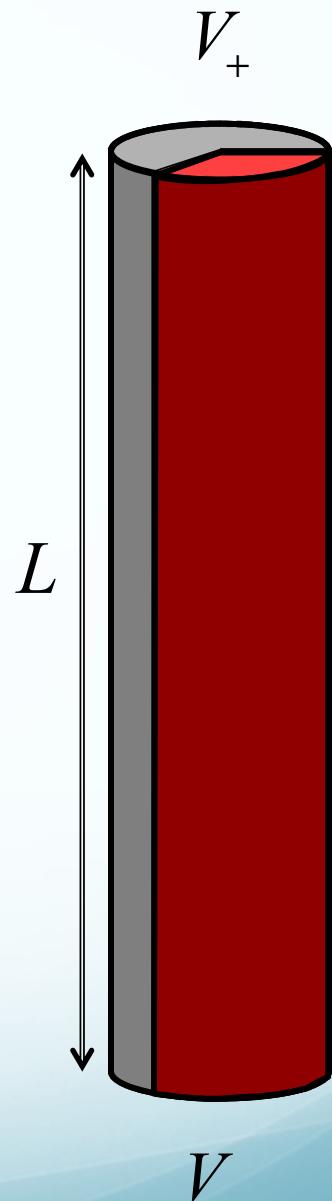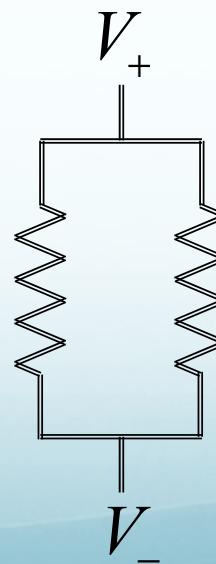

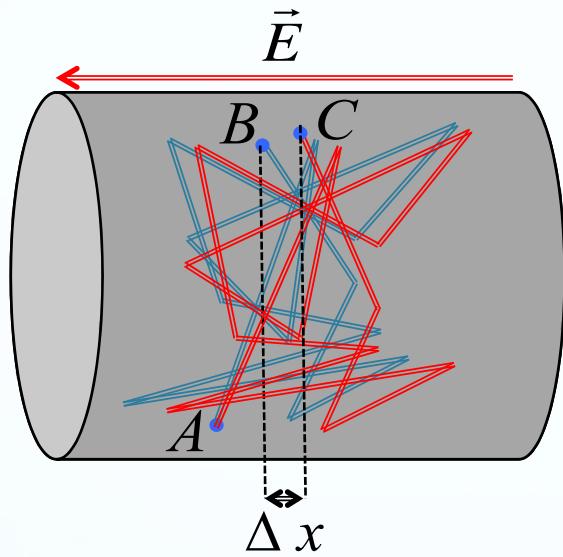Microscopic view of Ohm's law (resistivity)



Electrons bounce around inside the metal at speeds very high speeds on the order of 0.5% light speed.

When an electric field is applied in the conductor, there is a net force on the electrons, leading to “drift speed”

$$v_d = \frac{J}{ne}$$

microscopic picture of resistivity:

$$\rho = \frac{m}{ne^2 \tau}$$

$$\rho - \rho_0 = \rho_0 \alpha (T - T_0)$$

Temperature Dependent Resistance




$$R - R_0 = R_0 \left(\frac{2}{3} \alpha \right) (T - T_0)$$

Proof: Appendix 2-Chapter 26

$$\rho - \rho_0 = \rho_0 \alpha (T - T_0) \quad \leftarrow$$

Resistance vs. Temperature

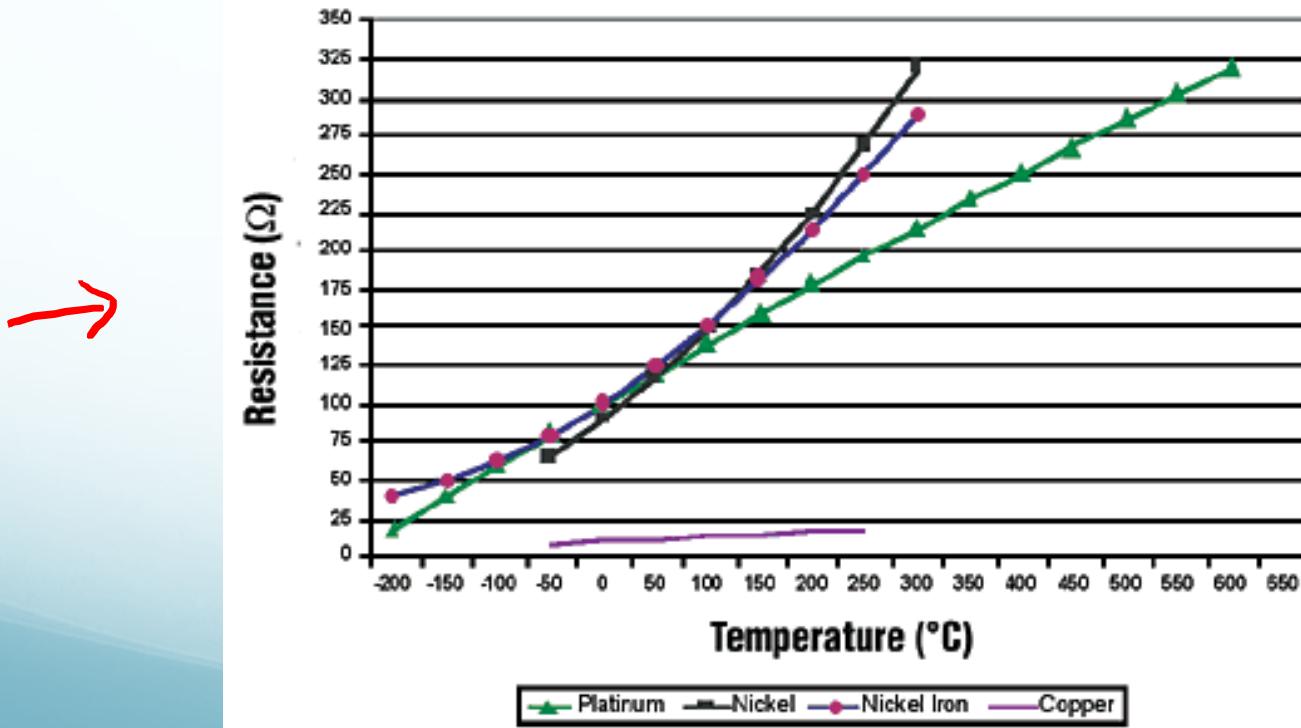

26-5 Power in circuits

Recall that **POWER** is the **rate at which work is done**

$$P = \frac{W}{\Delta t}$$

A battery with voltage ΔV raises the **potential energy** of a single charge q by an amount $q \Delta V$. This is the **work done** by the battery. For N charges

$$P = \frac{Nq \Delta V}{\Delta t} = \left(\frac{Nq}{\Delta t} \right) V = IV$$


Power in circuits →

$$P = IV = RI^2 = \frac{V^2}{R}$$


27 Circuits: continue of last section




Grounding

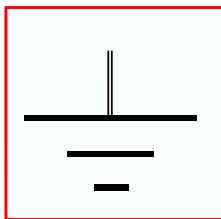

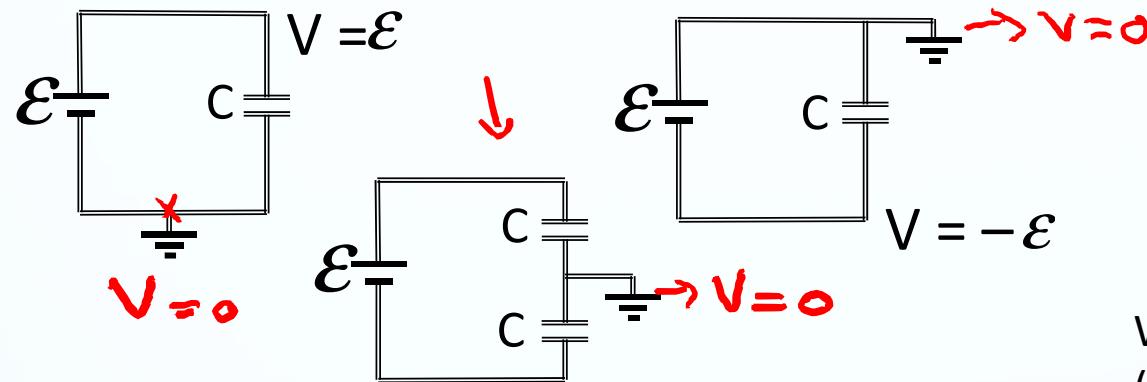This symbol is called “ground” and it represents the place in the circuit where $V=0$.




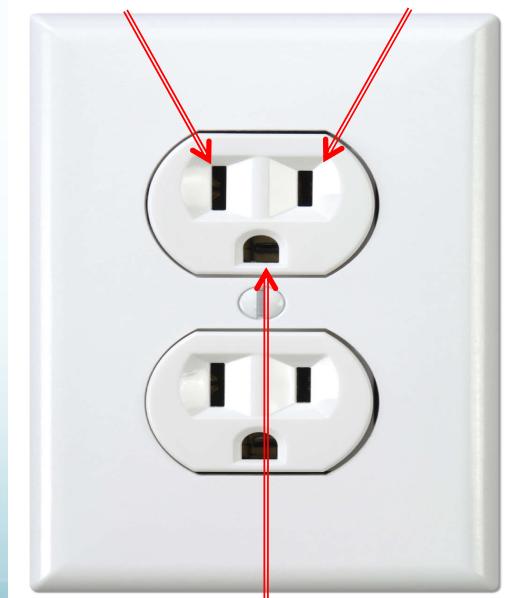Wide slot
(neutral) Narrow slot
(hot/live)




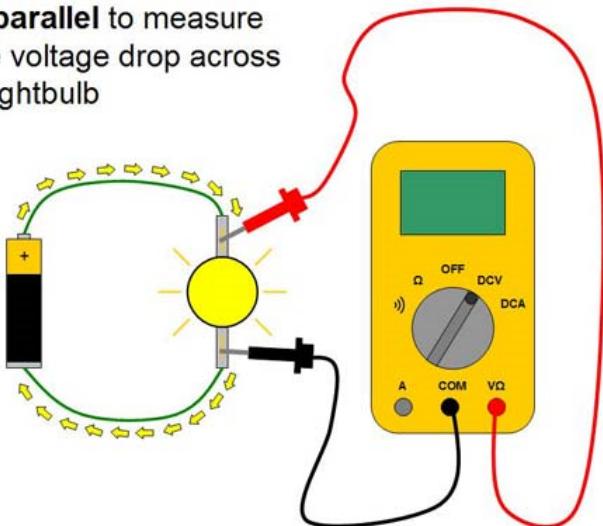27-3 The Ammeter and The Voltmeter


Connect a multimeter in **parallel** to measure the voltage drop across a lightbulb



<https://tinyurl.com/zpbg36w>

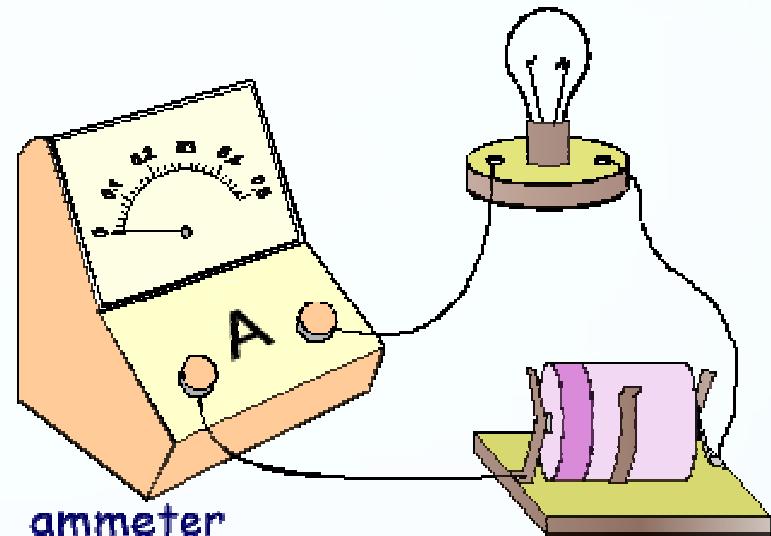



<https://tinyurl.com/jlktr03>

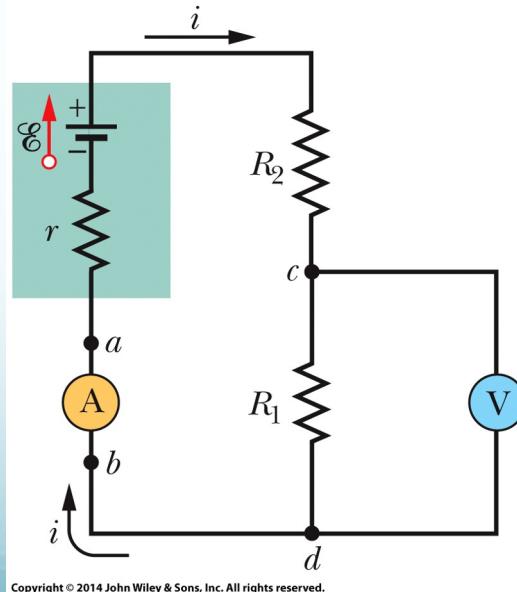

Non-ideal Batteries: internal resistance

Appendix 2-Chapter 26

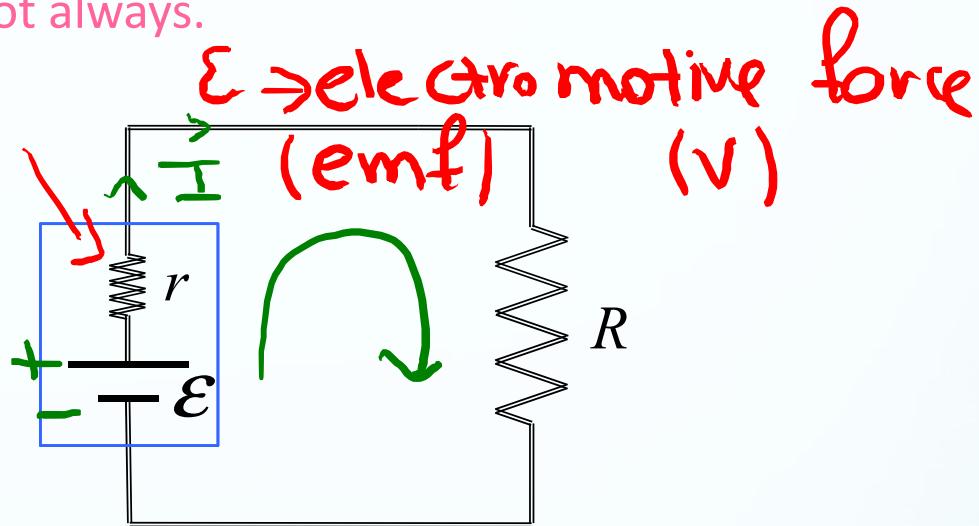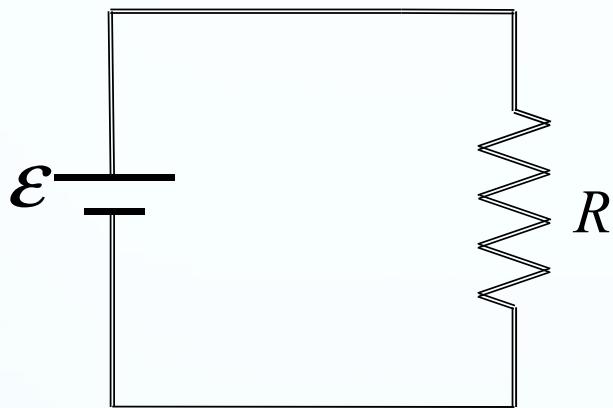
Every voltage source has **some** internal resistance to it. Usually this can be ignored but not always.



The internal resistance simply acts as a resistor in series with the rest of the circuit.

$$\mathcal{E} - Ir - IR = 0 \rightarrow I = \frac{\mathcal{E}}{(r + R)}$$


$$\mathcal{E} - I(r + R) = 0$$

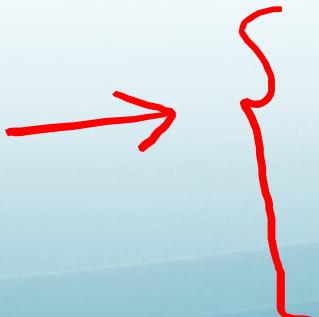

$$P_{\mathcal{E}} = I\mathcal{E} = \frac{\mathcal{E}^2}{R+r}$$

$$P_R = I^2 R = \frac{\mathcal{E}^2 R}{(R+r)^2}$$

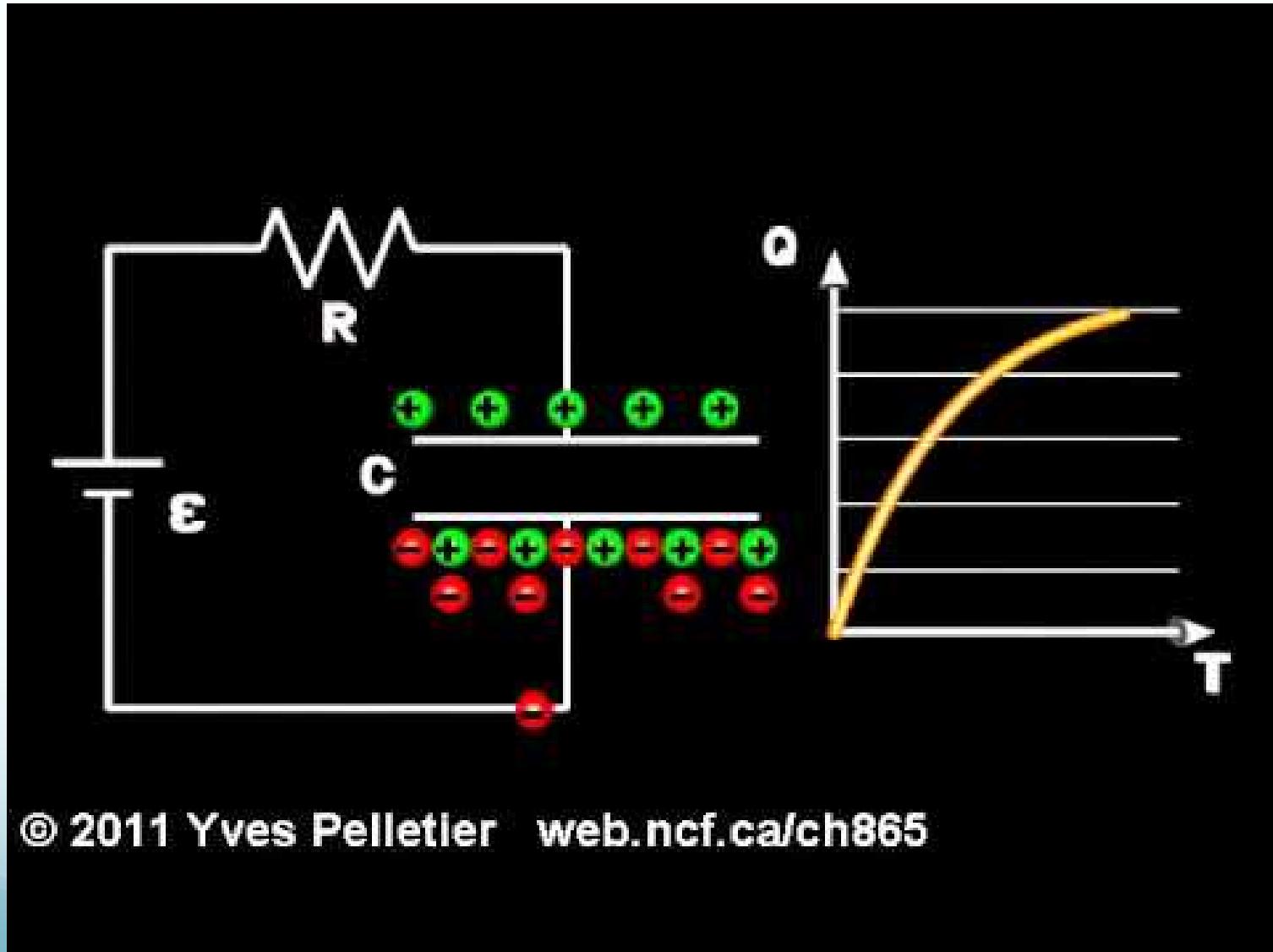27-4 RC Circuits (resistors + capacitors)




© 2011 Yves Pelletier web.ncf.ca/ch865

Until now → steady and continuous currents

many important circuit applications use a combination of capacitors and resistors to produce time dependent currents

Examples: wireless signals in a cordless phone, remote control, etc.

Simple RC Series Circuit

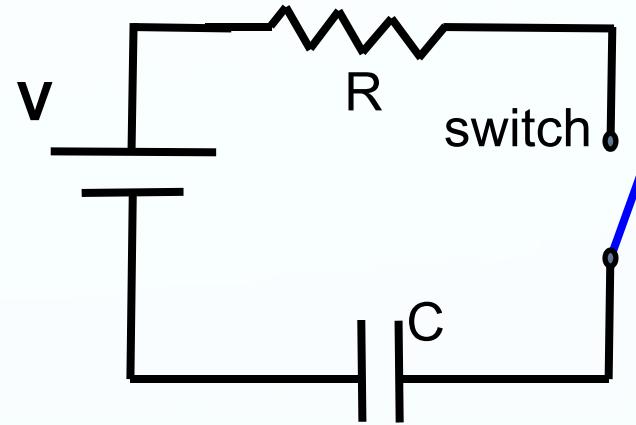

Open switch →

- ✓ no current can flow
- ✓ charge and voltage on capacitor
→ Zero

Closed switch for a long time →

- ✓ Charge on capacitor $Q = CV$
- ✓ Voltage across capacitor is V and no current flows in the circuit.


What happens immediately after switch is closed or opened?

We get time dependent currents!



Case 1: Charging a capacitor


(a) Capacitor initially uncharged

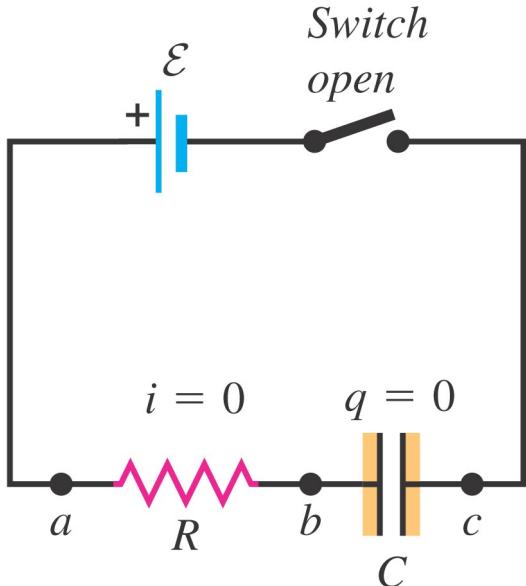


Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley.

R could be the internal resistance of the battery, resistance of the connecting wires, an actual resistance in the circuit or combination of all the above.

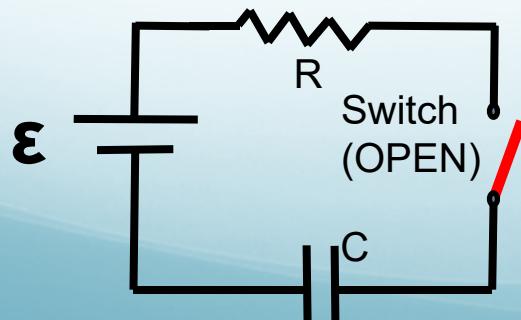Switch is open for a long time before $t=0$



Switch is suddenly closed at $t=0$

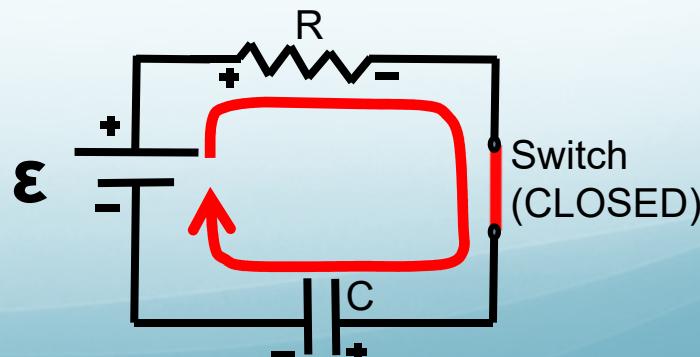

Case 1: Charging a capacitor

$$\epsilon - IR - \frac{q}{C} = 0 \rightarrow \frac{d}{dt} \rightarrow$$

~~$$\frac{d\epsilon}{dt} - R \frac{dI}{dt} - \frac{1}{C} \frac{dq}{dt} = 0$$~~

I


$$-R \frac{dI}{dt} - \frac{1}{C} I = 0 \rightarrow -R \frac{dI}{dt} = \frac{1}{C} I \rightarrow \frac{dI}{dt} = -\frac{1}{RC} I$$

$$\rightarrow \frac{dI}{I} = -\frac{1}{RC} dt \xrightarrow{\text{integral}}$$


$$I = \frac{V}{R} e^{-(t/t_{RC})}$$

$$I = \frac{dq}{dt} \rightarrow q = \int I dt \rightarrow q = CV(1 - e^{-t/RC})$$

Switch is suddenly closed at $t=0$

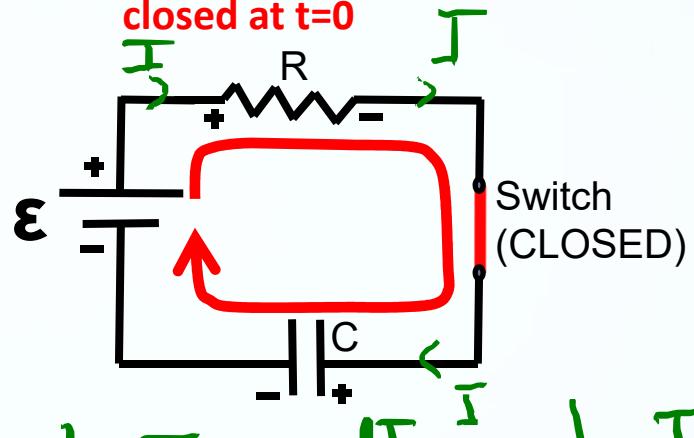


Case 1: Charging a capacitor

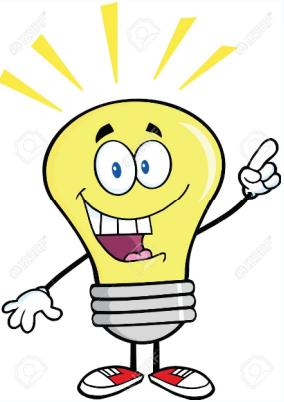


$$i = i_0 e^{-t/RC}$$

$$q = \epsilon C \left(1 - e^{-t/RC}\right) = Q_f \left(1 - e^{-t/RC}\right)$$

↳ *Q_f* of battery

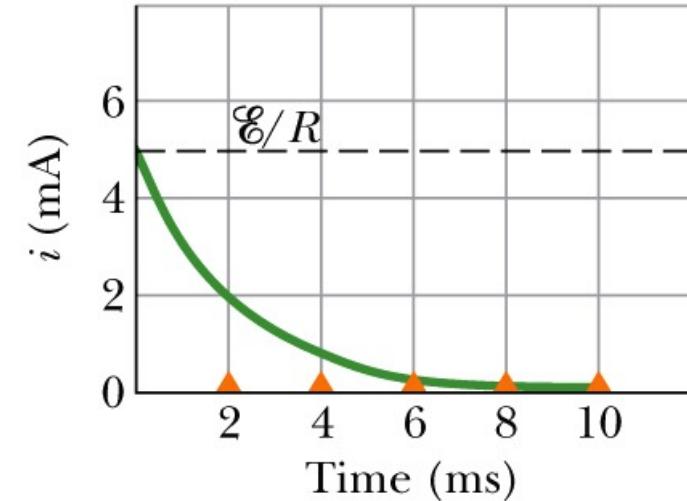

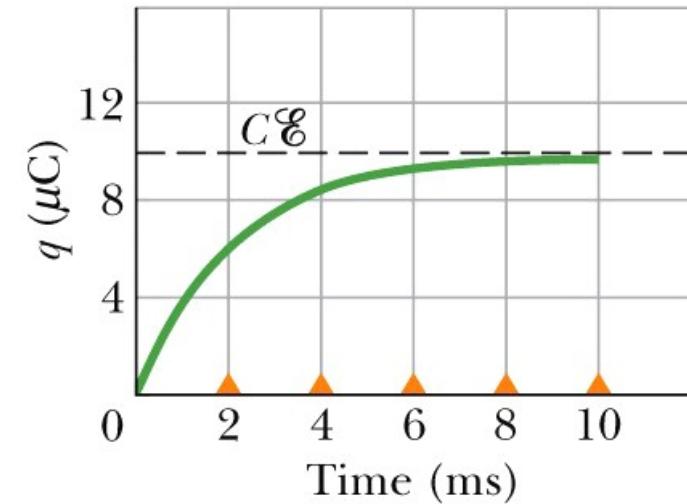
Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.


Case 2: Discharging a capacitor

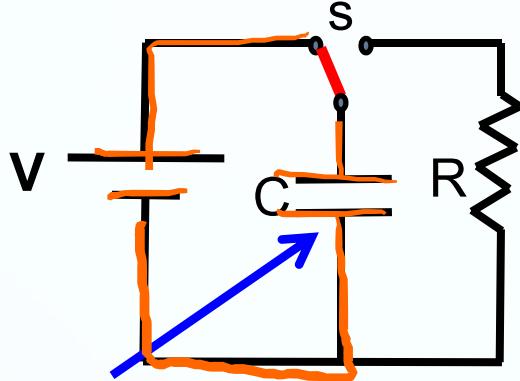Switch is connected to the left for a long time until $t=0-$



Capacitor charges up to voltage V

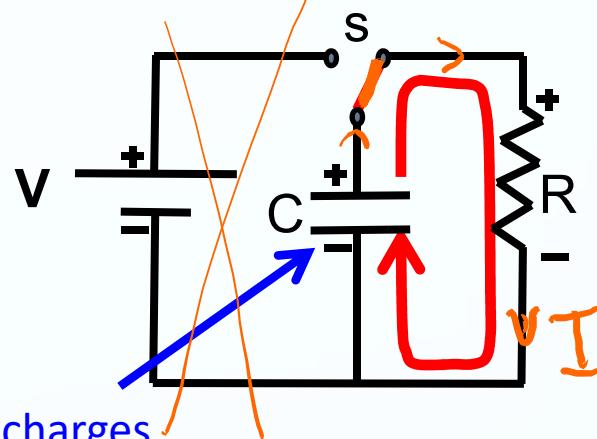Switch is suddenly flipped to the right at $t=0+$



Capacitor discharges

Once the switch is flipped to right \rightarrow

$$\frac{q(t)}{C} - iR = 0 \Rightarrow \boxed{\frac{q}{RC} = i} - \frac{dq}{dt}$$


NOTE here $dq < 0$

Solving for the charge $q(t)$ on the capacitor \rightarrow

$$q(t) = q_0 e^{-t/RC}$$

$$q_0 = CV$$


$$i(t) = i_0 e^{-t/RC}$$

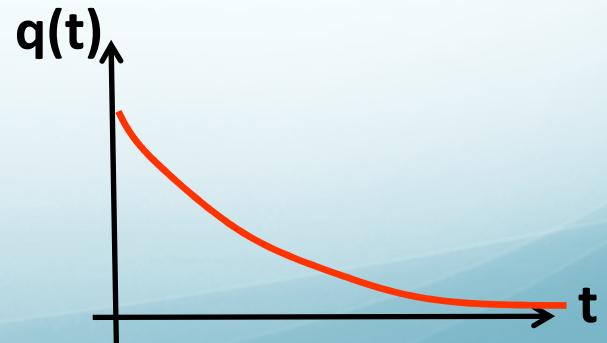

Top Hat Question

An RC circuit is shown below. Initially the switch is open and the capacitor is uncharged. At time $t=0$, the switch is closed. What is the voltage across the capacitor **immediately** after the switch is closed (time = 0^+)?

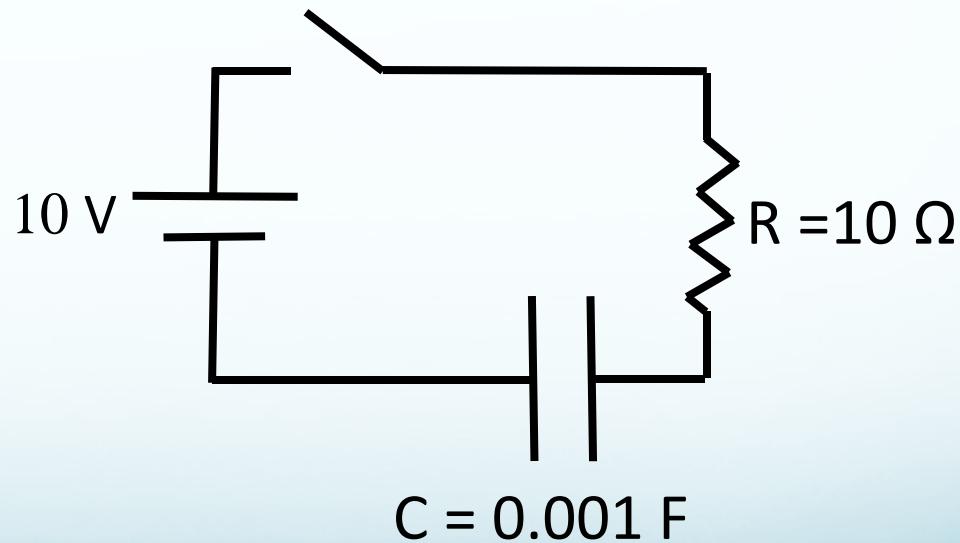- A. 0.0 V
- B. 10 V
- C. 5.0 V
- D. 1.0 V



This section we talked about:

Chapters 26 and 27

See you on Thursday

