

Monday March 13, 2017

# Last time:


- Calculation of charge
- Applications of dielectrics and capacitors
- Group activity

# Today:

- Electric current: a microscopic picture
- Current density (a vector) vs current (a scalar)
- Electric fields in conductors and electron drift speed
- Resistance as geometric quantity
- Resistors in series
- Resistors in parallel

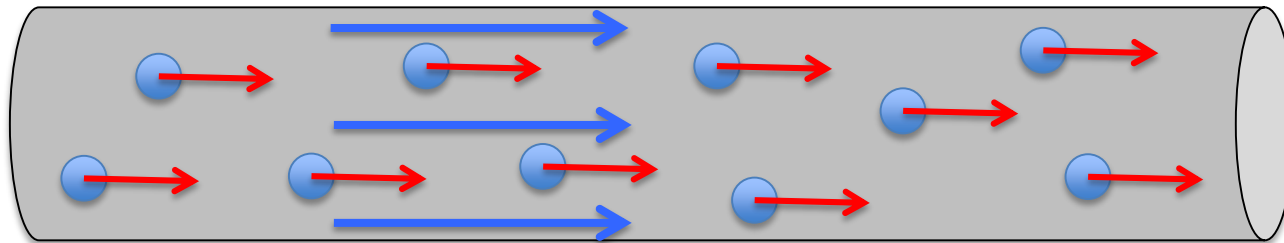
# Where we're going

We will be using what we have been building up to talk about **moving charges** in electric circuits. This is no longer electrostatic equilibrium, so **conductors are allowed to have non-zero electric field inside** (this is what causes the charges to move).



First, we will take a closer look at what happens inside conductors and use this to define what an electric current is

# Definition of current

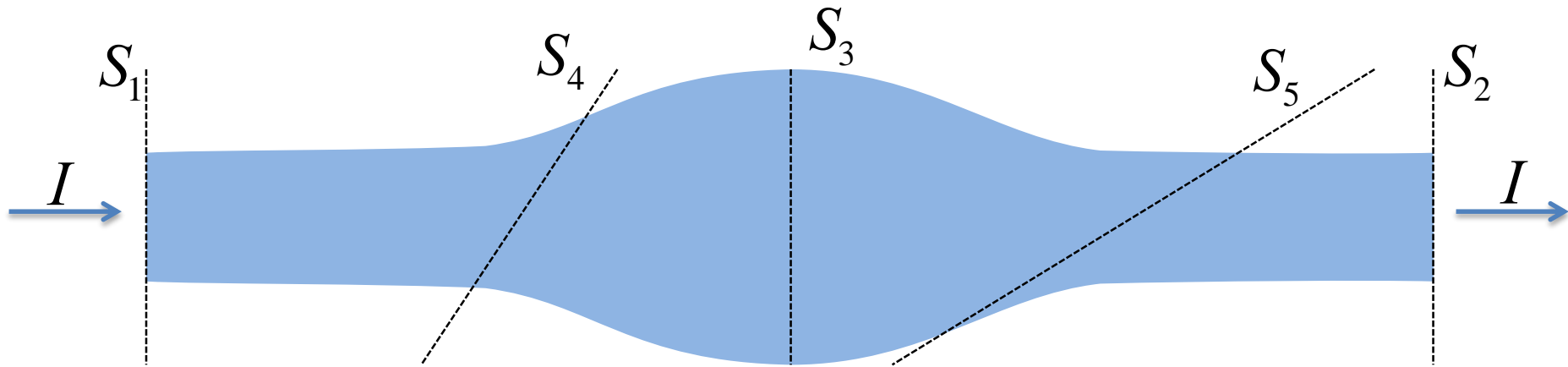


Total amount of charge  
flowing past this  
surface in a time  $\Delta t$

$$I = \frac{dq}{dt}$$

Total amount of charge  
flowing past this surface  
in the same time  $\Delta t$

Total amount of charge flowing through **ANY** surface in a time  $\Delta t$  must be constant, otherwise charges would begin to accumulate. **Current in a wire is constant.**

# Current and Current Density

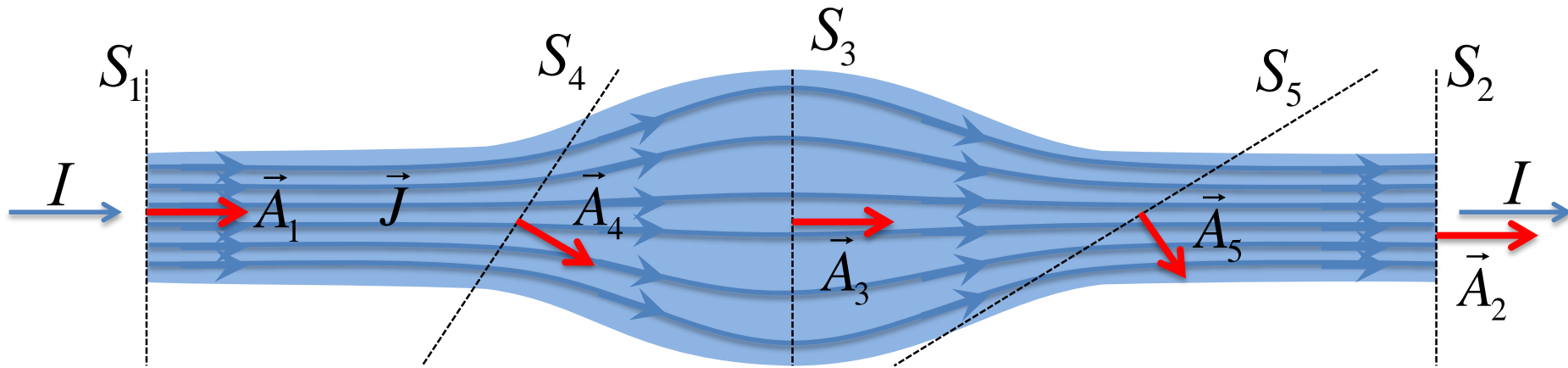


Total amount of charge flowing through **ANY** surface in a time  $\Delta t$  must be constant. This should be reminiscent of **FLUX**.

$$I = \oint_S \vec{J} \cdot d\vec{A}$$

The current in a wire is the flux of charge carriers (i.e. electrons) through a surface.

Since the current is constant, the flux through any cross-sectional surface must be the same.

# Current and Current Density

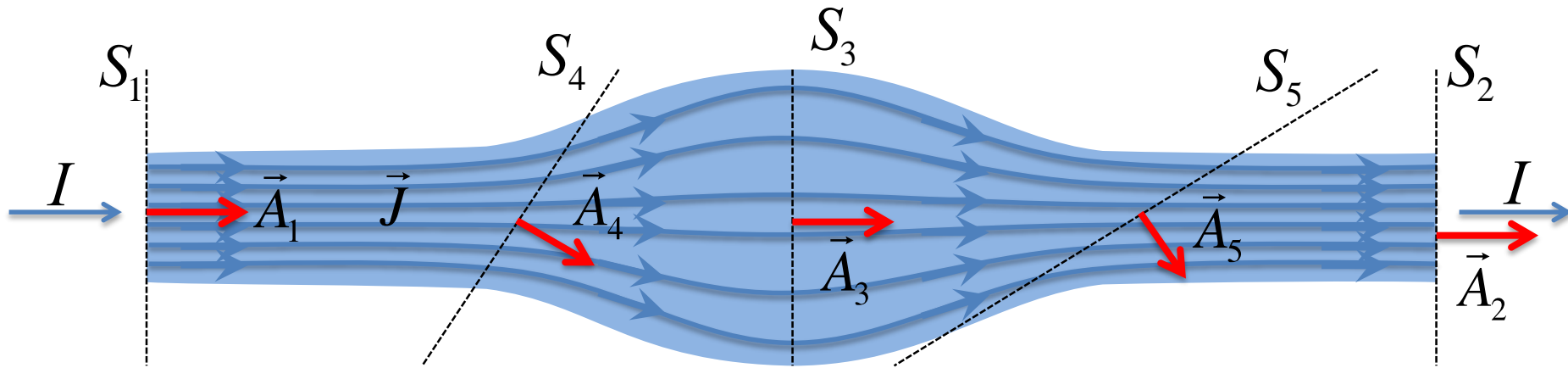


We call  $\vec{J}$  the **current density**. It encodes information about:

- The density of conduction electrons in the conductor
- The net velocity of these conduction electrons

The current  $I$  is then interpreted as the number of charges passing through a surface in a specified direction. Note: current density is a vector, current is a scalar.

# Inside a conductor

(a) No electric field

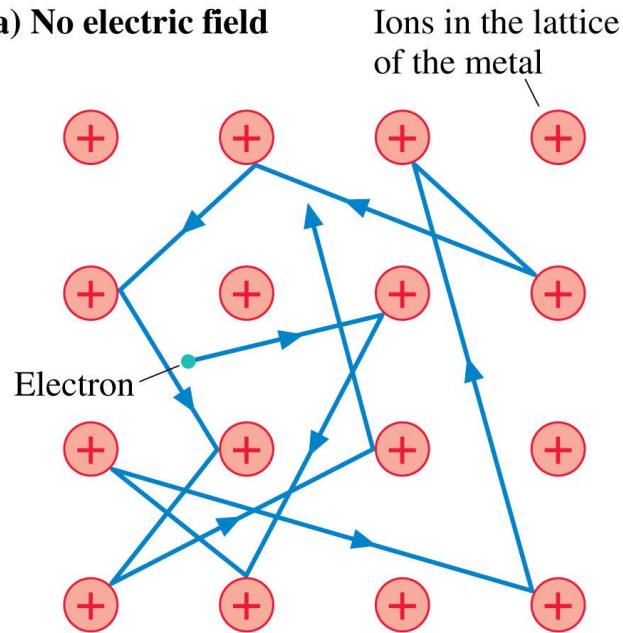


The electron has frequent collisions with ions, but it undergoes no net displacement.

© 2013 Pearson Education, Inc.

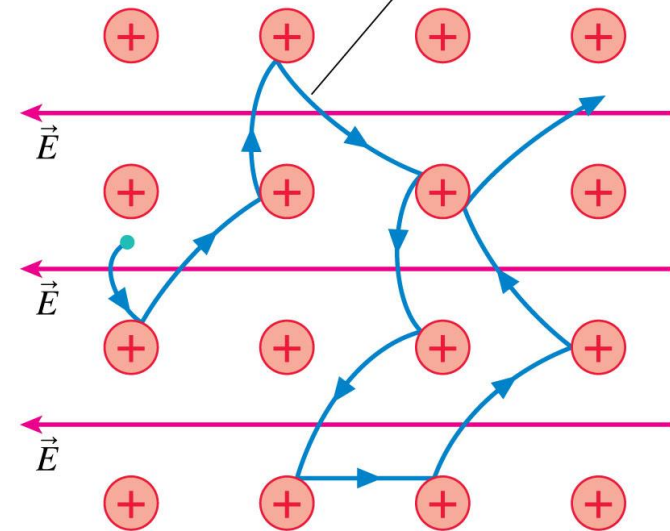(b) With an electric field

Parabolic trajectories in the electric field




Net displacement

A net displacement in the direction opposite to  $\vec{E}$  is superimposed on the random thermal motion.

© 2013 Pearson Education, Inc.

Net result: electrons move at an average net “drift speed”  $v_d$

# Current Density

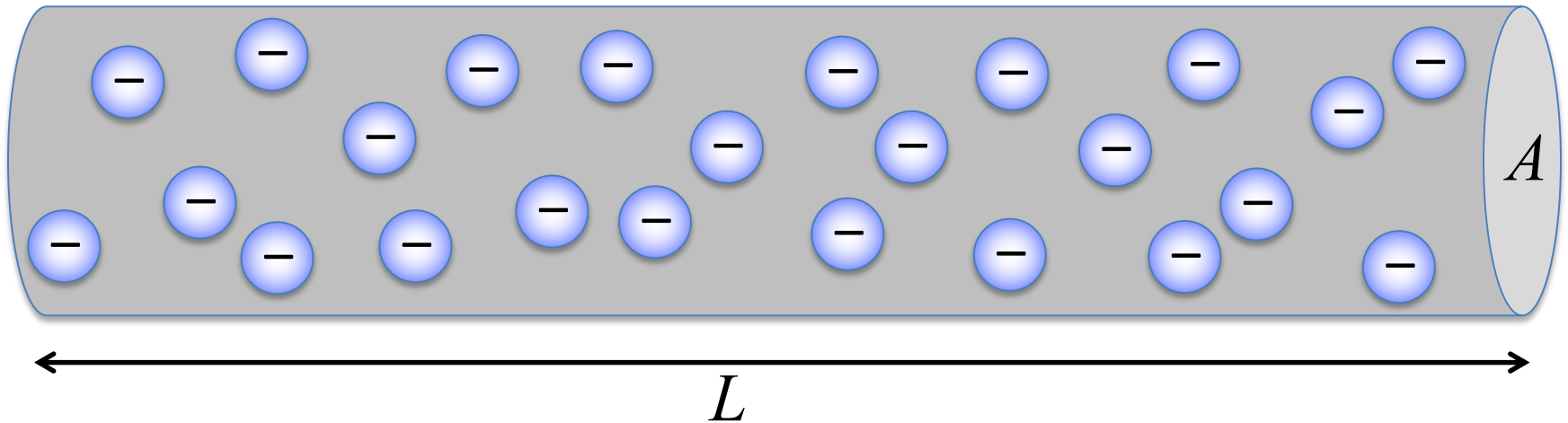

If the volume density of conduction electrons is  $n_e$ , then the amount of charge contained in a length  $L$  of the wire is


$$q = n(AL)e$$

The time it takes each charge to travel a distance  $L$  is  $t = L/v_d$ , so the current is

$$i = \frac{q}{t} = \frac{n(AL)e}{L/v_d} = nAev_d$$



# Current Density

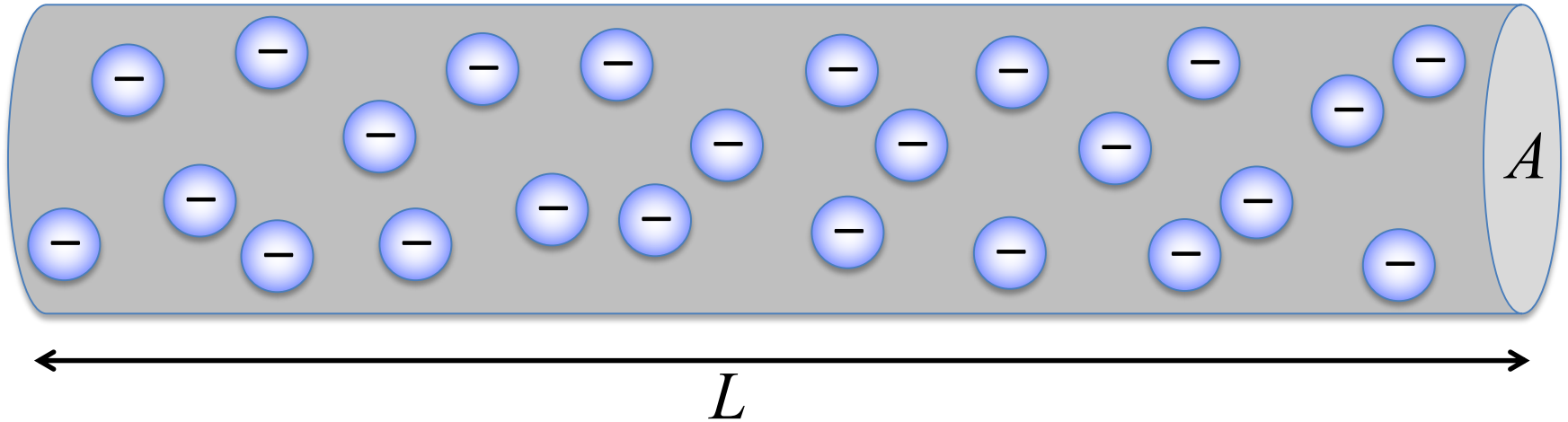


$$i = nAev_d = JA$$

The current density is then seen to be given by the **charge density**  $ne$  and the **drift velocity** (average velocity of the electrons)

$$\vec{J} = ne\vec{v}_d$$

# Current and Current Density

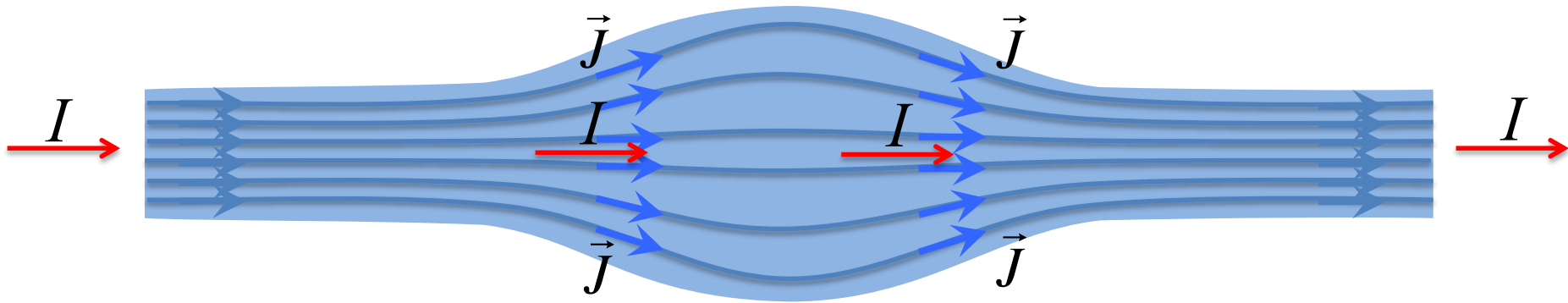

Because it is a vector,  $\vec{J}$  is always in the direction of the “streamlines” of the electrons at any given location in the wire.

The current  $I$ , on the other hand, is a scalar and so it just has a magnitude. The direction we typically associate with it is the average displacement of all the charges in the wire, and so always points along the general direction of the wire.

# TopHat questions

# Resistance

Resistance is a property of conductors that are not ideal:

- Electrons have frequent collisions with atomic nuclei. At constant temperature, this process is in thermal equilibrium.
- When a voltage difference is created across the conductor, this accelerates the electrons, making their collisions more energetic.
- This gets dissipated as heat inside the metal

Tungsten filament:




# Resistors

A resistor is any circuit element that dissipates energy. Light bulbs are the classic example, but there are others:




© 2013 Pearson Education, Inc.

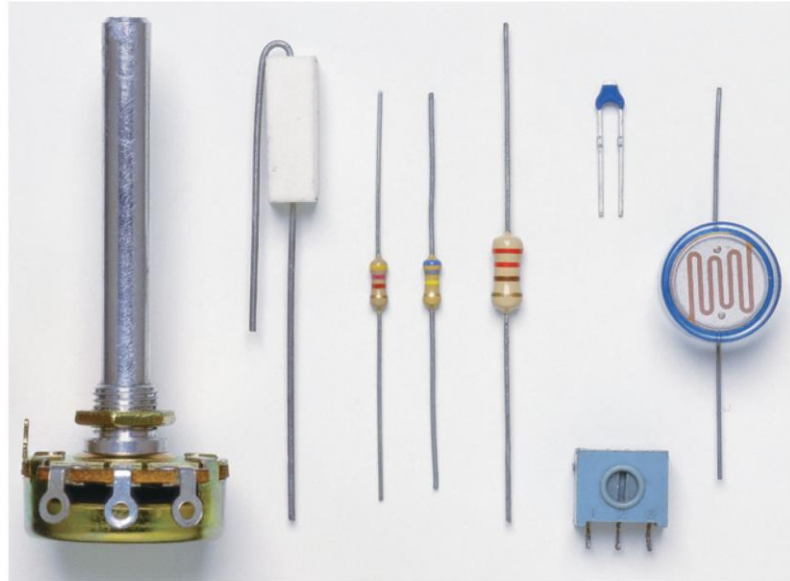

© 2013 Pearson Education, Inc.

How much energy is dissipated by a given resistor is encoded in a property called its resistance  $R$ . The resistance is dependent on the particular material used as well as the geometry.

# How can we quantify this

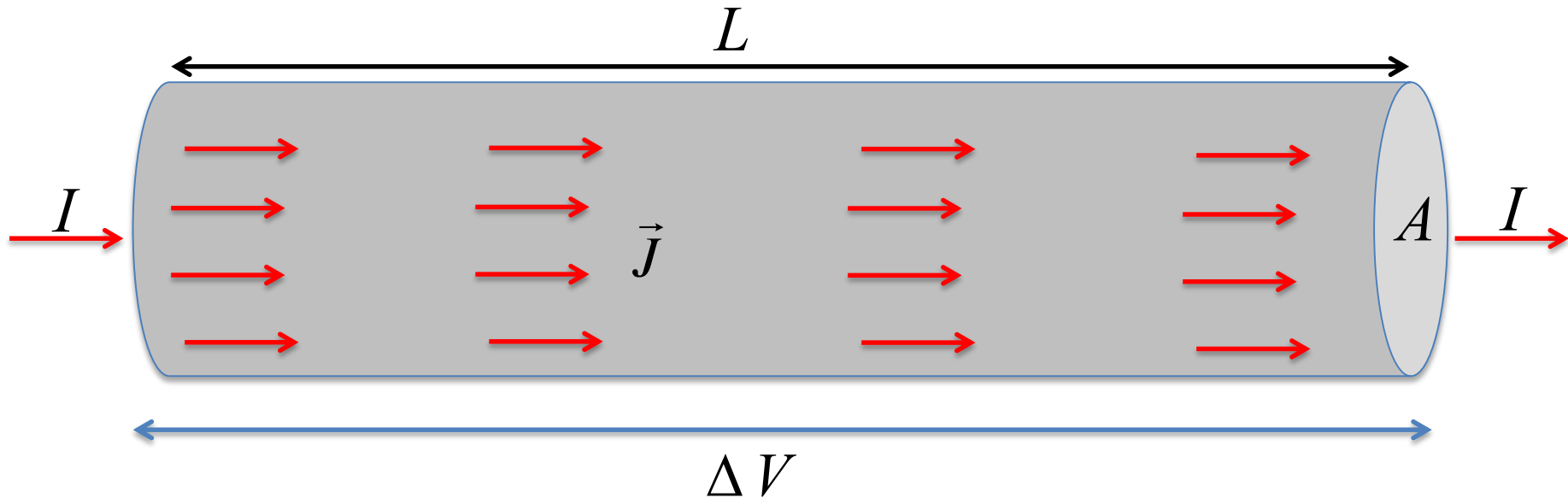

Ohm's Law states that the current density inside the conductor is related to the electric field causing the charges to move via

$$\vec{E} = \rho \vec{J}$$


The resistivity is a physical property of the material that makes up the resistor

$$r = \frac{E}{J} = \frac{\Delta V / L}{I / A}$$

Using the resistivity, we can define a geometric quantity of the resistor:

$$r \frac{L}{A} = \frac{\Delta V}{I}$$

# How can we quantify this

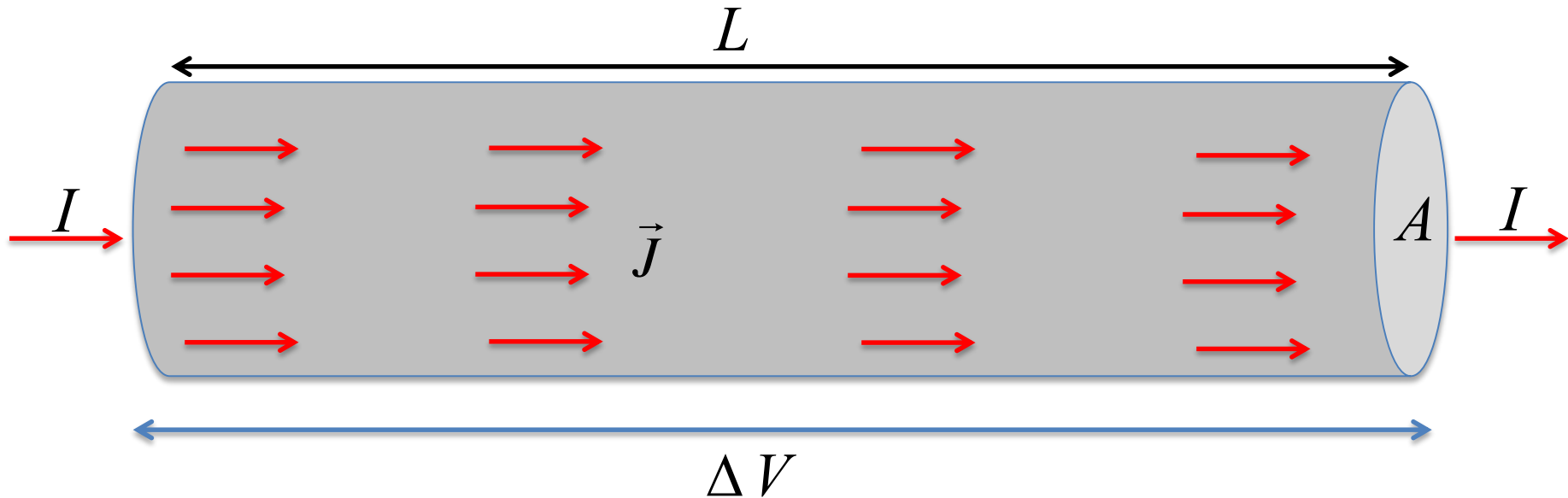

We introduce the resistance, which is dependent on  $\rho$  of the material and on the geometry of the resistor

$$r \frac{L}{A} \circ R$$

$$r \frac{L}{A} = \frac{\Delta V}{I}$$


$$R = \frac{\Delta V}{I}$$

This gives us the familiar form of Ohm's Law:

$$\Delta V = IR$$
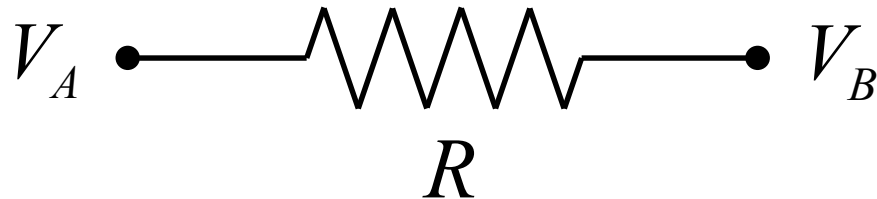
# Ohm's Law

When a voltage difference  $\Delta V$  is applied across a resistor  $R$ , the voltage difference causes electrons to flow through the resistor



This flow of electrons is the electric current  $I$ . These quantities are related by Ohm's Law:

$$\Delta V = IR$$

Current convention: the flow of positive charge (opposite the flow of negative charge)

A diagram illustrating current convention. On the left, a red circle with a '+' sign has a red arrow pointing to the right. On the right, a blue circle with a '-' sign has a blue arrow pointing to the left. Between them is the equation  $(+e)(+\vec{v}) = (-e)(-\vec{v})$ .


Both define a current  $I$  pointing to the right, so it is more convenient to think in terms of + charges moving


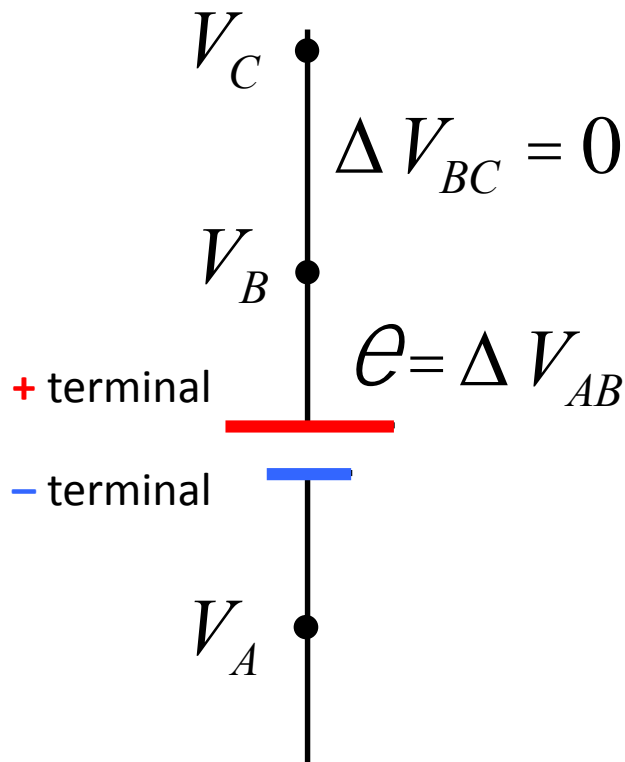
# Ideal wires & batteries

Real wires always have some **resistance** to them, but it is usually **small enough** that we can **ignore** it.

In this class we will usually treat wires as **ideal**, meaning  $\Delta V = 0$  across any wire segment even if there is a current flowing.



A battery is any **source** that supplies a **voltage difference** in an electric circuit. The voltage is either specified by  $V$  or by the symbol  $\mathcal{E}$  which stands for **electromotive force** (EMF)

Real batteries also have a resistance to them and we will see later how to account for this.


# A Basic Circuit

The simplest circuit has an ideal battery, ideal wires, and a single resistor.

## Kirchhoff's Loop Rule:

The sum of the voltage differences around a closed loop in a circuit must be zero.

(conservation of energy)

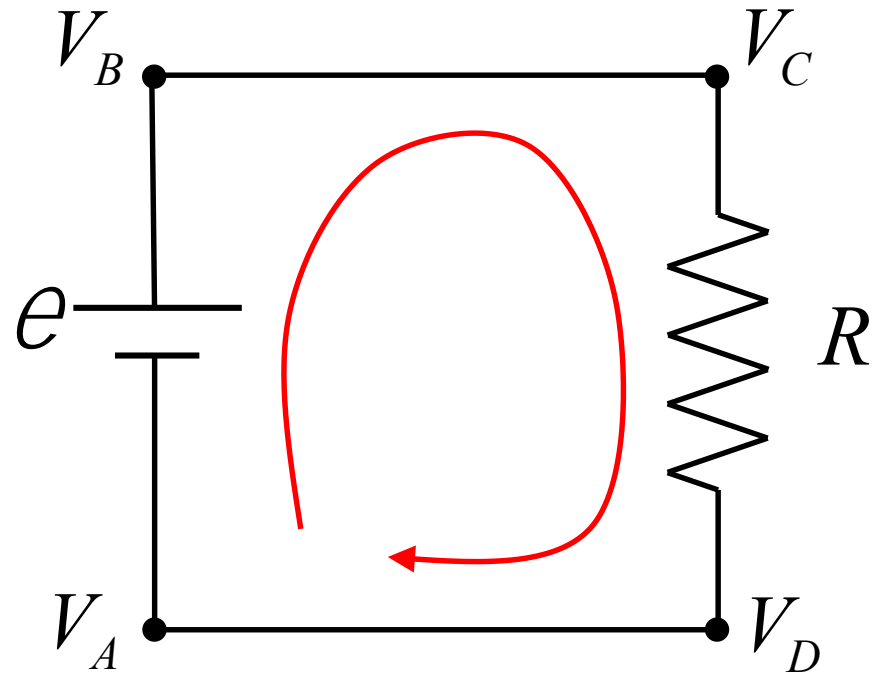


$$\Delta V_{AB} + \Delta V_{BC} + \Delta V_{CD} + \Delta V_{DA} = 0$$

$$(V_B - V_A) + (V_C - V_B) + (V_D - V_C) + (V_A - V_D) = 0$$
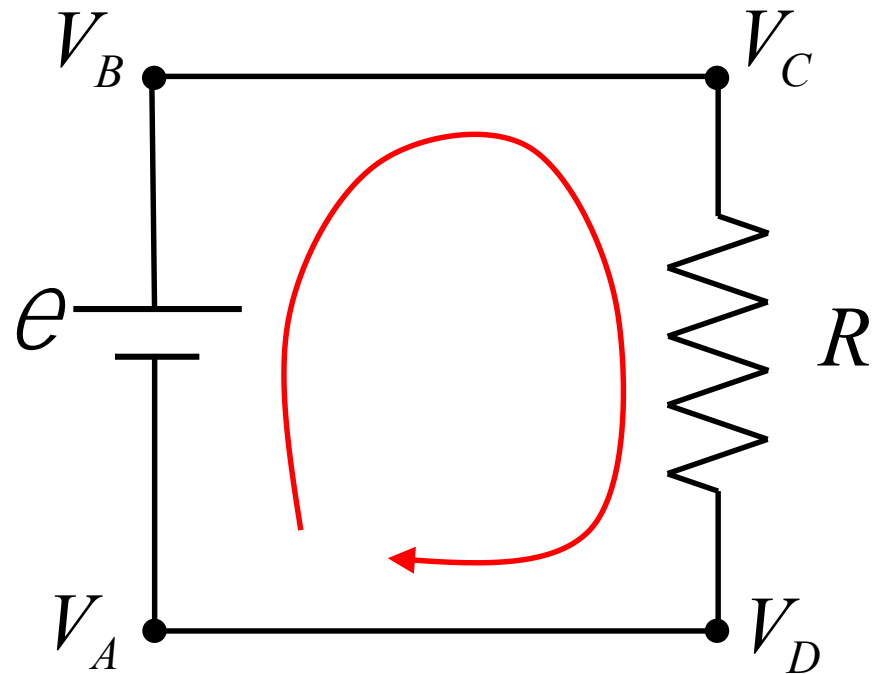
# A Basic Circuit

The voltage across a resistor is **negative** if you are going around the loop in the **direction of the flow of current**.

Current flows **from the negative terminal to the positive terminal**



$$\Delta V_{AB} + \cancel{\Delta V_{BC}} + \Delta V_{CD} + \cancel{\Delta V_{DA}} = 0$$

ideal wires


$$e - IR = 0$$

Ohm's Law
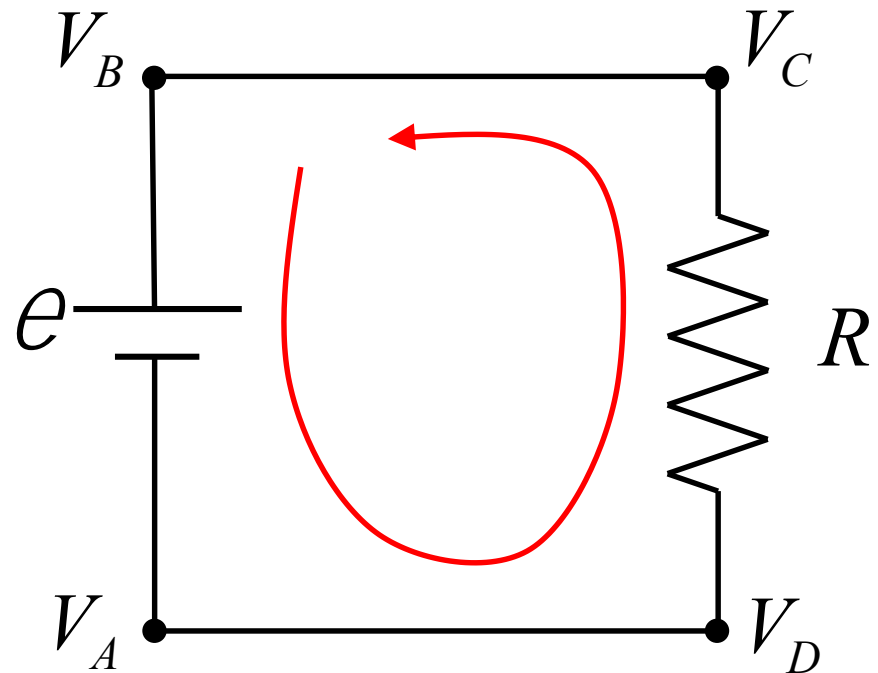
# A Basic Circuit

The voltage across a resistor is **positive** if you are going around the loop in the **opposite direction of the flow of current**.

Voltage across a battery is **negative** going **from positive to negative**




$$\Delta V_{BA} + \cancel{\Delta V_{AD}} + \Delta V_{DC} + \cancel{\Delta V_{CB}} = 0$$

ideal wires


$$-e + IR = 0$$

Same as before


# Kirchhoff's Loop Rule

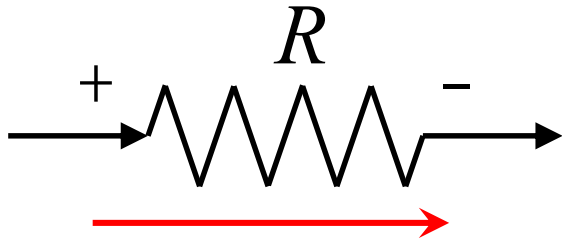


Higher to lower V:  $\Delta V = -IR$

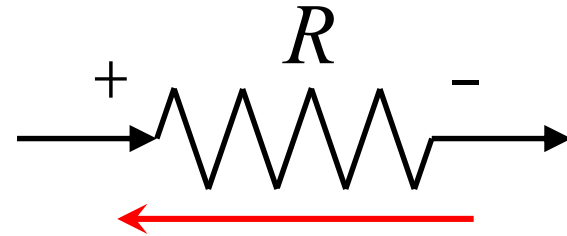


Lower to higher V:  $\Delta V = +IR$

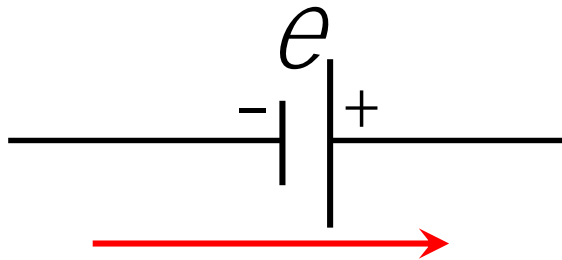


Lower to higher V:  $\Delta V = +e$

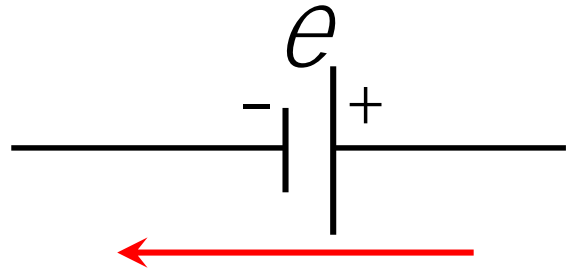

Higher to lower V:  $\Delta V = -e$

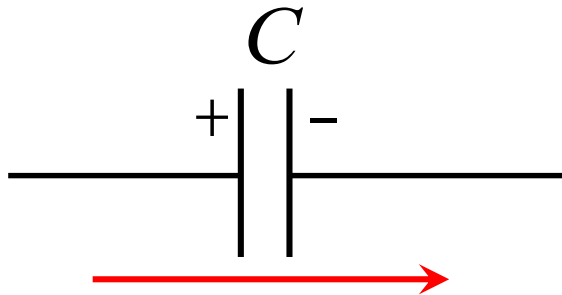

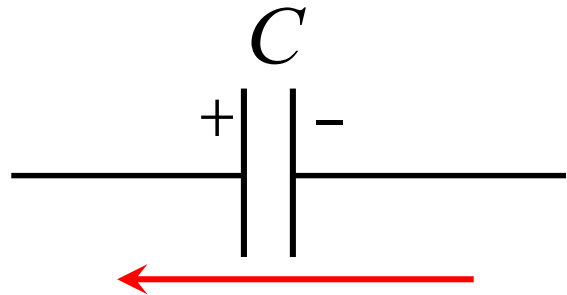
Higher to lower V:  $\Delta V = -\frac{Q}{C}$



Lower to higher V:  $\Delta V = +\frac{Q}{C}$
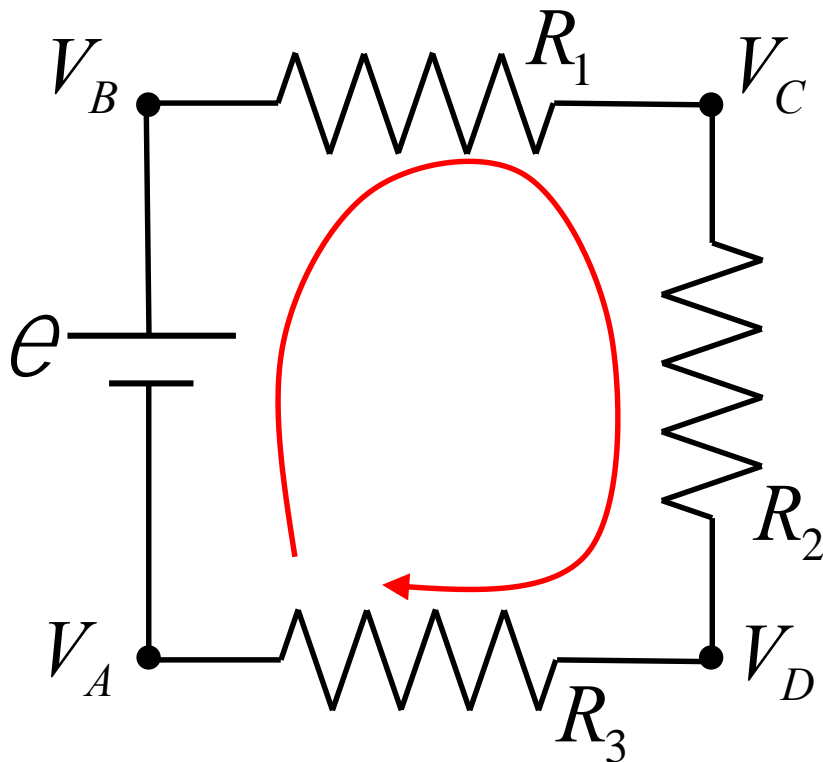
# Resistors in Series

A slightly more complicated circuit has multiple resistors in series



Kirchhoff's Loop Rule:

$$\Delta V_{AB} + \Delta V_{BC} + \Delta V_{CD} + \Delta V_{DA} = 0$$

Current through each  $R$  is same

$$e - IR_1 - IR_2 - IR_3 = 0$$



Rewrite this as

$$e - I(R_1 + R_2 + R_3) = 0$$

Define an equivalent resistance

$$e - IR_{eq} = 0$$

# Resistors in Series

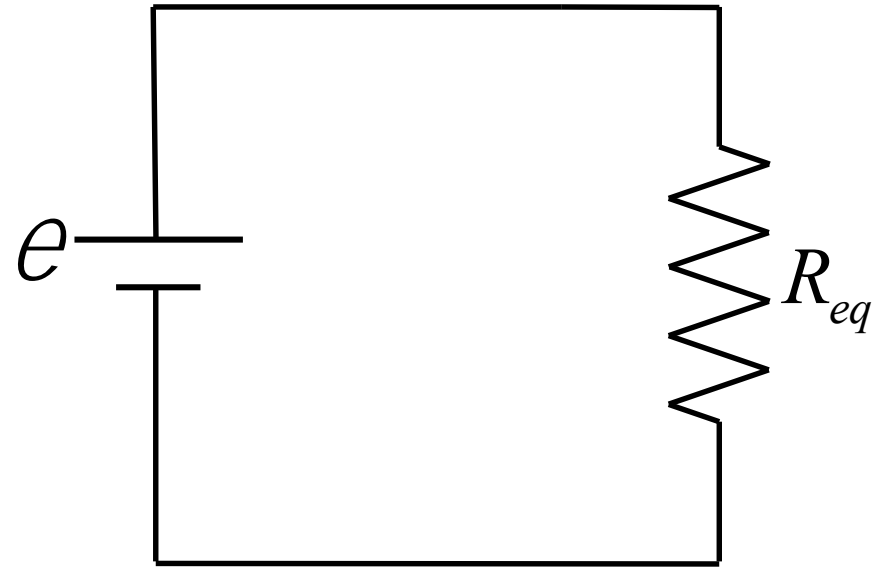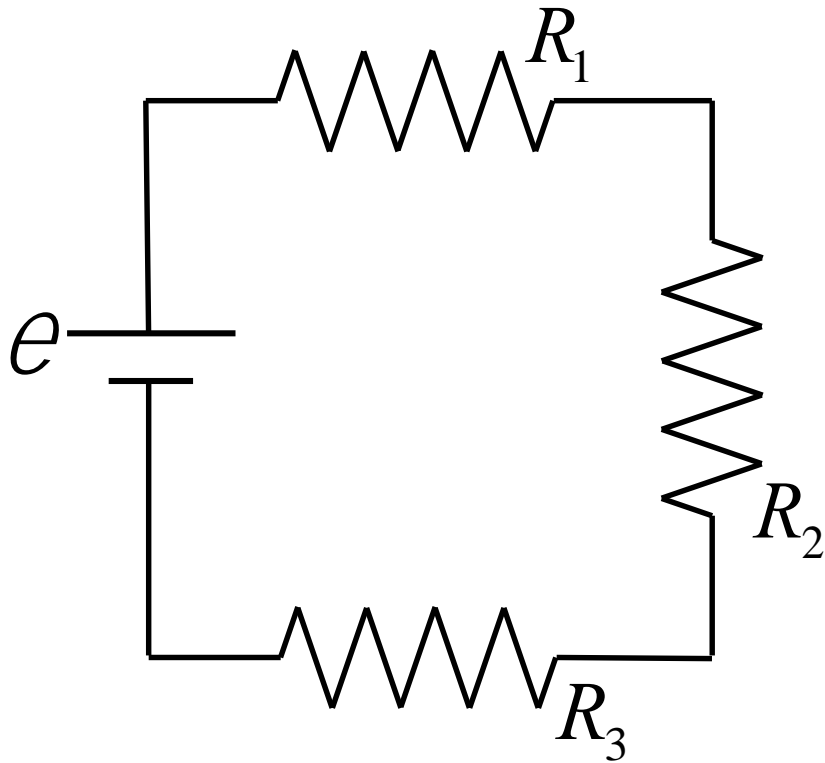


Resistors in series act like a single equivalent resistor:

$$R_{eq} = R_1 + R_2 + R_3$$
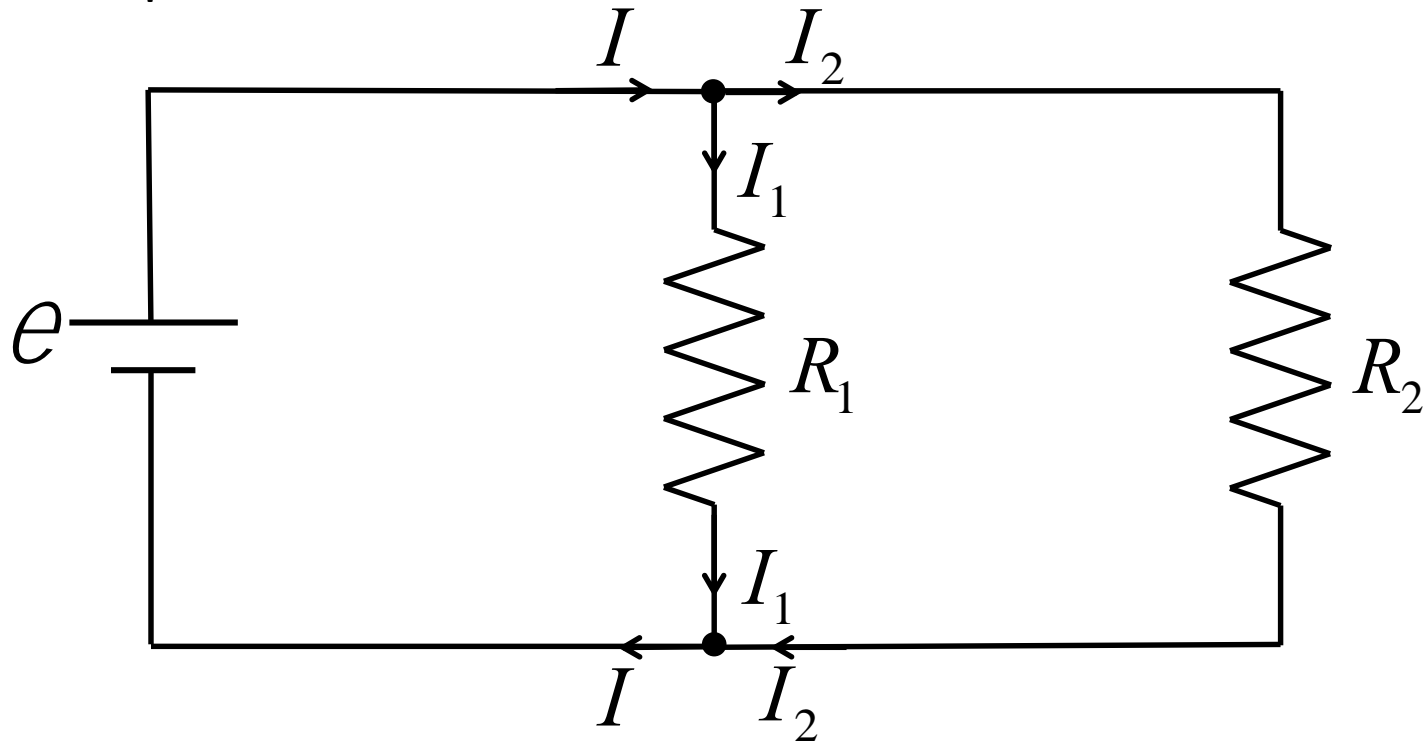
# Resistors in Parallel and Kirchhoff's junction rule

A slightly more complicated circuit has multiple branches with resistors in parallel




Current is the flow of charges. Charge has to be conserved.

Current into junction = current out of junction  $I = I_1 + I_2$



# Resistors in Parallel

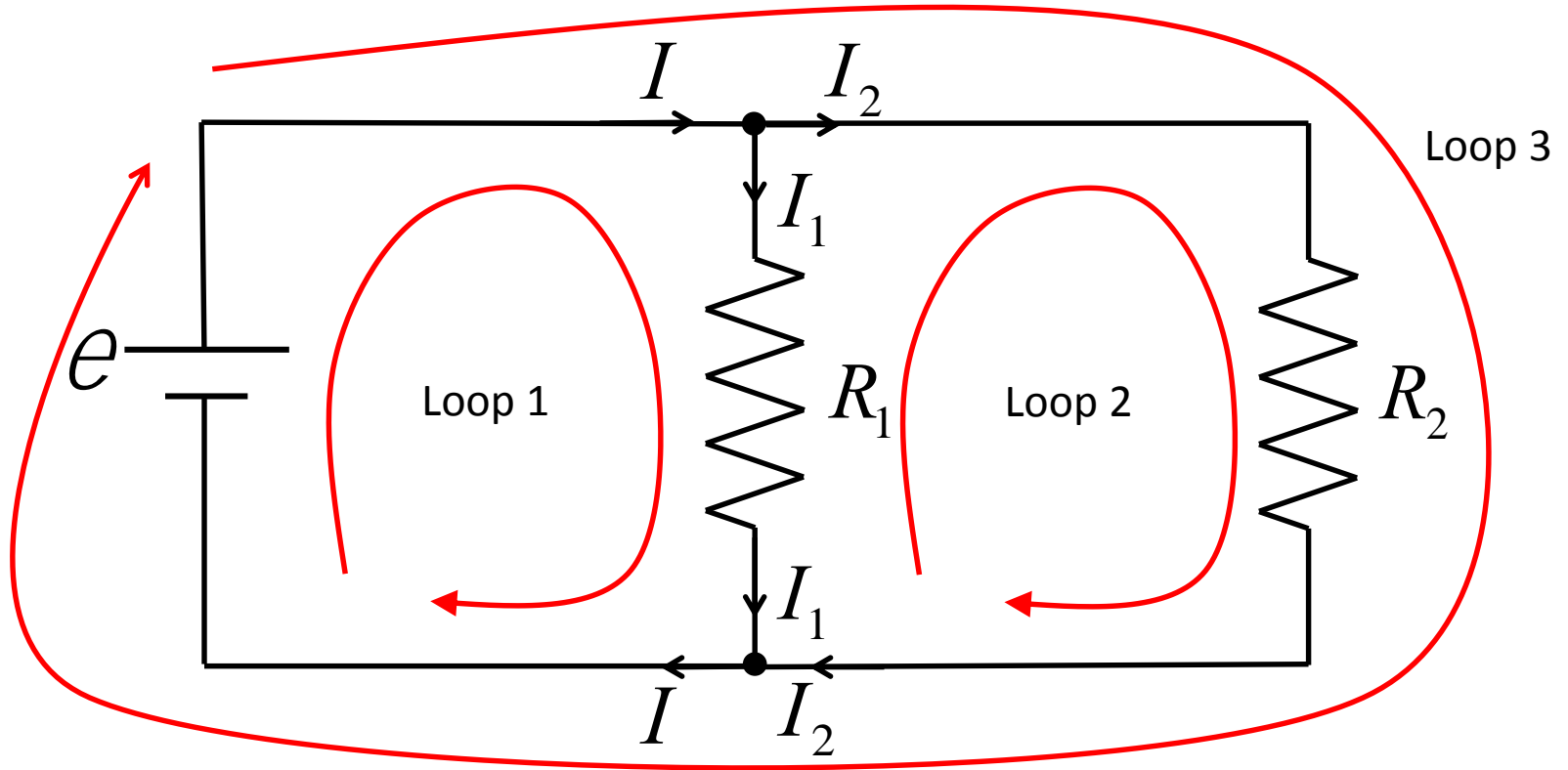


Loop 1:  $e - I_1 R_1 = 0$

Loop 2:  $I_1 R_1 - I_2 R_2 = 0$

Loop 3:  $e - I_2 R_2 = 0$

$$I_1 = \frac{e}{R_1} \quad I_2 = \frac{e}{R_2}$$

# Resistors in Parallel

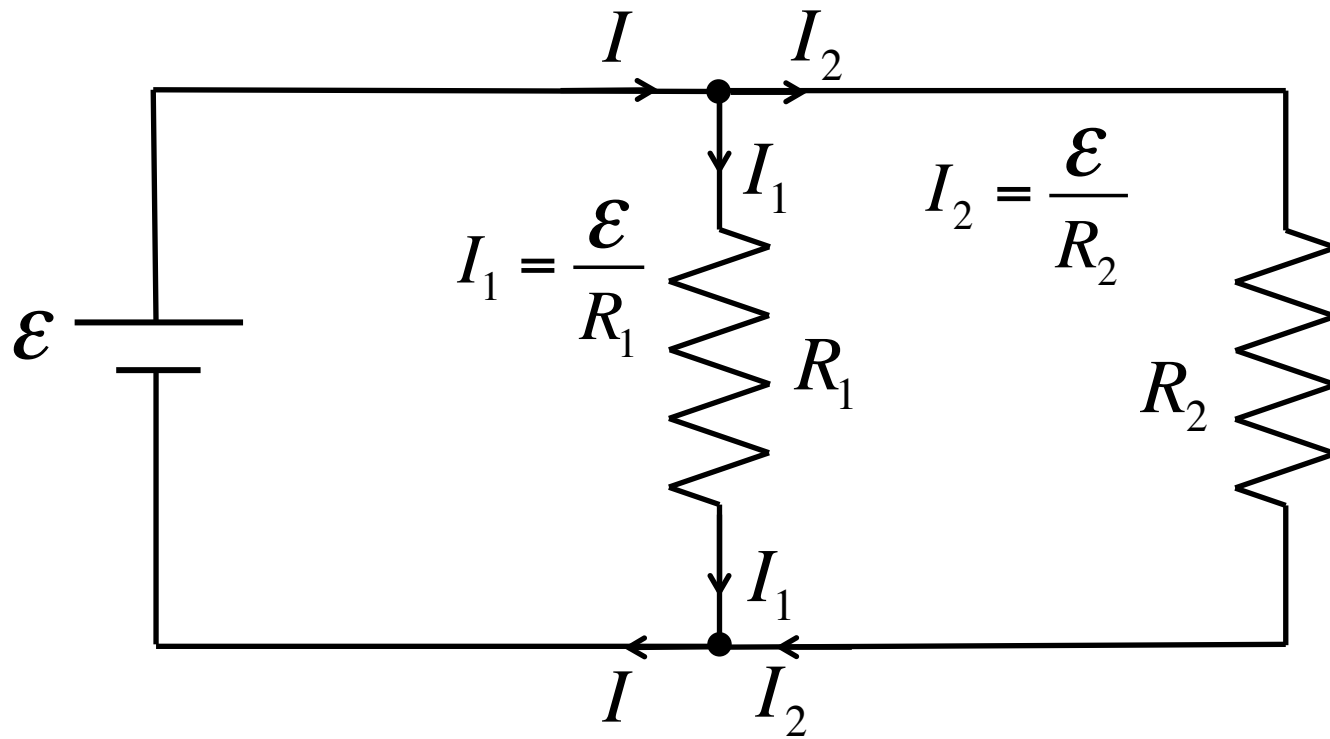

$$I = I_1 + I_2$$

$$I = \frac{\mathcal{E}}{R_1} + \frac{\mathcal{E}}{R_2}$$

$$= \mathcal{E} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= \frac{\mathcal{E}}{R_{eq}}$$

Resistors in parallel: 
$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

# Summary of Resistors

Ohm's Law

$$\Delta V_R = IR$$

Resistors in Series: have the same current running through them

$$R_{eq} = R_1 + R_2 + \dots + R_N$$

Resistors in Parallel: have the same voltage across them

$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)^{-1}$$