

Electricity and Magnetism

- Physics 259 – L02
- Lecture 33



UNIVERSITY OF
CALGARY

Chapters 26 & 27



Last time


- Chapter 25- Capacitance

This time

- Chapters 26 and 27




26-1 Current and Resistance

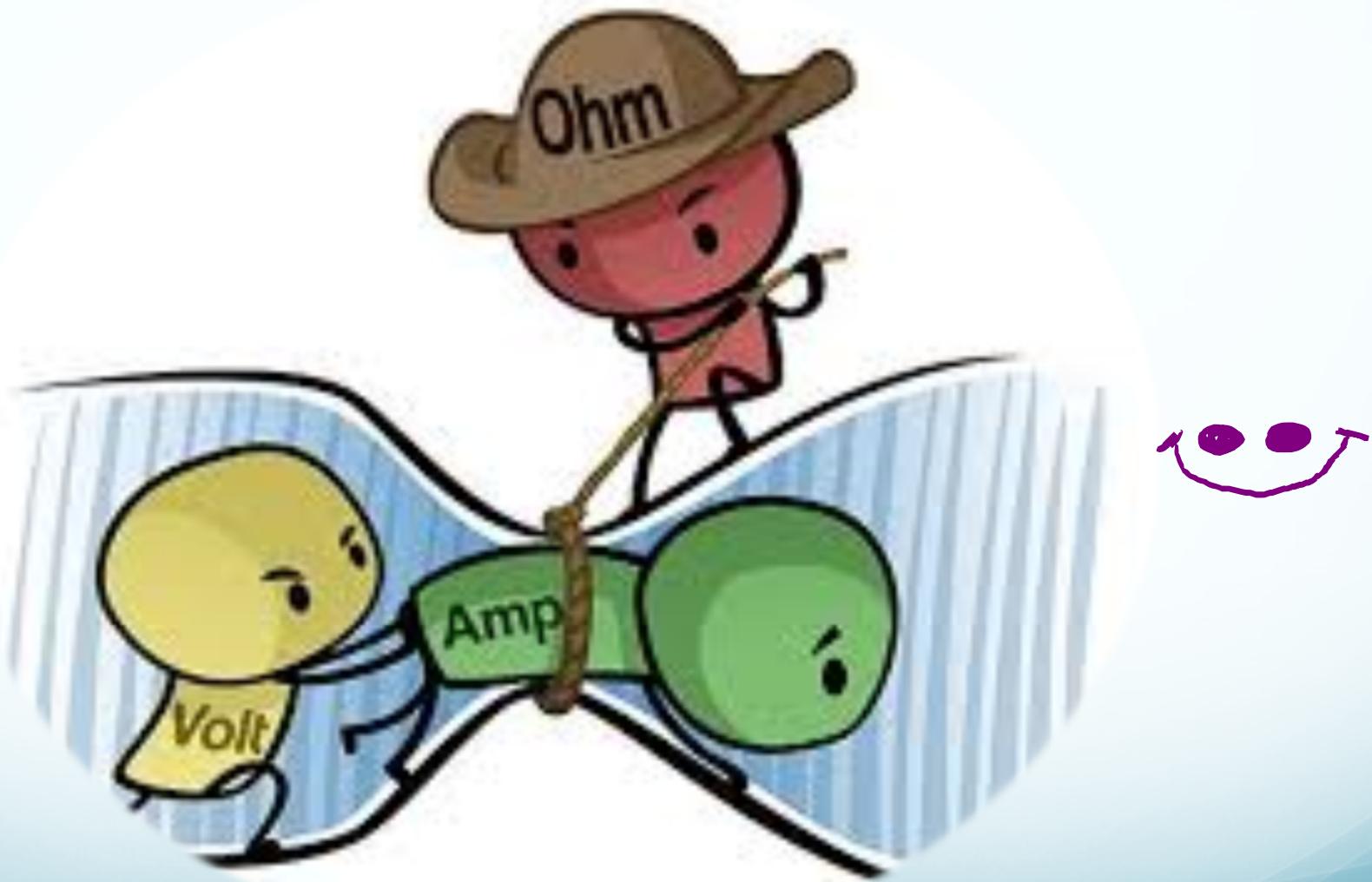


26-1 Electric Current


Where we're going?

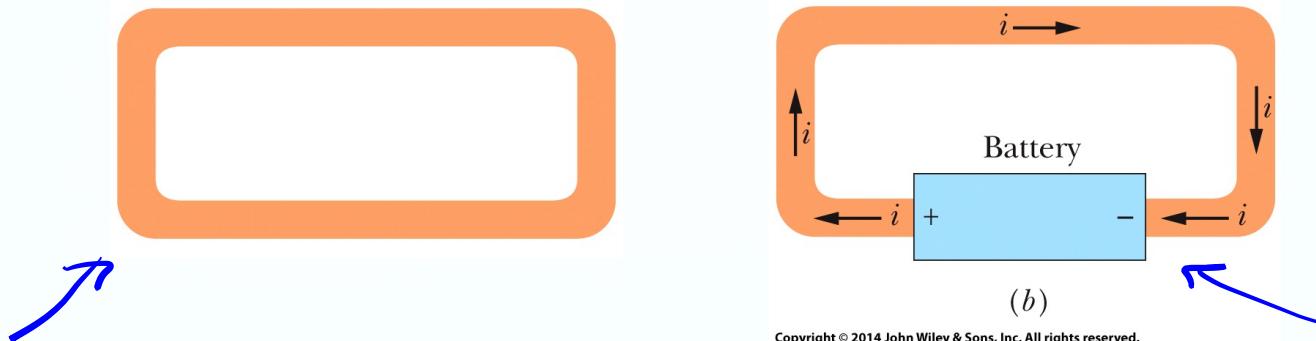

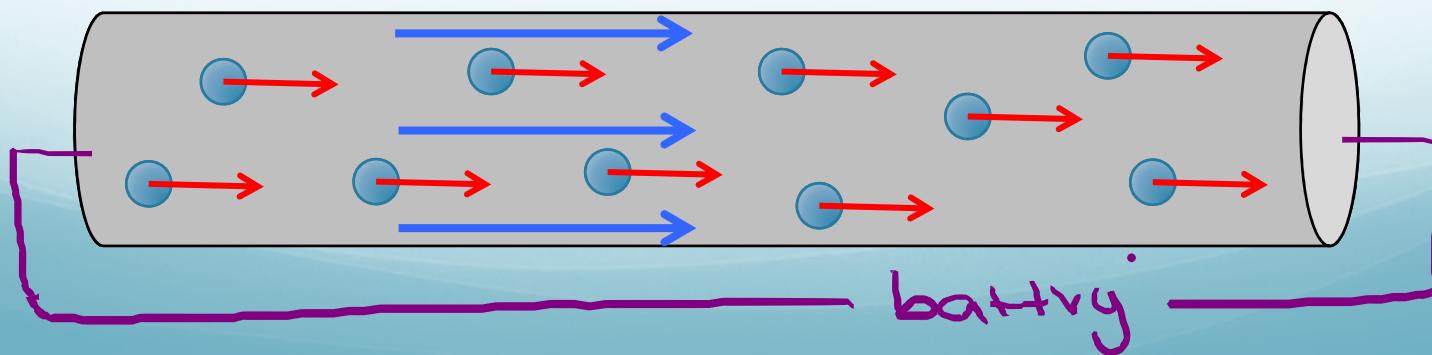Moving charges in electric circuits \rightarrow no electrostatic equilibrium \rightarrow
conductors are allowed to have non-zero electric field inside
(this is what causes the charges to move).



Definition of current

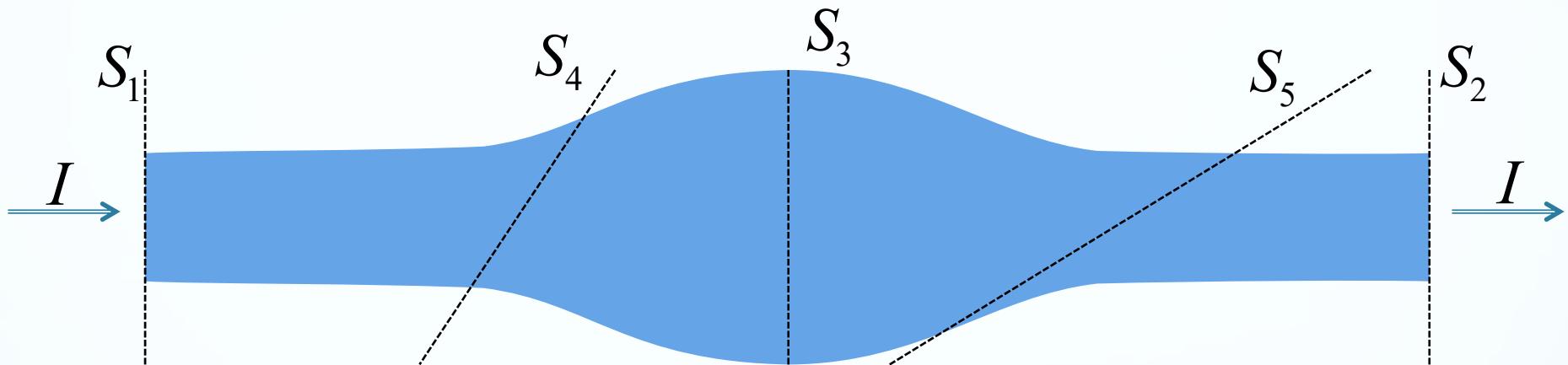

Total amount of charge
flowing past this
surface in a time Δt


$$i = I = \frac{dq}{dt} = \frac{\Delta q}{\Delta t}$$

Total amount of charge
flowing past this surface
in the same time Δt

Total amount of charge flowing through **ANY** surface in a time Δt must
be constant, otherwise charges would begin to accumulate.

Current in a wire is constant.

26-2 Current Density

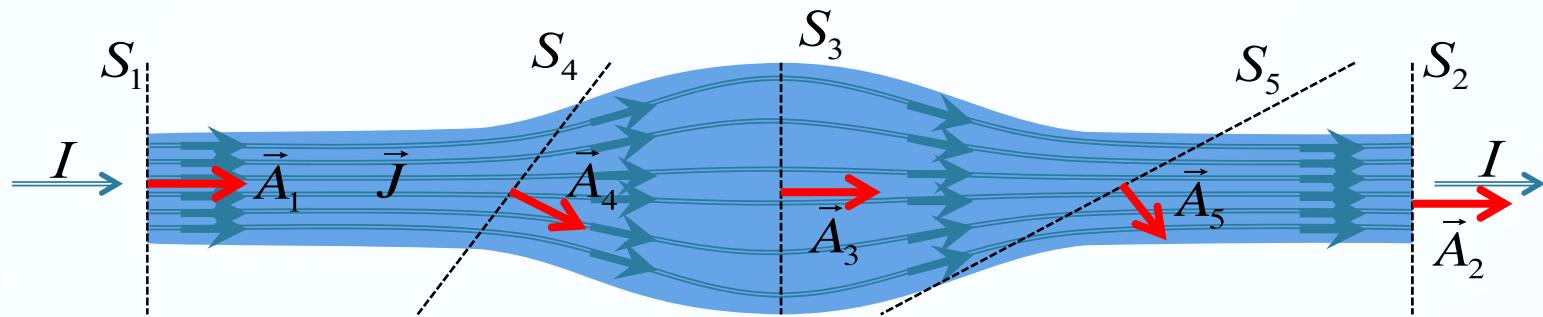


$$\Phi = \oint \vec{E} \cdot d\vec{A}$$

$$I = \oint_S \vec{J} \cdot d\vec{A}$$

$\vec{J} \rightarrow$ current density

$$J = \frac{I}{A}$$

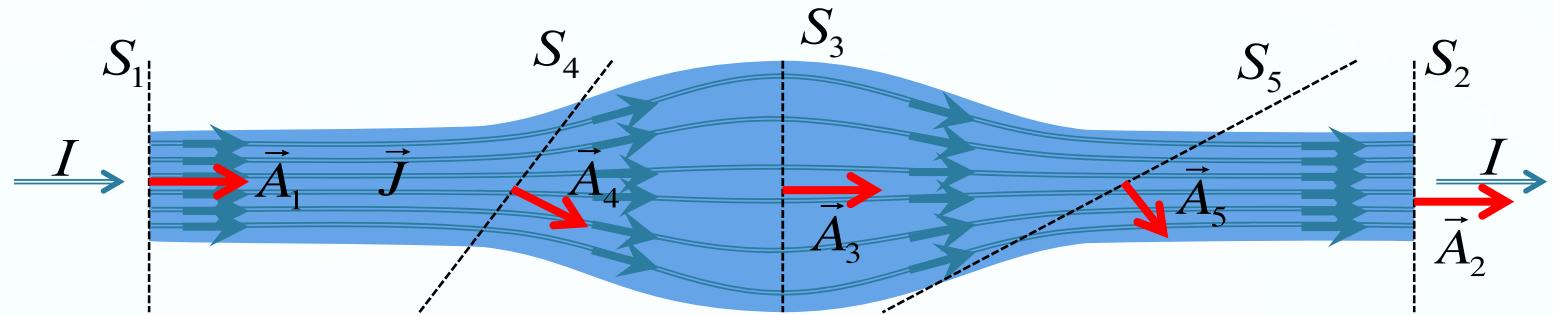The current I is then interpreted as the number of charges passing through a surface in a specified direction.




\vec{J} encodes information about:

- The density of conduction electrons in the conductor
- The net velocity of these conduction electrons

$$J = \frac{I}{A}$$



Current density $J \rightarrow$ same direction as the velocity of the positive moving charges and opposite direction if the moving charges are negative.

Inside a conductor

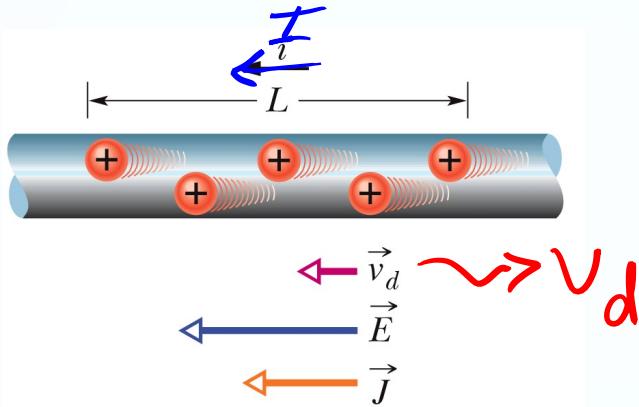


Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

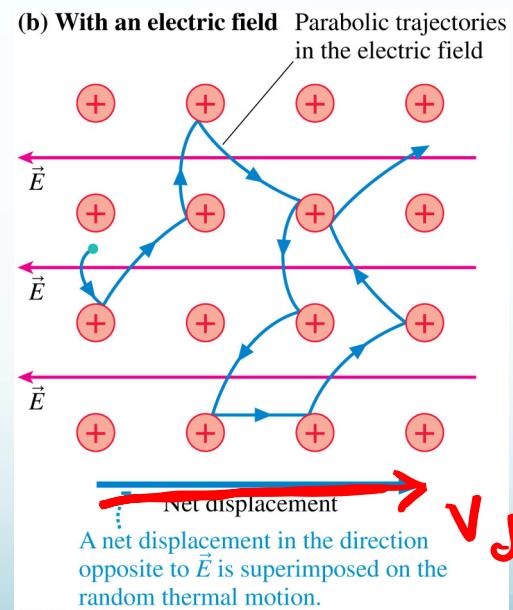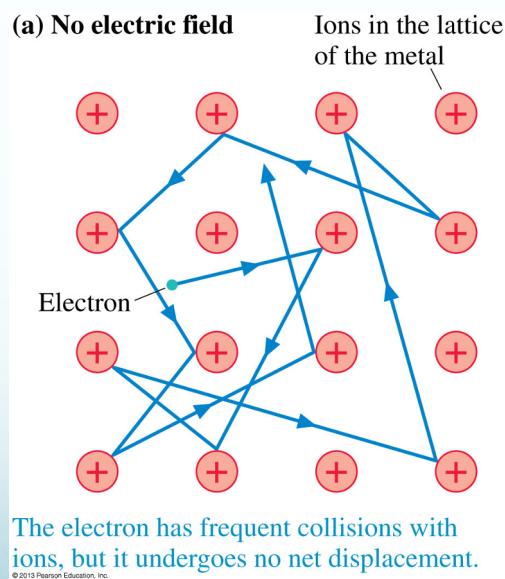Conduction electrons are actually moving to the right but the conventional current i is said to move to the left.



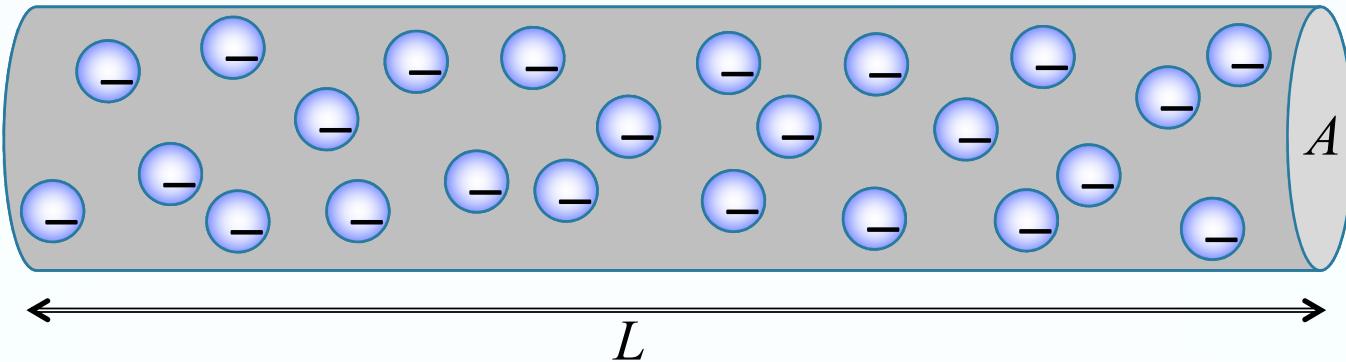Net result: electrons move at an average net “drift speed” v_d



Current $\rightarrow i = \frac{q}{t} = JA$

$$I = \frac{q}{+}$$

✓ volume density of conduction electrons $\rightarrow n_e$ $q = n_e \times V$

✓ Amount of charge contained in a length L of the wire $\rightarrow q = n_e (AL) e$


✓ Time it takes each charge to travel a distance $L \rightarrow t = L/v_d$

$$\hookleftarrow X = V + \rightarrow + = \frac{X}{V}$$

Current $\rightarrow i = \frac{q}{t} = \frac{n_e (AL) e}{L/v_d} = n_e A e v_d$

$$\rightarrow J = \frac{i}{A} \rightarrow$$

$$\vec{J} = n_e e \vec{v}_d$$

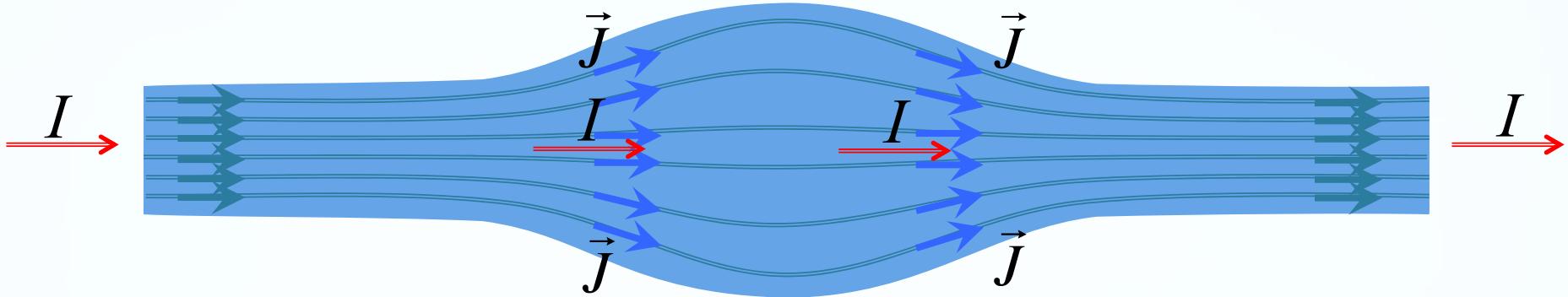

$$J = \frac{I}{A} \rightarrow \text{Const.}$$

\vec{J} is a vector \rightarrow is always in the direction of the “streamlines” of the electrons at any given location in the wire. \rightarrow direction $\Rightarrow +$ charge

I is a scalar \rightarrow just has a magnitude.

Direction \rightarrow is the average displacement of all the charges in the wire, and so always points along the general direction of the wire.

26-3 Resistance and Resistivity

Resistance is a property of conductors that are not ideal:

- Electrons have frequent collisions with atomic nuclei.
- When a voltage difference is created across the conductor, this accelerates the electrons, making their collisions more energetic.
- This gets dissipated as heat inside the metal

Tungsten filament:




Resistors

A resistor is any circuit element that dissipates energy. Light bulbs are the classic example, but there are others:



© 2013 Pearson Education, Inc.

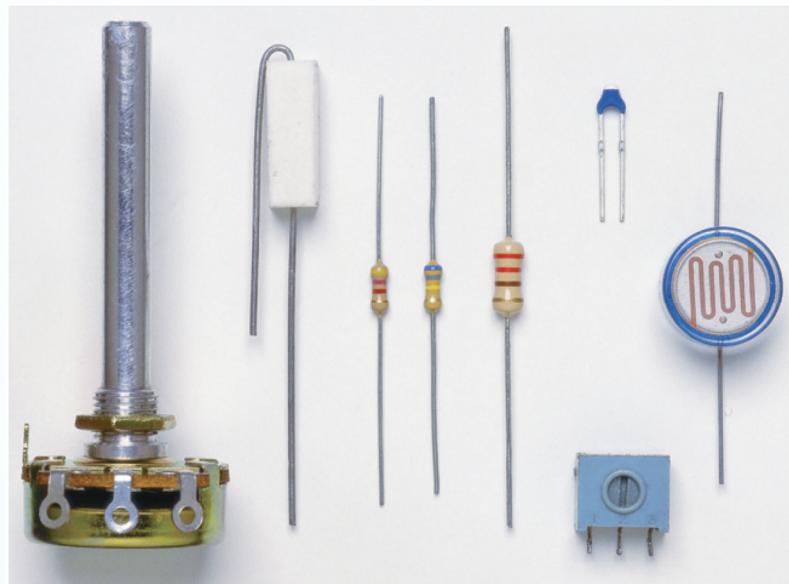



© 2013 Pearson Education, Inc.

How much energy is dissipated by a given resistor is encoded in a property called its resistance R .



The resistance is dependent on the particular material used as well as the geometry.

How can we quantify resistance?

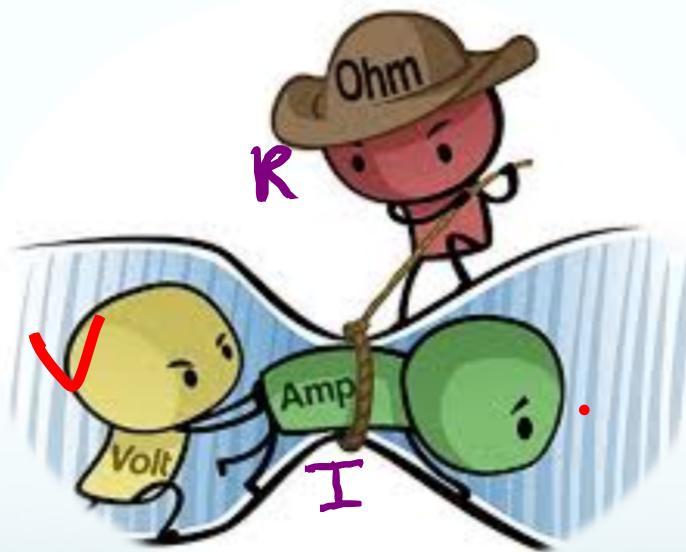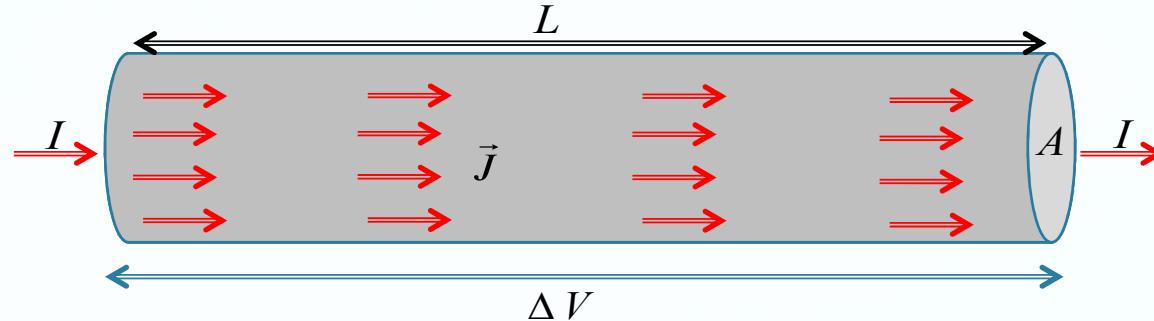

$$C = \frac{q}{V}$$

$$R = \frac{V}{I}$$

Ohm's law

$$\Delta V = IR$$

Proof → Appendix 21-1



Resistance is a property of an object. Resistivity is a property of a material.

Instead of the resistance R of an **object**, we may deal with the **resistivity** ρ of the material:

$$\rightarrow \rho = \frac{E}{J} \quad (\text{definition of } \rho).$$

The reciprocal of resistivity is **conductivity** σ of the material:

$$\sigma = \frac{1}{\rho} \quad (\text{definition of } \sigma).$$


The resistance R of a conducting wire of length L and uniform cross section is

$$R = \frac{V}{I} \quad \&$$

$$R = \rho \frac{L}{A}.$$

Here A is the cross-sectional area.

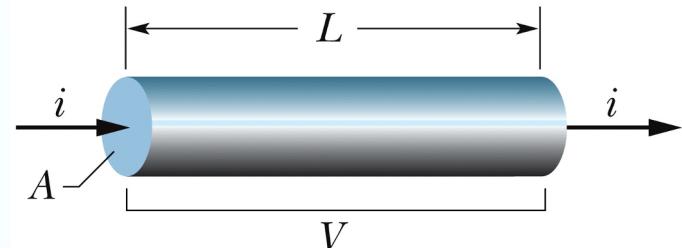Current is driven by a potential difference.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

The resistivity ρ for most materials changes with temperature.

$$\rho - \rho_0 = \rho_0 \alpha(T - T_0).$$


Here T_0 is a reference temperature, ρ_0 is the resistivity at T_0 , and α is the temperature coefficient of resistivity for the material.

27 Circuits



Ohm's Law

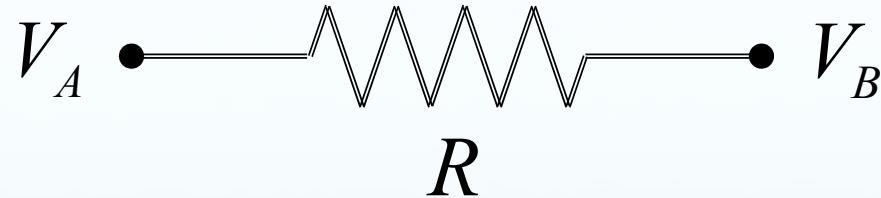When a voltage difference ΔV is applied across a resistor R , the voltage difference causes electrons to flow through the resistor



This flow of electrons is the electric current I . These quantities are related by Ohm's Law:

$$\rightarrow \Delta V = IR$$

Ideal wires & batteries

In this class we will usually treat wires as **ideal**, meaning $\Delta V = 0$ across any wire segment even if there is a current flowing.

$$\Delta V = IR \rightarrow \Delta V = -$$

A battery is any **source** that supplies a **voltage difference** in an electric circuit. The voltage is either specified by V or by the symbol ε which stands for **electromotive force** (EMF) $\varepsilon = IR$ (V)

Real batteries also have a resistance to them and we will see later how to account for this.


Current convention → the flow of positive charge (opposite the flow of negative charge)

A Basic Circuit

The simplest circuit has an ideal battery, ideal wires, and a single resistor


Kirchhoff's Loop Rule:

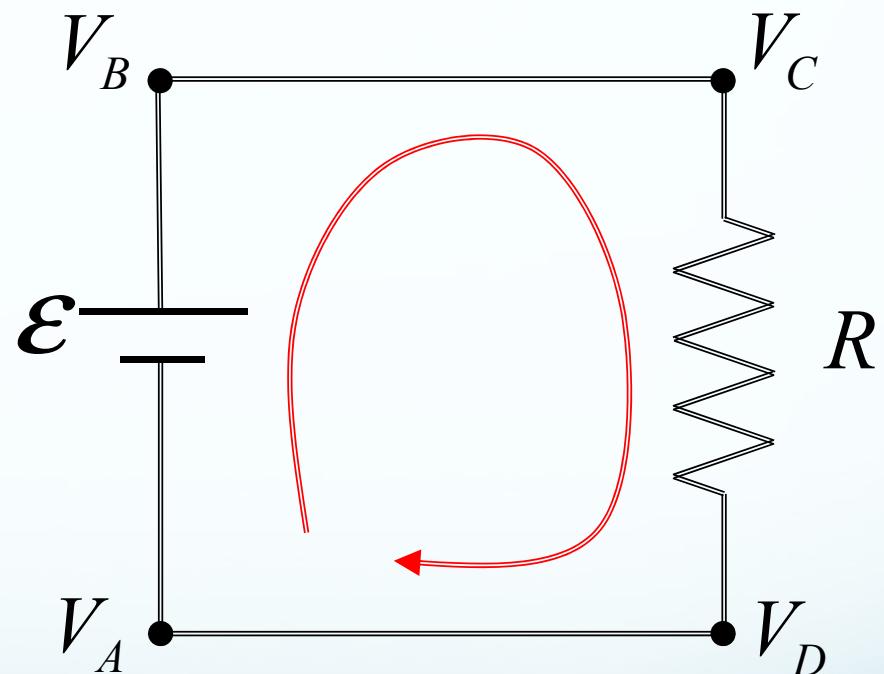The sum of the voltage differences around a closed loop in a circuit must be zero.
(conservation of energy)



$$\Delta V_{AB} + \Delta V_{BC} + \Delta V_{CD} + \Delta V_{DA} = 0$$

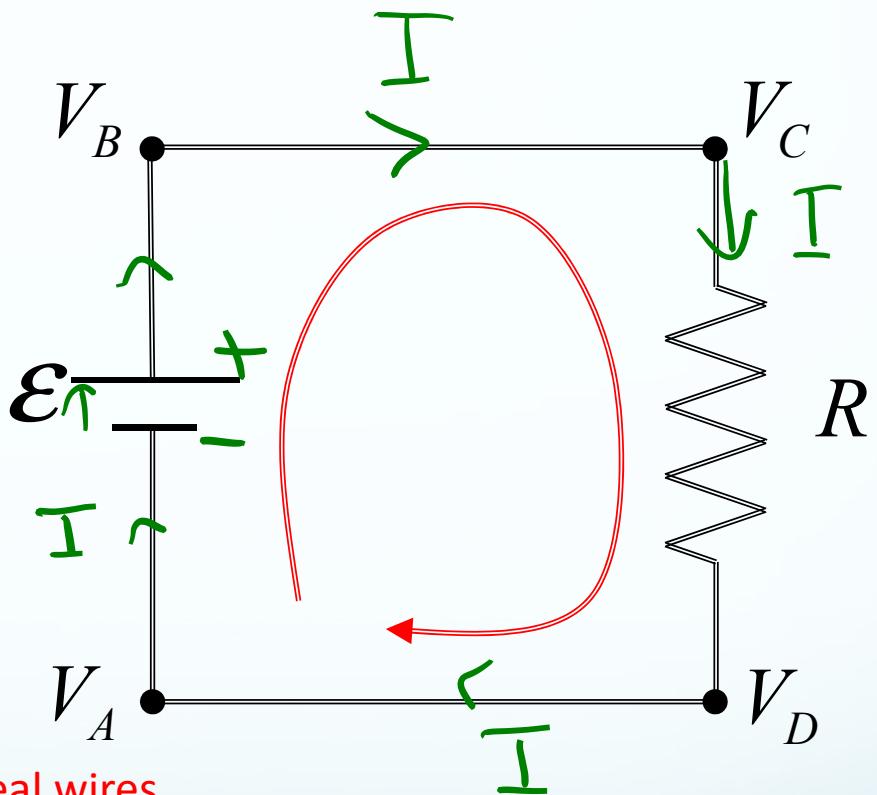The voltage across a resistor is **negative** if you are going around the loop in the **direction of the flow of current**.
 Current flows **from the negative terminal to the positive terminal**




$$\Delta V_{AB} + \cancel{\Delta V_{BC}} + \Delta V_{CD} + \cancel{\Delta V_{DA}} = 0$$

$$\mathcal{E} - IR = 0$$

Ohm's Law

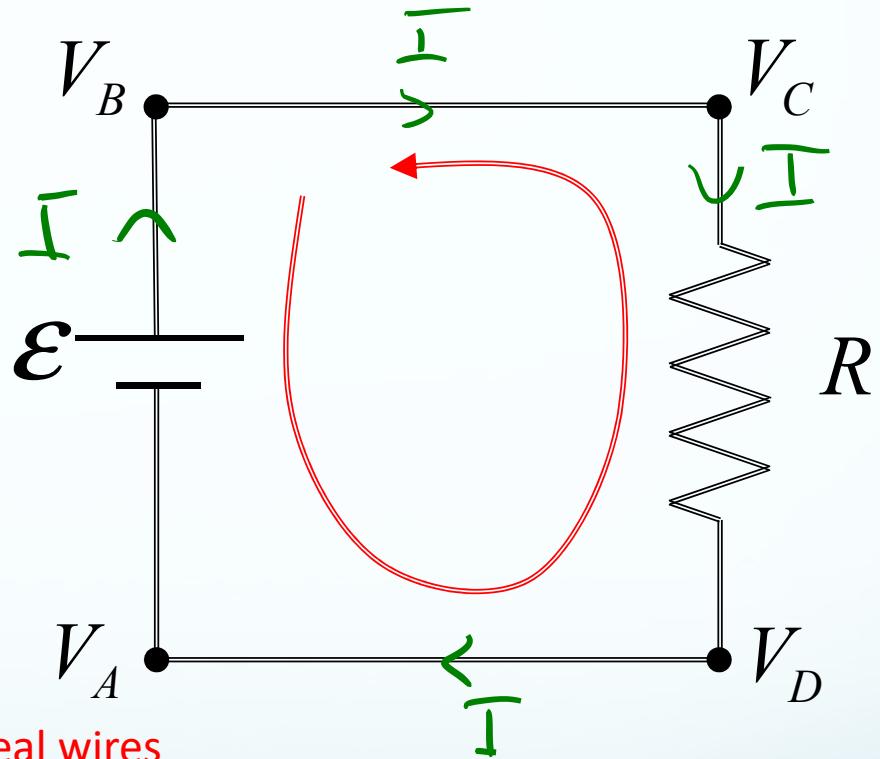The voltage across a resistor is **positive** if you are going around the loop in the **opposite direction of the flow of current**. Voltage across a battery is **negative** going **from positive to negative**




$$\Delta V_{BA} + \cancel{\Delta V_{AD}} + \Delta V_{DC} + \cancel{\Delta V_{CB}} = 0$$


$$-\mathcal{E} + IR = 0$$

Same as before


Kirchhoff's Loop Rule

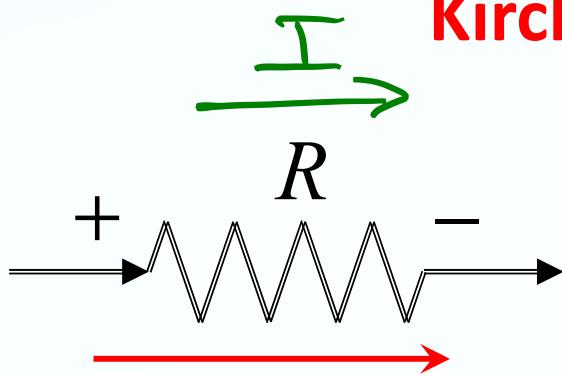


Higher to lower V: $\Delta V = -IR$

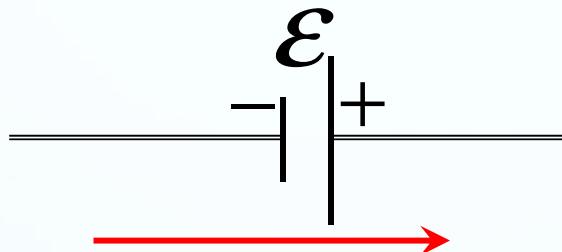

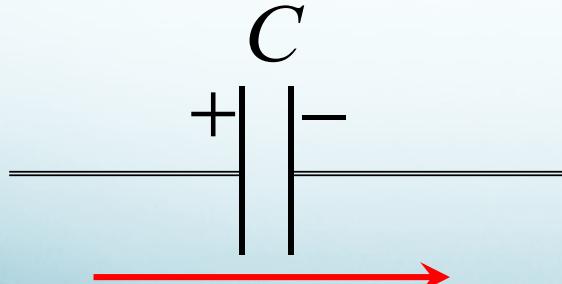
Lower to higher V: $\Delta V = +\mathcal{E}$



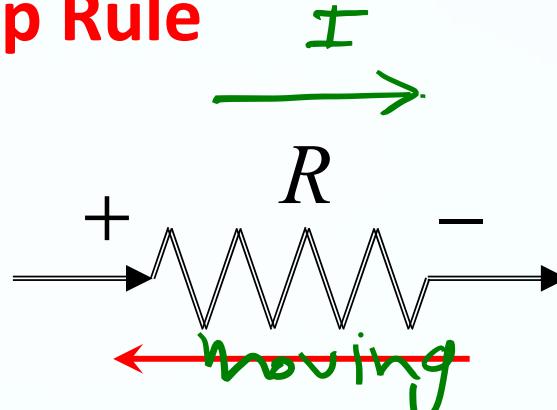
Higher to lower V: $\Delta V = -\frac{Q}{C}$



Lower to higher V: $\Delta V = +IR$

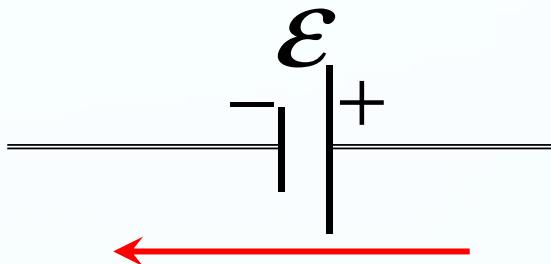

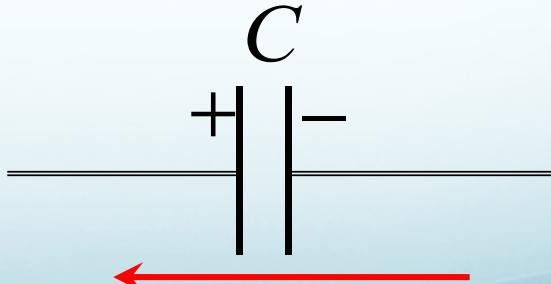Higher to lower V: $\Delta V = -\mathcal{E}$





Lower to higher V: $\Delta V = +\frac{Q}{C}$

Resistors in Series



<https://tinyurl.com/j6cb8sr>

Resistors in Series

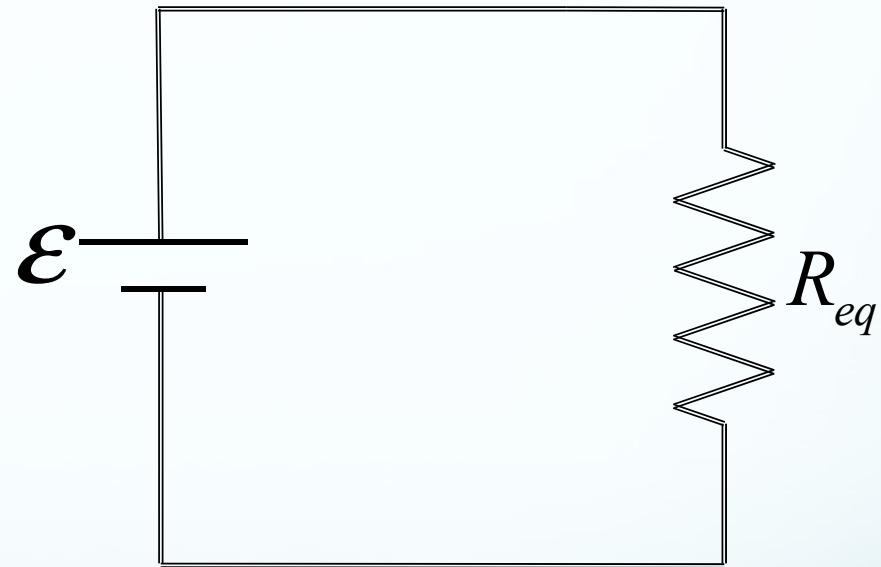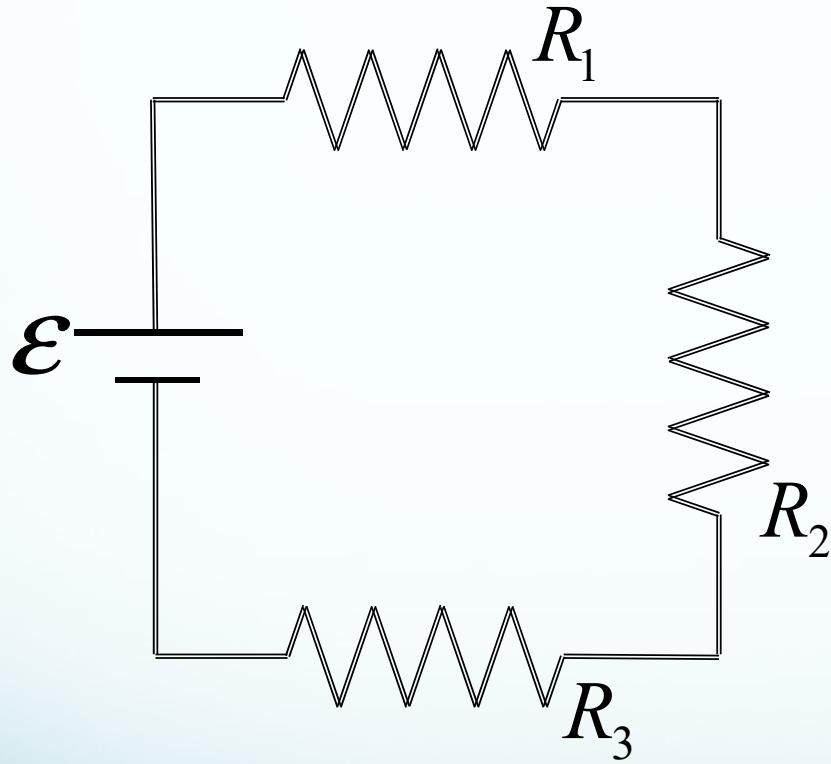

Resistors in series act like a single equivalent resistor:




$$R_{eq} = R_1 + R_2 + R_3$$

Resistors in Parallel



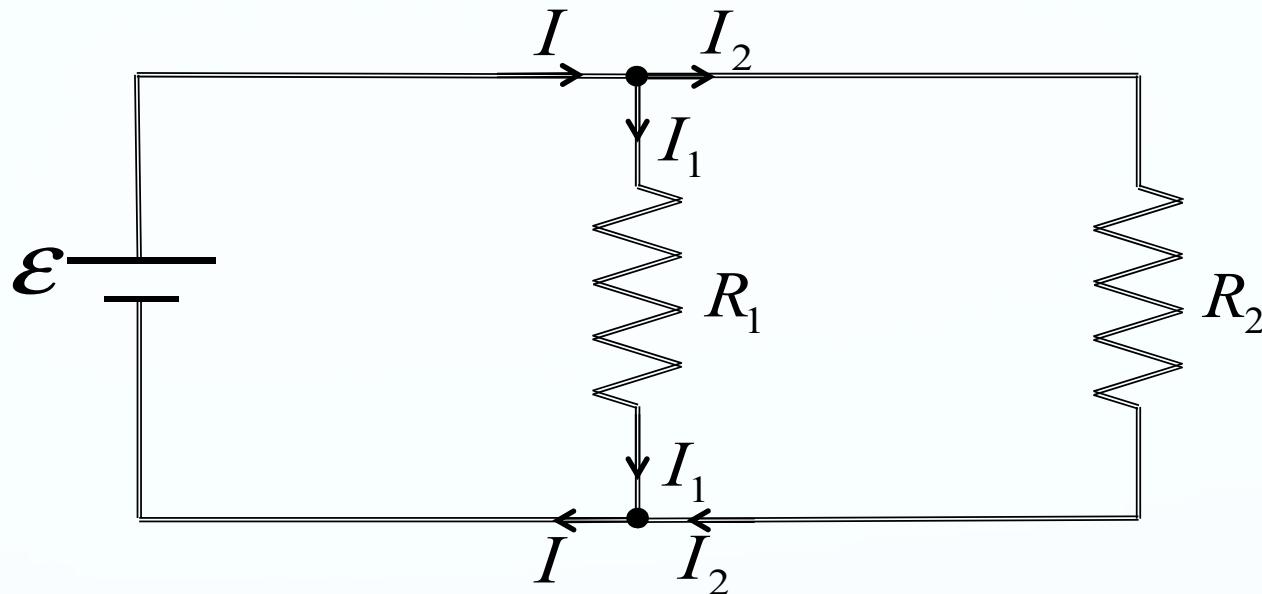Resistors in Parallel and Kirchhoff's junction rule



$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

Current is the flow of charges. Charge has to be conserved.
Current into junction = current out of junction

$$I = I_1 + I_2$$

Summary of Resistors

Ohm's Law

$$\Delta V_R = IR$$

Resistors in Series: have the same current running through them

$$R_{eq} = R_1 + R_2 + \dots + R_N$$

Resistors in Parallel: have the same voltage across them

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)^{-1}$$

This section we talked about:

Chapters 26 and 27

See you on Wednesday

