

# Electricity and Magnetism

- Physics 259 – L02
  - Lecture 36



UNIVERSITY OF  
CALGARY

# Chapter 27



## 27 Circuits



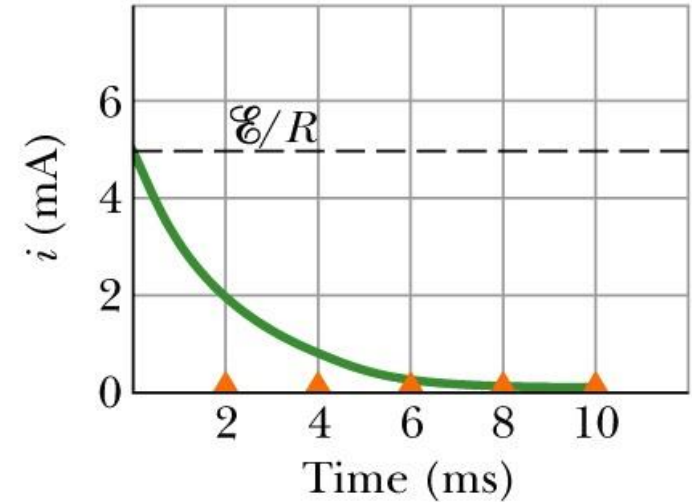
# Case 1: Charging a capacitor




$$i = i_0 e^{-t/RC}$$

$$q = \varepsilon C (1 - e^{-t/RC}) = Q_f (1 - e^{-t/RC})$$



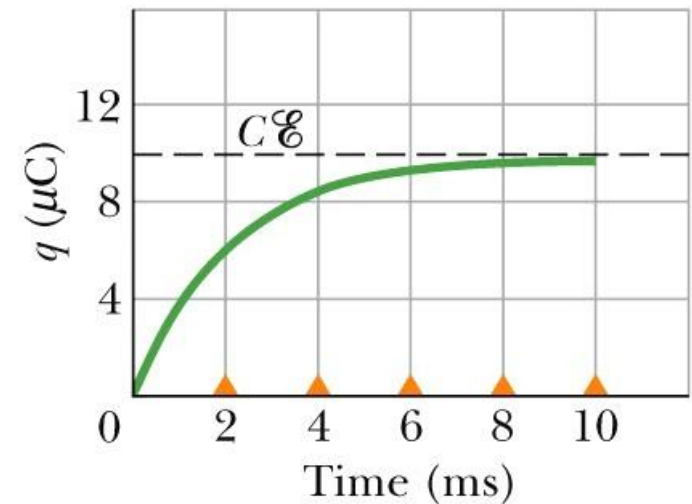
Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

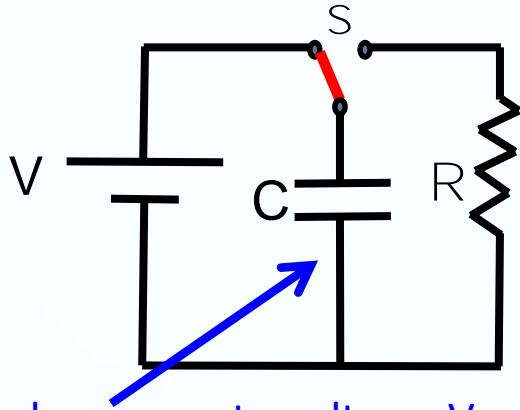
## Case 2: Discharging a capacitor

Switch is connected to the left for a long time until  $t=0^-$



Capacitor charges up to voltage  $V$

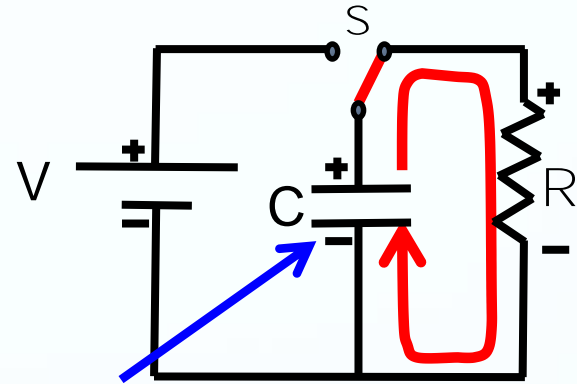Switch is suddenly flipped to the right at  $t=0^+$




Capacitor discharges

$$q(t) = q_0 e^{-t/RC}$$

$$i(t) = i_0 e^{-t/RC}$$



$$q_0 = CV$$

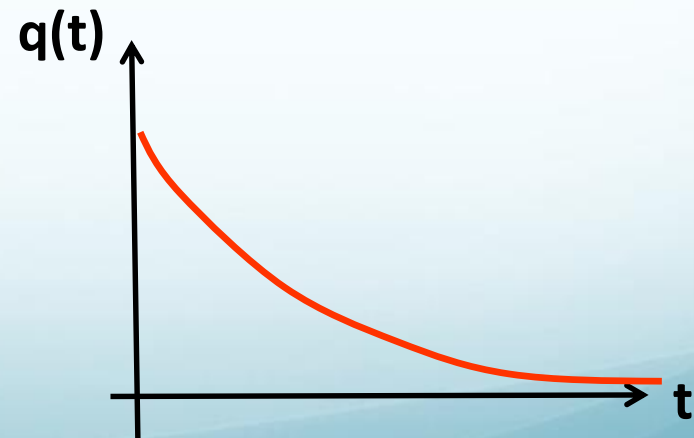

# Charging/Discharging Capacitors



Charging:  $q(t) = Q_f \left( 1 - e^{-\frac{t}{RC}} \right)$

$$i(t) = i_0 e^{-\frac{t}{RC}}$$

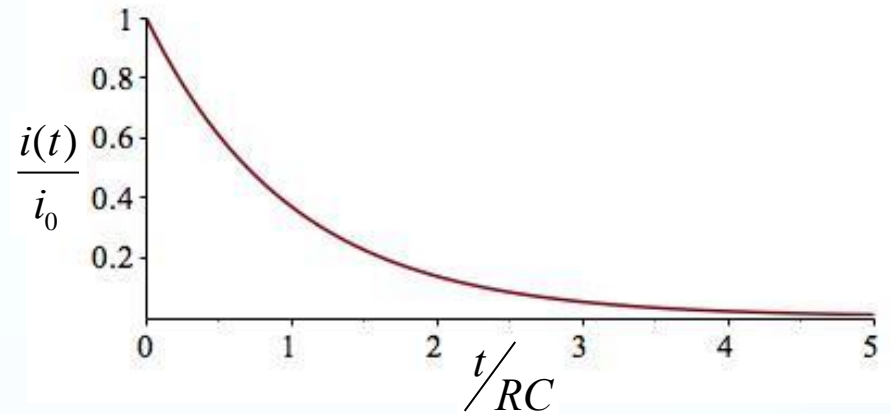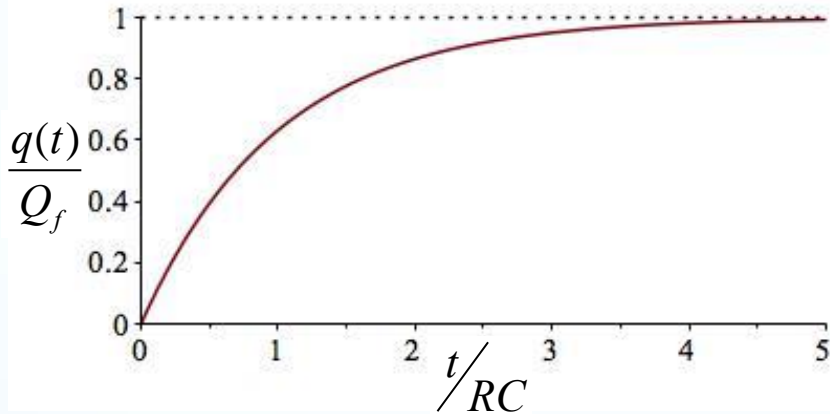

Discharging:  $q(t) = Q_0 e^{-\frac{t}{RC}}$

$$i(t) = i_0 e^{-\frac{t}{RC}}$$

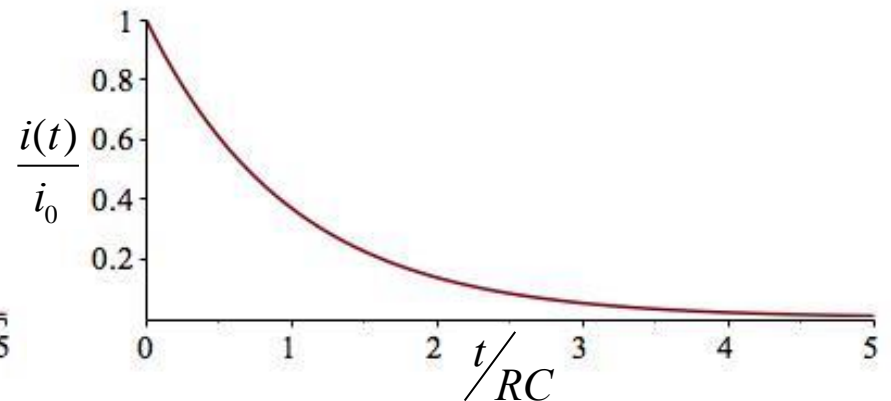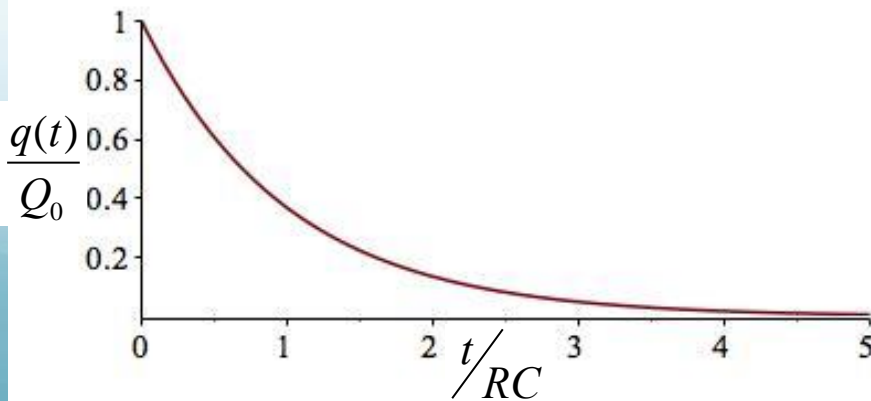



# The RC time constant

The constant RC pops up in the exponential factor for both charging and discharging capacitors. What does it represent?

The units of RC is seconds:  $[RC] = \frac{V}{A} \frac{C}{V} = \frac{C}{C/s} = s$

We call RC the “**RC time constant**” and it tells us how quickly a capacitor can charge or discharge.

$$RC \propto t$$

After a time  $\tau$ , the charge on a discharging capacitor is reduced by a factor of  $1/e$ . After a time  $N\tau$ , it is reduced by a factor of  $1/e^N$

$$q(t) = Q_0 e^{-\frac{t}{\tau}}$$




## Top Hat Question

An RC circuit is shown below. Initially the switch is open and the capacitor is fully charged. At time  $t = 0$ , the switch is closed.

How much charge is left on the capacitor plates after  $t = 10 \text{ ms}$ ?

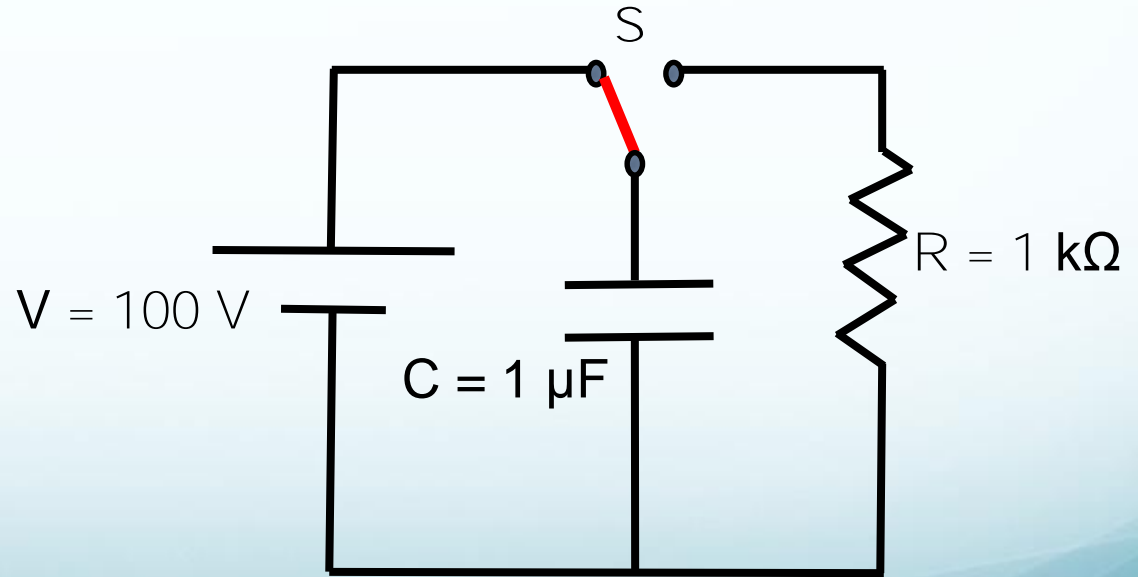- A.  $0.67 \text{ nC}$
- B.  $14 \text{ } \mu\text{C}$
- C.  $37 \text{ } \mu\text{C}$
- D.  $4.5 \text{ nC}$




# Top Hat Question

An RC circuit is shown below. Initially the switch is open and the capacitor is fully charged. At time  $t = 0$ , the switch is closed.


How much charge is left on the capacitor plates after  $t = 10 \text{ ms}$ ?

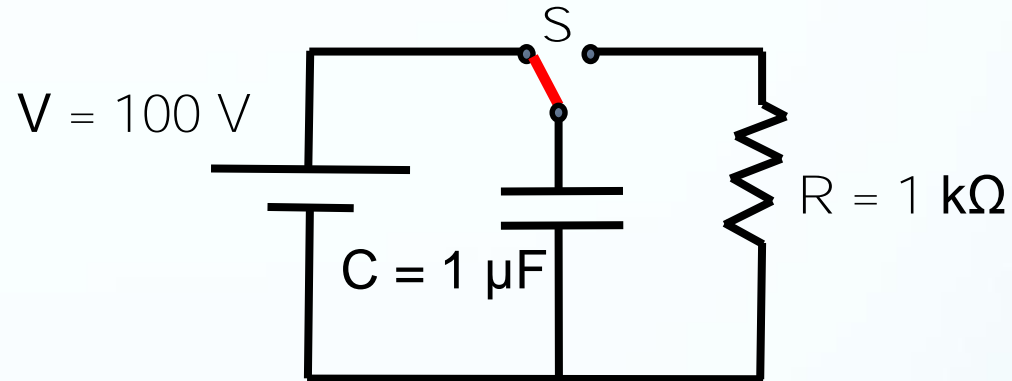- A.  $0.67 \text{ nC}$
- B.  $14 \text{ } \mu\text{C}$
- C.  $37 \text{ } \mu\text{C}$
- D.  $4.5 \text{ nC}$


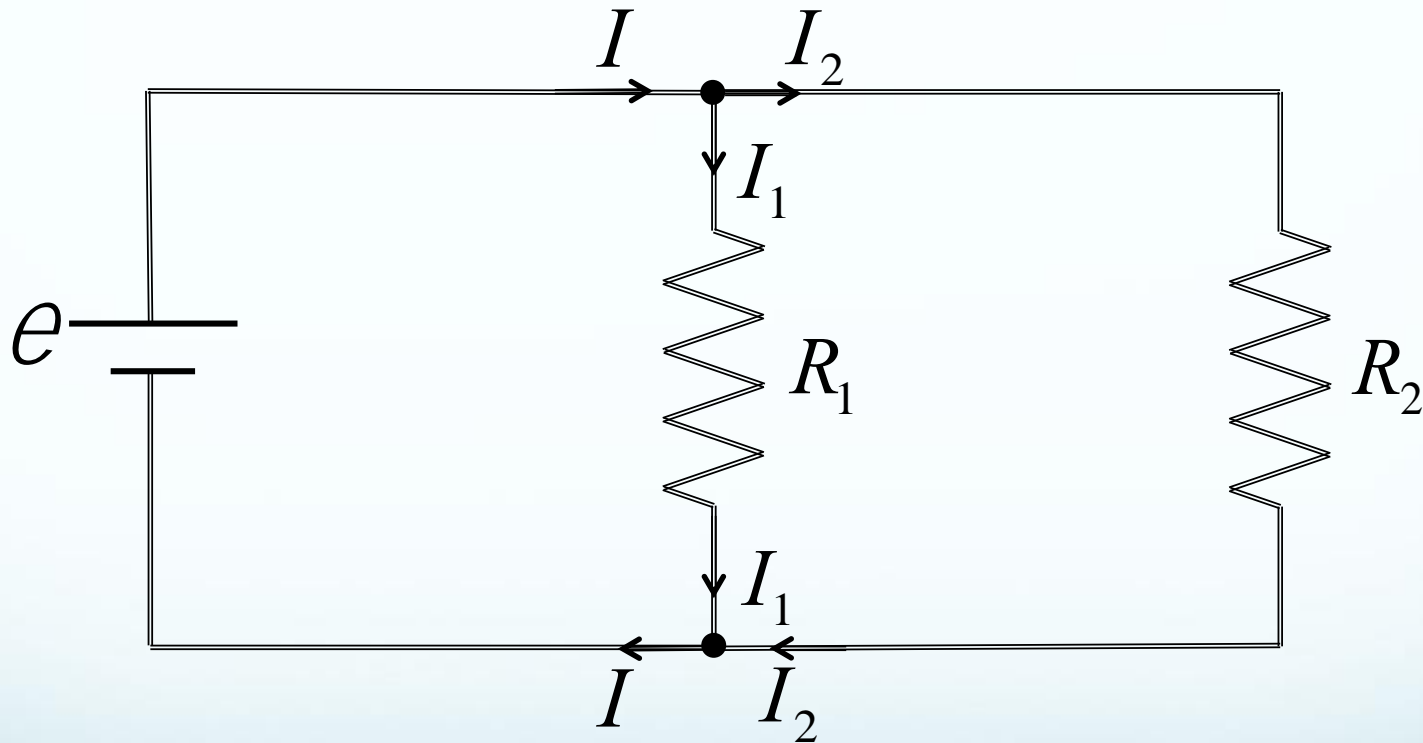
# Kirchhoff's junction rule

A slightly more complicated circuit has multiple branches with resistors in parallel



Current is the flow of charges. Charge has to be conserved.

**Current into junction = current out of junction**

$$I = I_1 + I_2$$

This section we talked about:

## Chapter 27

*See you on Monday*

