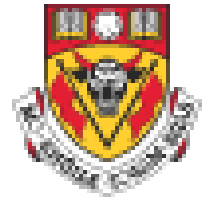


Electricity and Magnetism

- Physics 259 – L02
 - Lecture 36



UNIVERSITY OF
CALGARY


Chapter 27




27 Circuits



Case 1: Charging a capacitor

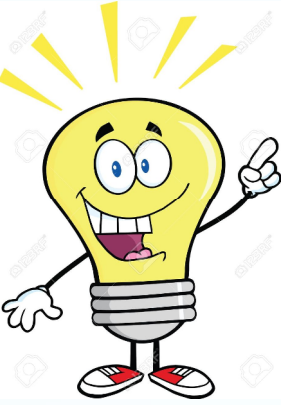


$$i = i_0 e^{-t/RC}$$

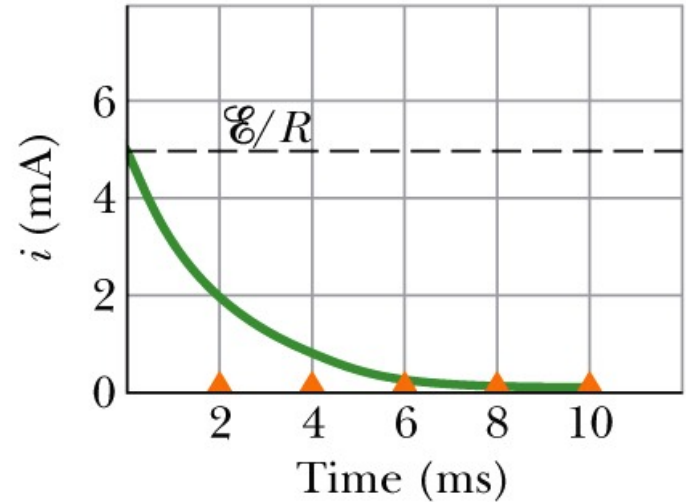

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

$$q = \epsilon C (1 - e^{-t/RC}) = \overset{\substack{\text{CV} \\ \uparrow}}{Q_f} (1 - e^{-t/RC})$$


charge of fully charged capacitor

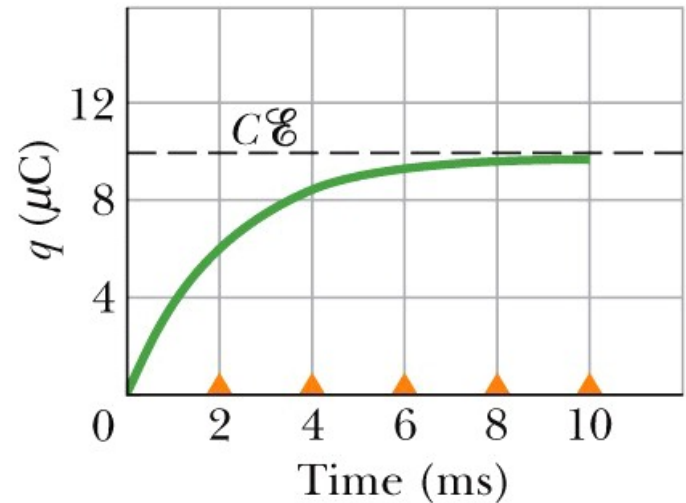

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.


Case 2: Discharging a capacitor

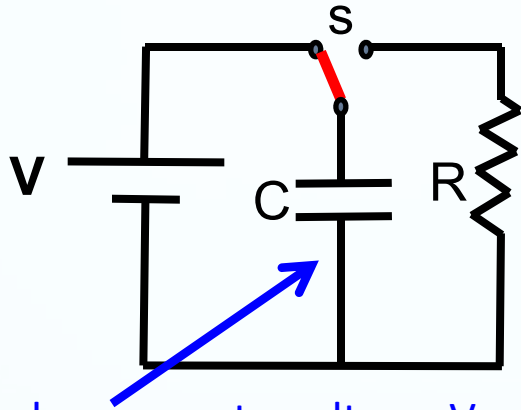Switch is connected to the left for a long time until $t=0^-$



Capacitor charges up to voltage V

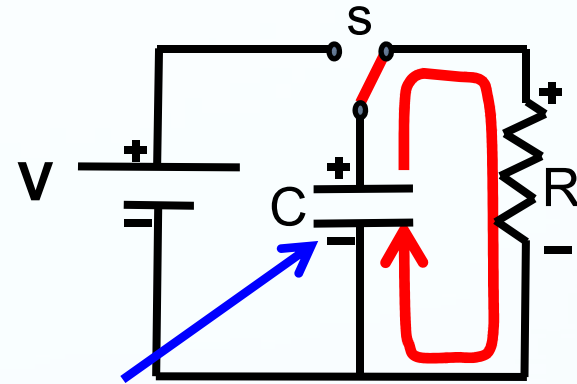
Switch is suddenly flipped to the right at $t=0^+$



Capacitor discharges

$$q(t) = q_0 e^{-t/RC}$$



$$i(t) = i_0 e^{-t/RC}$$

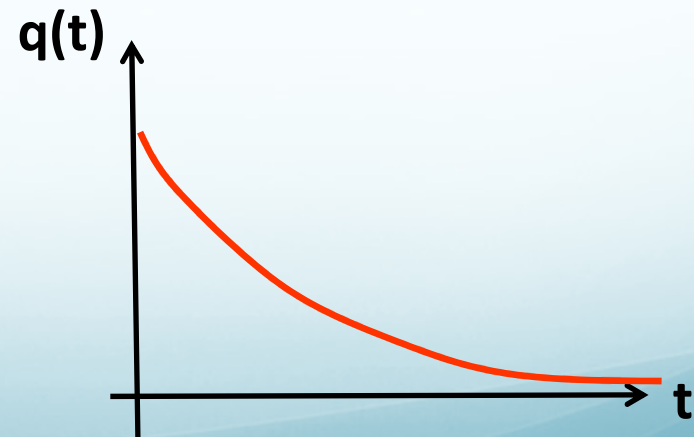

Charging/Discharging Capacitors



Charging: $q(t) = Q_f \left(1 - e^{-\frac{t}{RC}} \right)$


$$i(t) = i_0 e^{-\frac{t}{RC}}$$

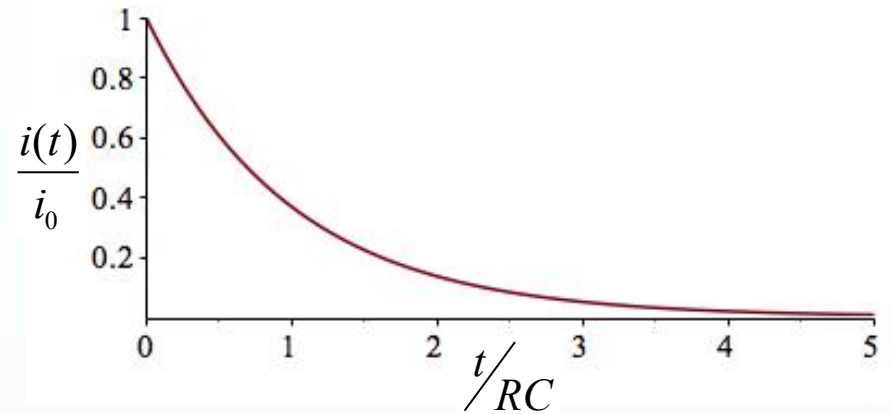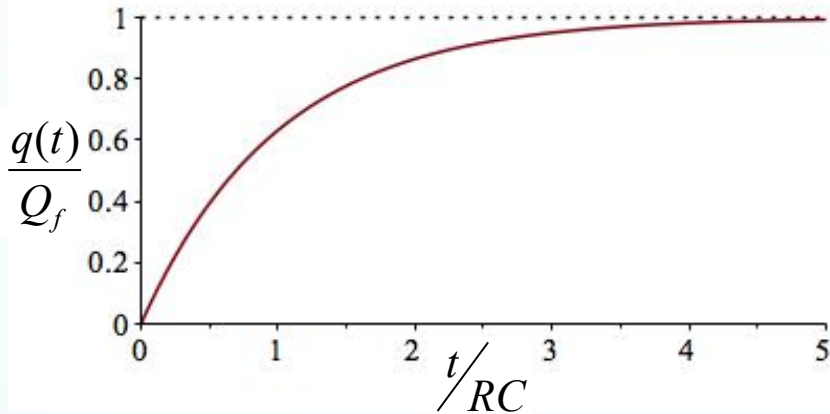

Discharging: $q(t) = Q_0 e^{-\frac{t}{RC}}$

$$i(t) = i_0 e^{-\frac{t}{RC}}$$

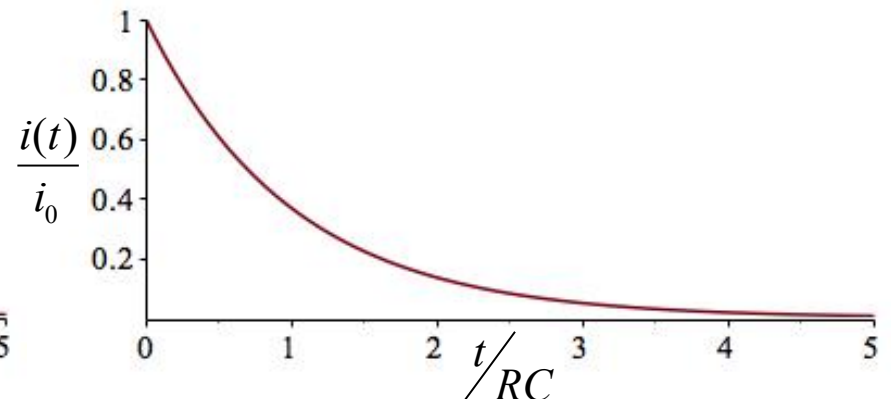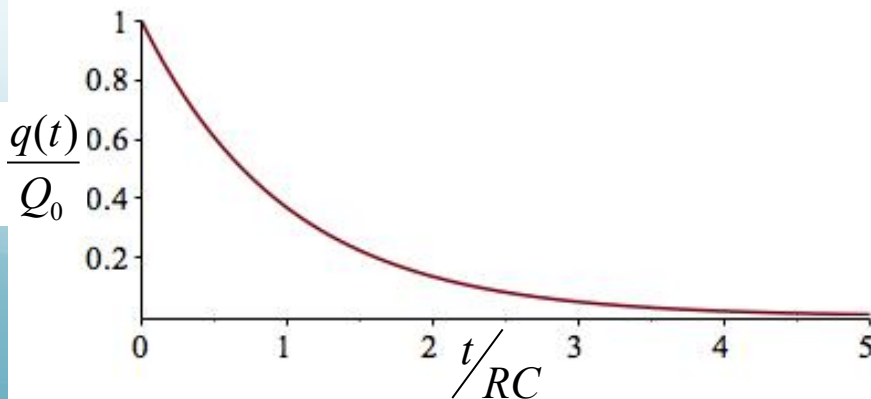

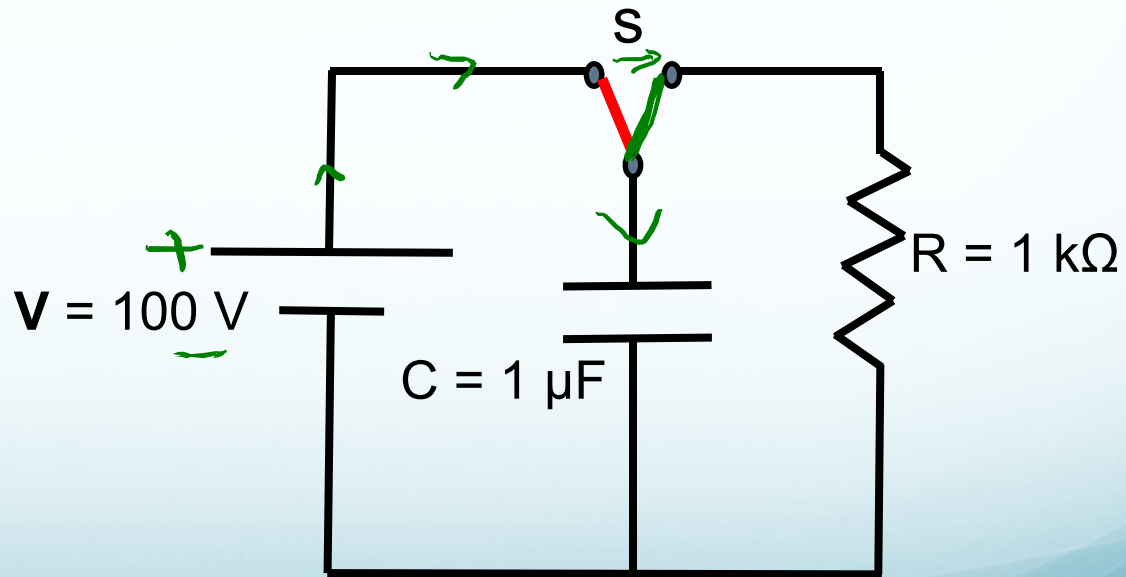

I in this circuit

The RC time constant

The constant RC pops up in the exponential factor for both charging and discharging capacitors. What does it represent?

The units of RC is seconds: $[RC] = \frac{V}{A} \frac{C}{V} = \frac{C}{C/s} = s$

We call RC the “**RC time constant**” and it tells us how quickly a capacitor can charge or discharge.

$$RC \equiv \tau$$

After a time τ , the charge on a discharging capacitor is reduced by a factor of $1/e$. After a time $N\tau$, it is reduced by a factor of $1/e^N$


$$q(t) = Q_0 e^{-\frac{t}{\tau}}$$

Top Hat Question

An RC circuit is shown below. Initially the switch is open and the capacitor is fully charged. At time $t = 0$, the switch is closed.

How much charge is left on the capacitor plates after $t = 10 \text{ ms}$?

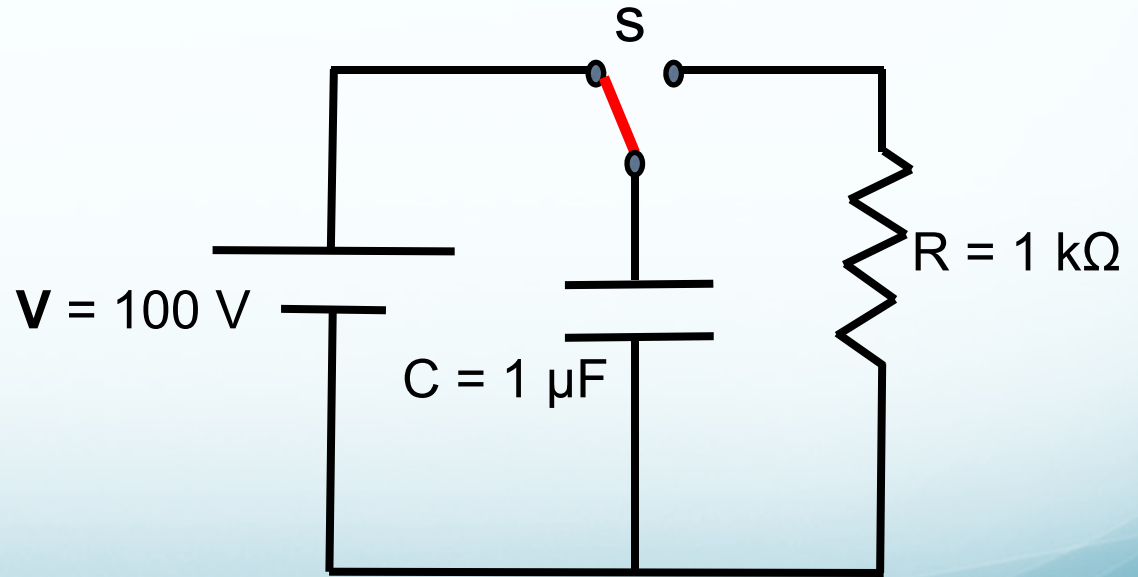- A. 0.67 nC
- B. $14 \text{ } \mu\text{C}$
- C. $37 \text{ } \mu\text{C}$
- D. 4.5 nC




Top Hat Question

An RC circuit is shown below. Initially the switch is open and the capacitor is fully charged. At time $t = 0$, the switch is closed.

How much charge is left on the capacitor plates after $t = 10$ ms?

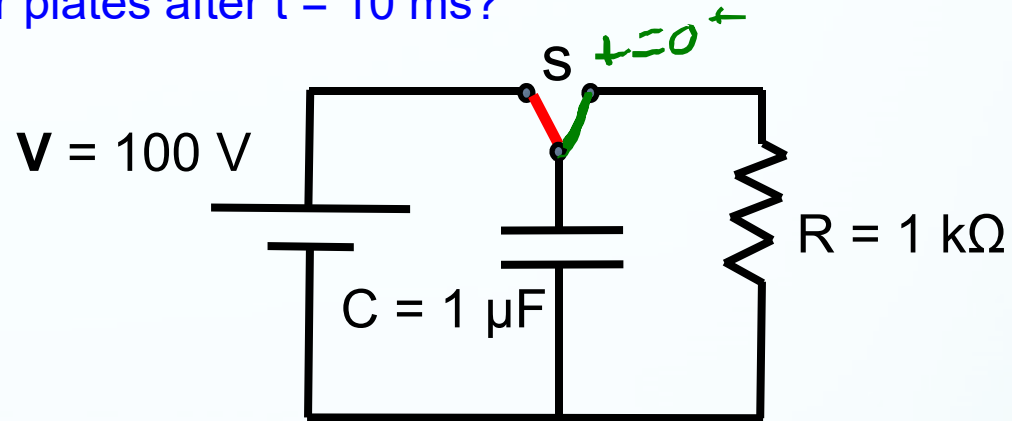- A. 0.67 nC
- B. 14 μC
- C. 37 μC
- D. 4.5 nC



discharging $\rightarrow q(t) = q_0 e^{-t/RC}$

$q_0 \rightarrow q_f$ of charging $\Rightarrow q_0 = CV$
 $= 1\ \mu\text{F} \times 100\text{ V} = 100\ \mu\text{C}$


$\rightarrow q(t) = 100\ \mu\text{C} \times e^{-t/RC} = (100\ \mu\text{C}) e^{-\frac{10}{1\text{ ms}}}$

$q(t) = (100\ \mu\text{C}) e^{-\frac{10}{1\text{ ms}}} = 4.54\ \text{nC}$

$V = 100\text{ V}$
 $R = 1\ \text{k}\Omega$
 $C = 1\ \mu\text{F}$

Kirchhoff's junction rule

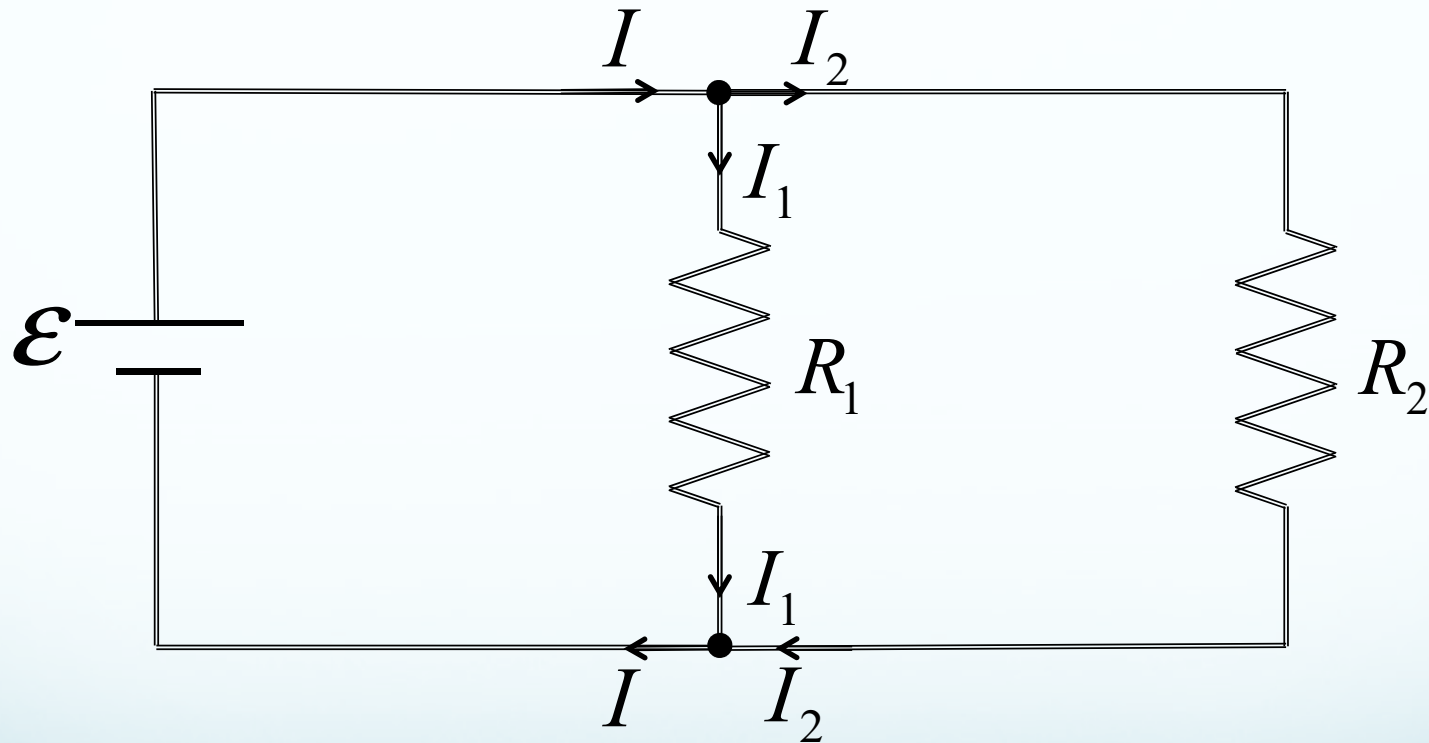A slightly more complicated circuit has multiple branches with resistors in parallel



Current is the flow of charges. Charge has to be conserved.

Current into junction = current out of junction

$$I = I_1 + I_2$$

This section we talked about:

Chapter 27

See you on Monday

