

Wednesday Mar 8, 2017

# Last time:

- Capacitors
- Capacitance as a geometric quantity
- General Capacitors, relating  $Q$  to  $\Delta V$
- Setting up a process to find Capacitance


# Today:

- Energy stored in parallel plate, spherical, and cylindrical capacitors
- Potential energy stored in the electric field itself.
- Capacitors in electric circuits: how charges move
- Kirchhoff's loop rule with capacitors
- Capacitors in series and parallel
- More complicated capacitor circuit
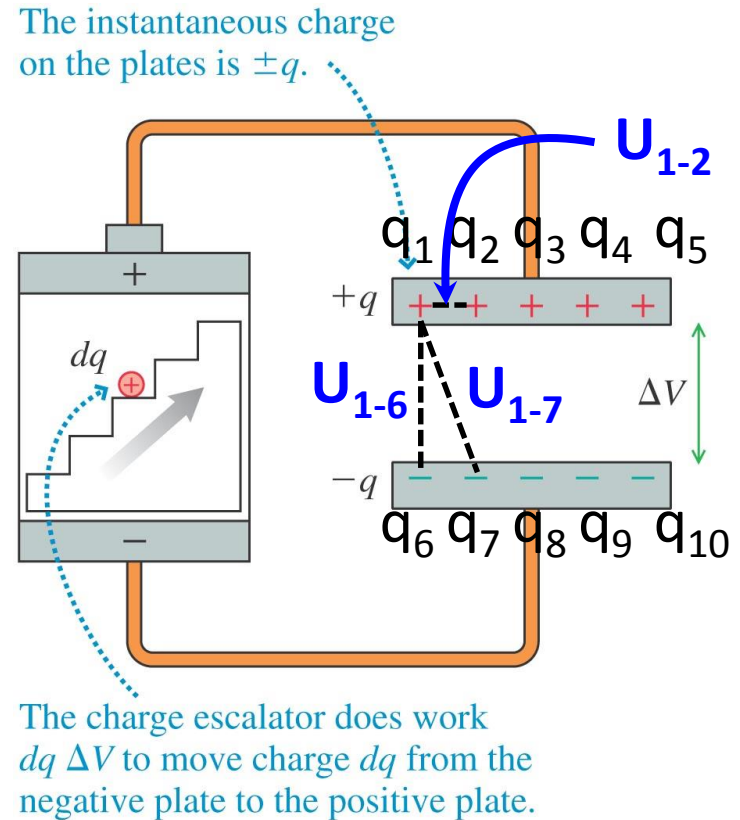
# Energy Storage in Capacitors

We want to calculate this potential energy stored in the capacitor.

It is **way** too hard to add up all the potential energies of every pair of charges in the capacitor:



$$U = U_{1-2} + U_{1-3} + \dots + U_{1-10} + U_{2-1} + \mathbf{U_{ij} \text{ of every other pair}}$$

## Easier way!

Move a tiny charge,  $dq$ , from the negative plate to the positive plate.

It moves through a potential difference  $\Delta V$ .


So its potential energy increases by an amount

$$dU = dq DV_C$$

But we also know  $DV_C = \frac{q}{C}$

$$dU = dq \frac{q}{C} = \frac{q dq}{C}$$

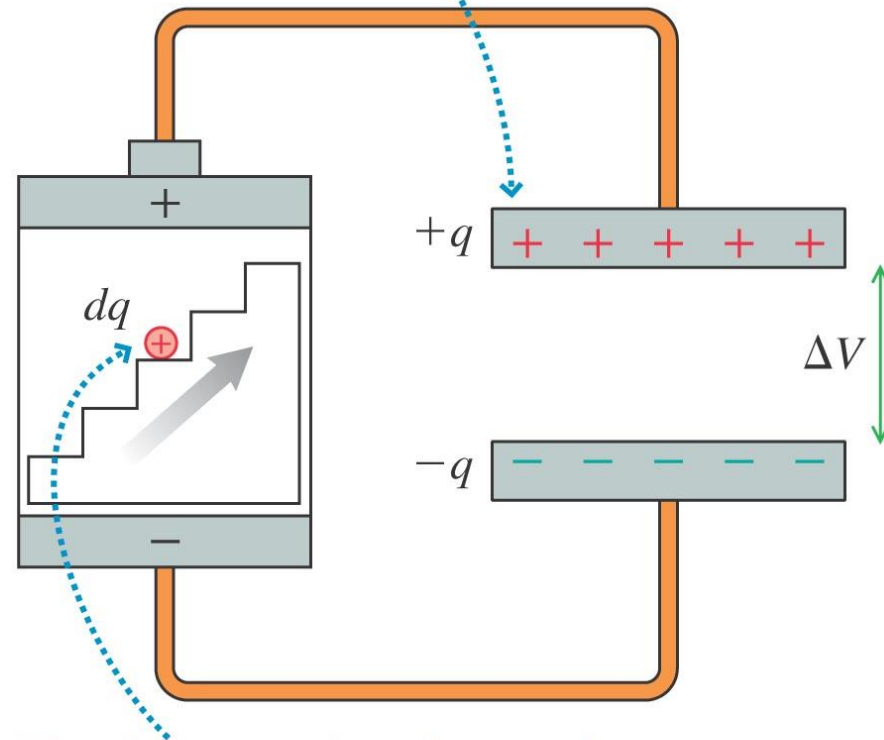The instantaneous charge on the plates is  $\pm q$ .



The charge escalator does work  $dq \Delta V$  to move charge  $dq$  from the negative plate to the positive plate.

Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley.

$$U = \frac{1}{C} \int_0^Q q dq = \frac{1}{2} \frac{Q^2}{C}$$

# Potential Energy in a Capacitor

Energy storage in terms of the charge on the plates:

$$U = \frac{1}{2} \frac{Q^2}{C}$$

Use the general relation for a capacitor to swap charge for voltage

$$Q = CDV_c$$

Energy storage in terms of the voltage across the plates:

$$U = \frac{1}{2} \frac{(CDV_c)^2}{C}$$
$$= \frac{1}{2} C (DV_c)^2$$

# Where is the Energy Stored?

$$U = \frac{1}{2} C (DV_C)^2$$


$$= \frac{1}{2} C E^2 d^2$$

$$= \frac{1}{2} \frac{e_0 A}{d} E^2 d^2 = \frac{1}{2} e_0 E^2 (Ad)$$

$$DV = Ed$$

$$C = \frac{e_0 A}{d}$$

$$u = \frac{U}{Ad}$$

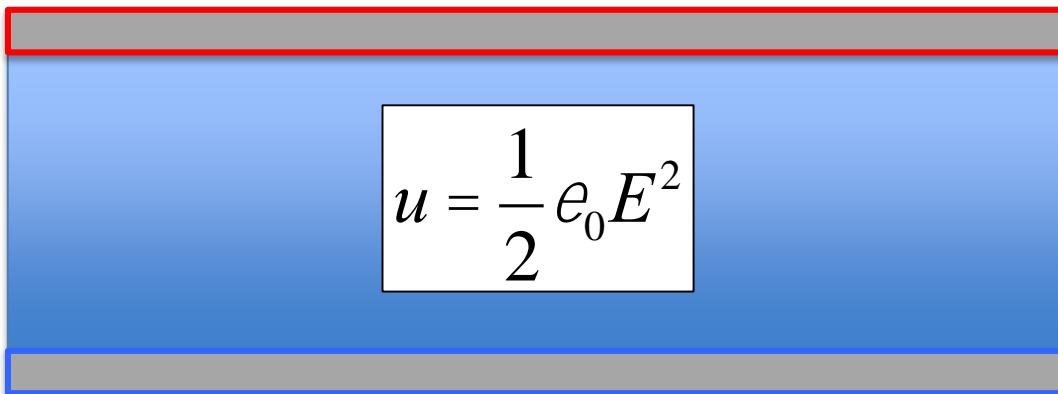


The capacitor's energy is stored in the electric field between the plates!
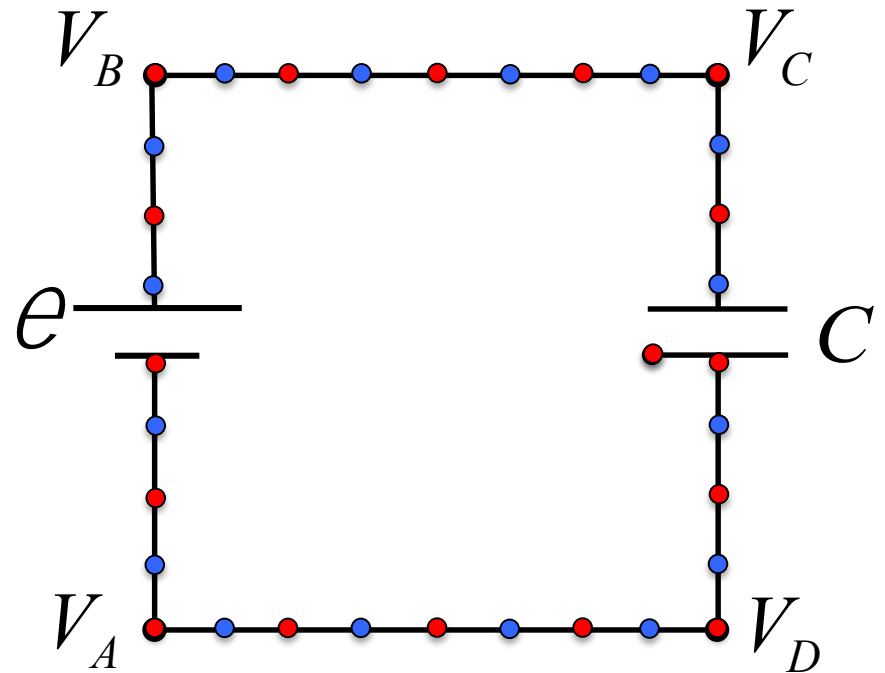
# A Basic Circuit with Capacitor

The simplest capacitor circuit has an ideal battery, ideal wires, and a single capacitor.


The battery causes charges to flow from the bottom plate to the top plate. This creates a potential  $\Delta V_C$  between the two plates. Remember charges never “jump the gap” between the two plates of a capacitor.


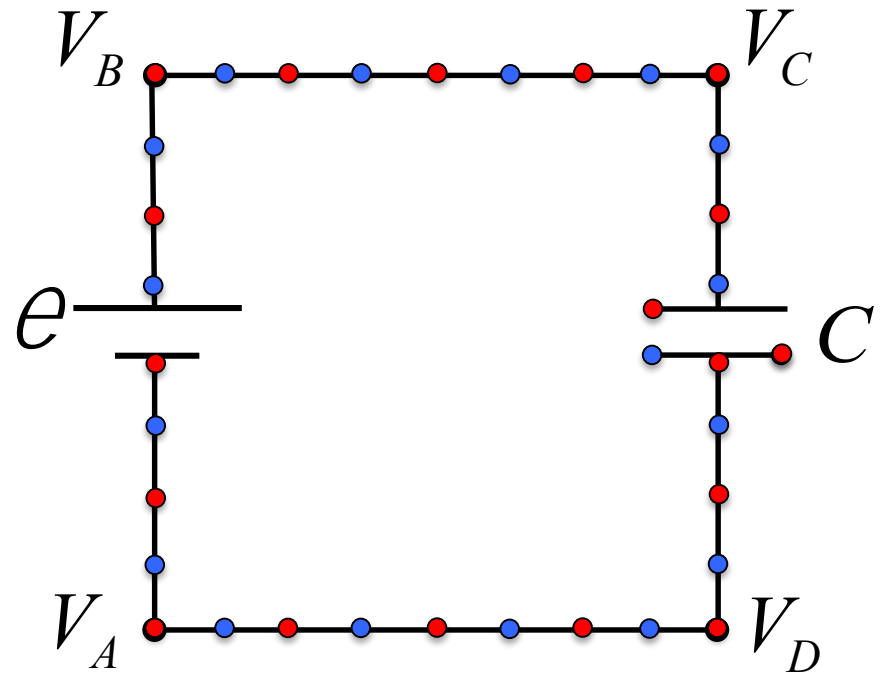
# A Basic Circuit with Capacitor

The simplest capacitor circuit has an ideal battery, ideal wires, and a single capacitor.

The battery causes charges to flow from the bottom plate to the top plate. This creates a potential  $\Delta V_C$  between the two plates. Remember charges never “jump the gap” between the two plates of a capacitor.





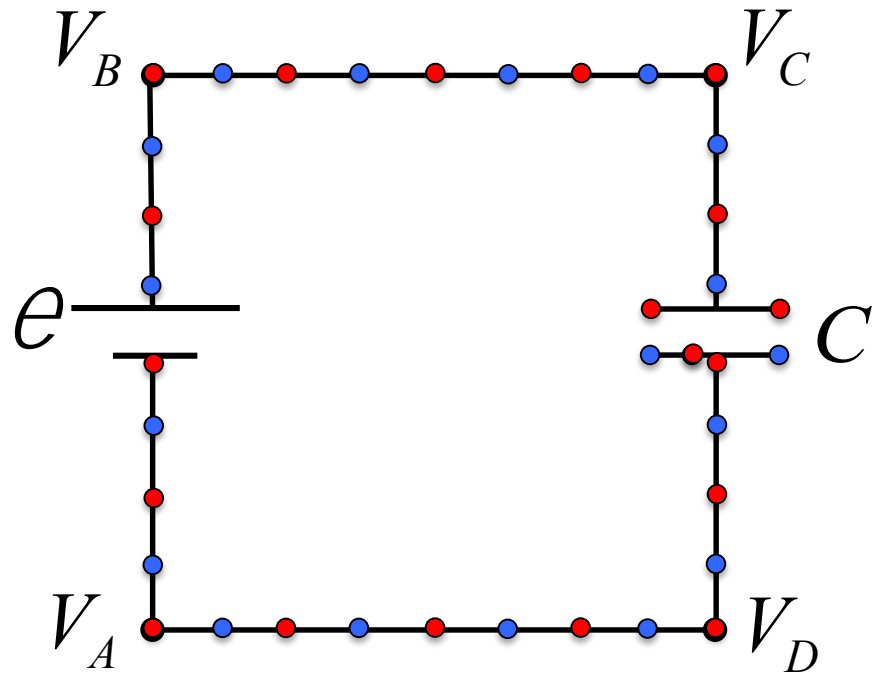
# A Basic Circuit with Capacitor

The simplest capacitor circuit has an ideal battery, ideal wires, and a single capacitor.


The battery causes charges to flow from the bottom plate to the top plate. This creates a potential  $\Delta V_C$  between the two plates. Remember charges never “jump the gap” between the two plates of a capacitor.


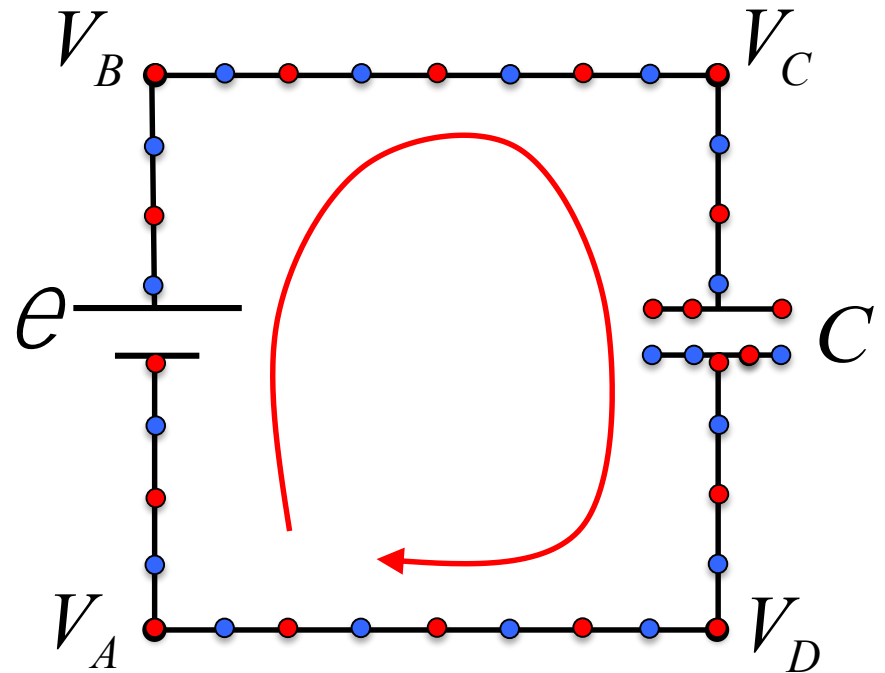
# A Basic Circuit with Capacitor

The simplest capacitor circuit has an ideal battery, ideal wires, and a single capacitor.


The battery causes charges to flow from the bottom plate to the top plate. This creates a potential  $\Delta V_C$  between the two plates. Remember charges never “jump the gap” between the two plates of a capacitor.



$$\Delta V_{AB} + \Delta V_{BC} + \Delta V_{CD} + \Delta V_{DA} = 0$$
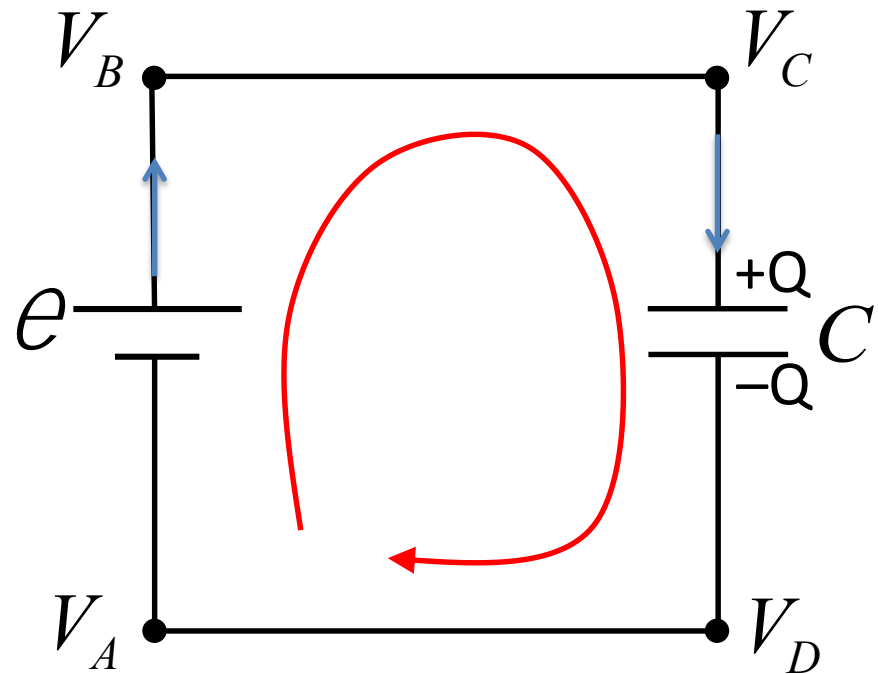
# A Basic Circuit

The voltage across a capacitor is **negative** if you are going around the loop in the direction **from the + plate to the – plate**. Current flows **from the negative terminal to the positive terminal**



ideal wires


$$\Delta V_{AB} + \cancel{\Delta V_{BC}} + \Delta V_{CD} + \cancel{\Delta V_{DA}} = 0$$

$$e - \frac{Q}{C} = 0$$
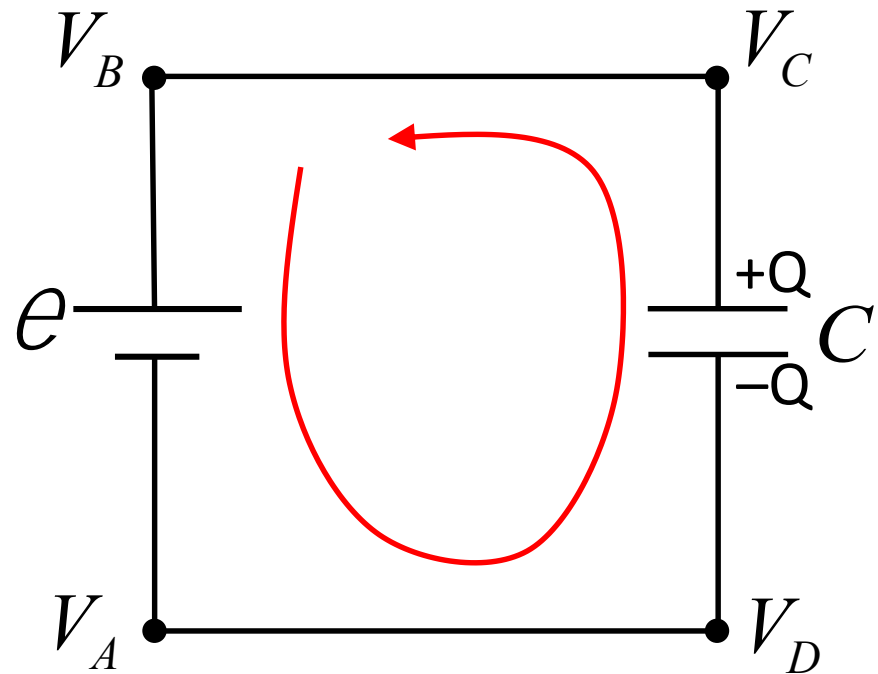
# A Basic Circuit

The voltage across a capacitor is **positive** if you are going around the loop in the direction **from – plate to + plate**.

Voltage across a battery is **negative** going **from positive to negative**



$$\Delta V_{BA} + \cancel{\Delta V_{AD}} + \Delta V_{DC} + \cancel{\Delta V_{CB}} = 0$$

ideal wires

$$-e + \frac{Q}{C} = 0$$


Same as before

# TopHat Question
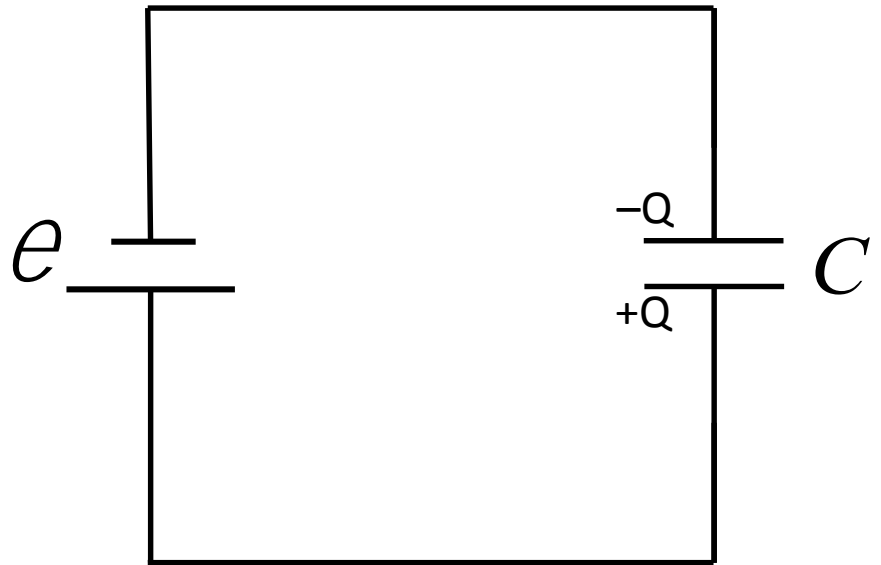
# TopHat Question

What is the charge on the top plate of the capacitor in the circuit shown?

$\mathcal{E} = 12 \text{ V}$  and  $C = 0.25 \text{ }\mu\text{F}$ .



A.  $Q = 3.0 \text{ }\mu\text{C}$


B.  $Q = 48 \text{ }\mu\text{C}$

C.  $Q = 21 \text{ nC}$

D.  $Q = -3.0 \text{ }\mu\text{C}$
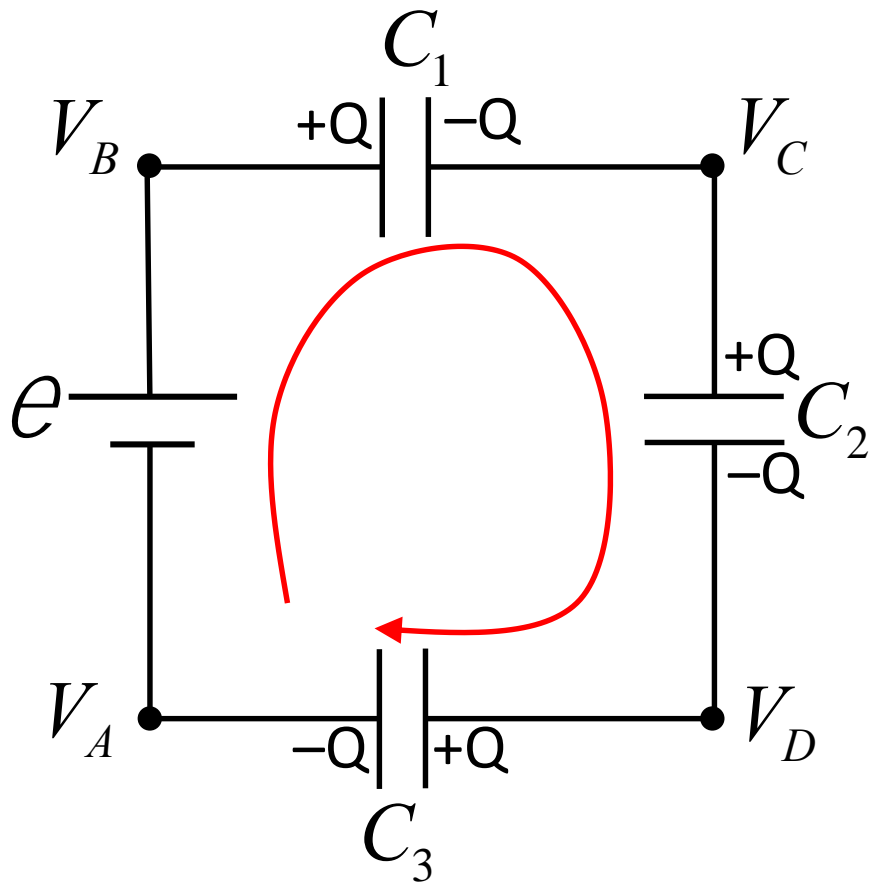
# Capacitors in Series

A slightly more complicated circuit has multiple capacitors in series



Kirchhoff's Loop Rule:

$$\Delta V_{AB} + \Delta V_{BC} + \Delta V_{CD} + \Delta V_{DA} = 0$$

Charge on each plate is the same

$$e - \frac{Q}{C_1} - \frac{Q}{C_2} - \frac{Q}{C_3} = 0$$


Rewrite this as

$$e - Q \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) = 0$$

Define an equivalent capacitance

$$e - \frac{Q}{C_{eq}} = 0$$

# Capacitors in Series

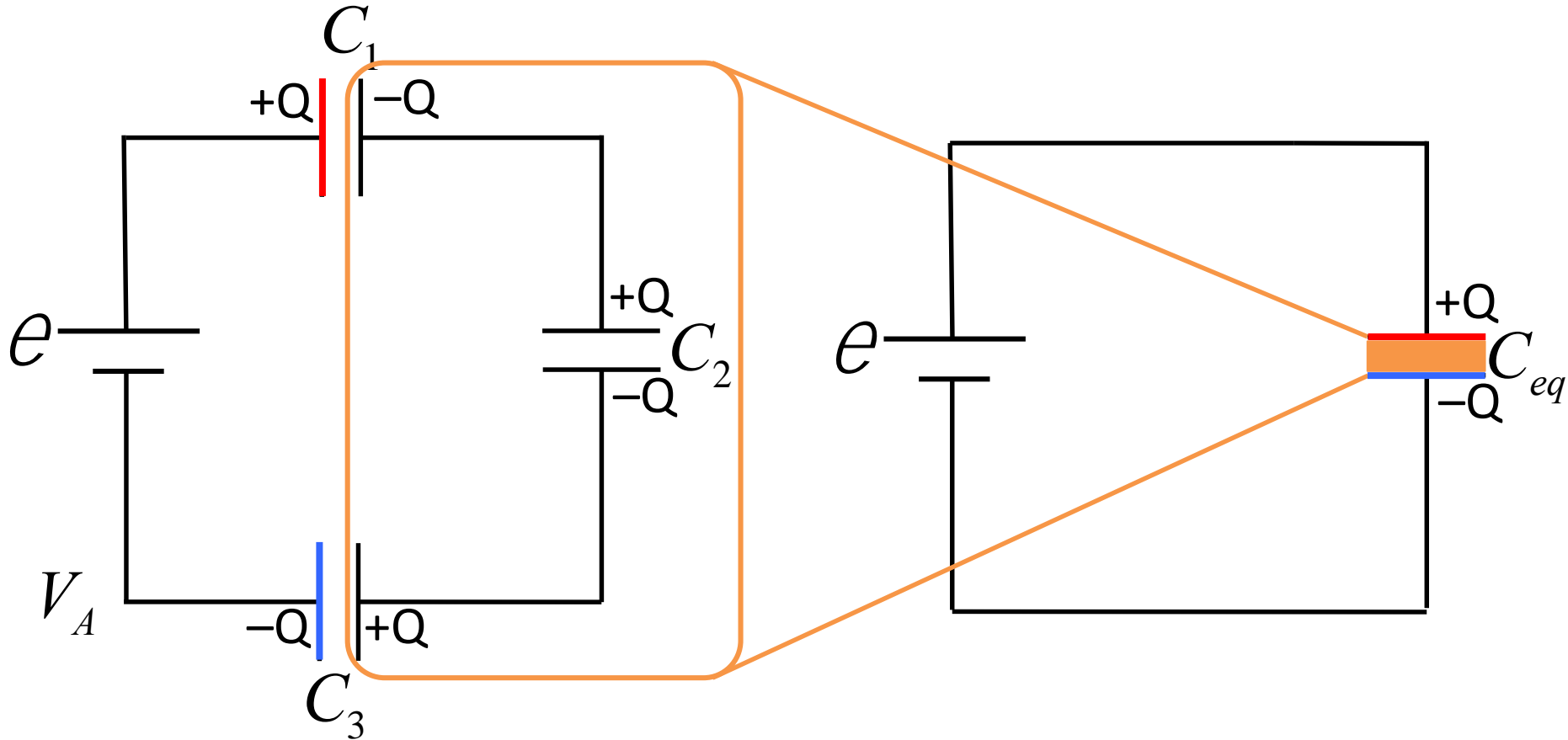


Capacitors in series act like a single equivalent capacitor:

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$


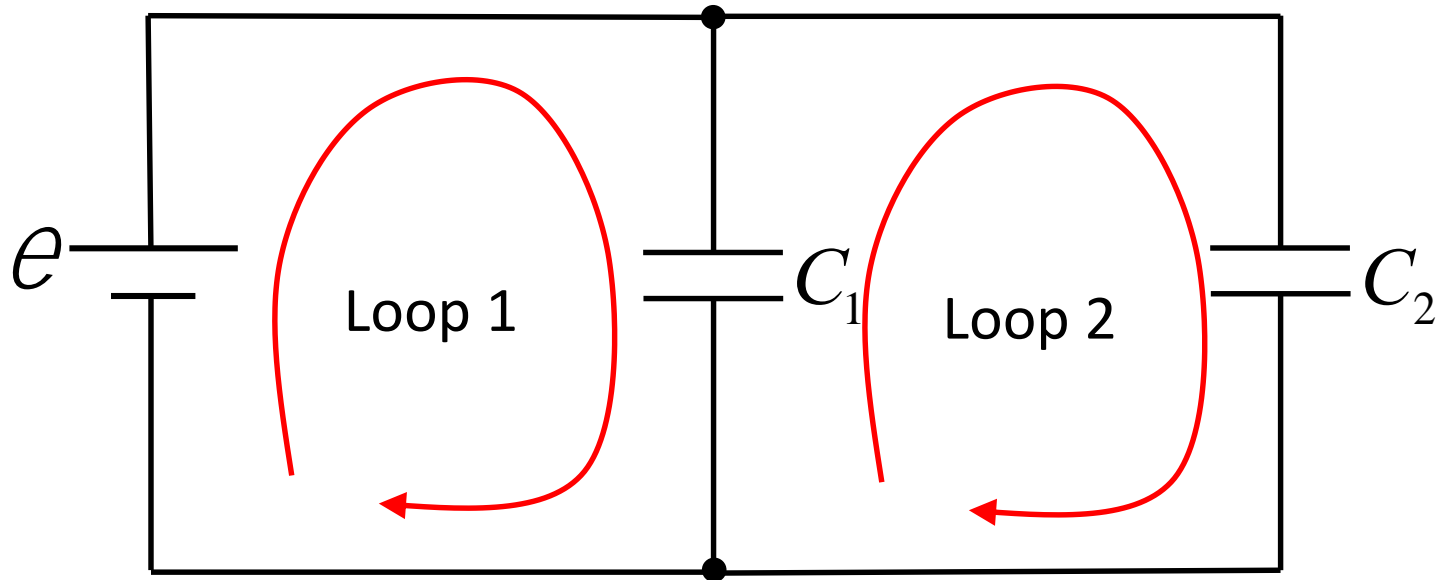
# Capacitors in Parallel


A slightly more complicated circuit has multiple branches with capacitors in parallel



Capacitors in parallel have the same voltage across their plates

$$\text{Loop 1: } e - \Delta V_{C_1} = 0 \quad \text{Loop 2: } \Delta V_{C_1} - \Delta V_{C_2} = 0$$

# Capacitors in Parallel

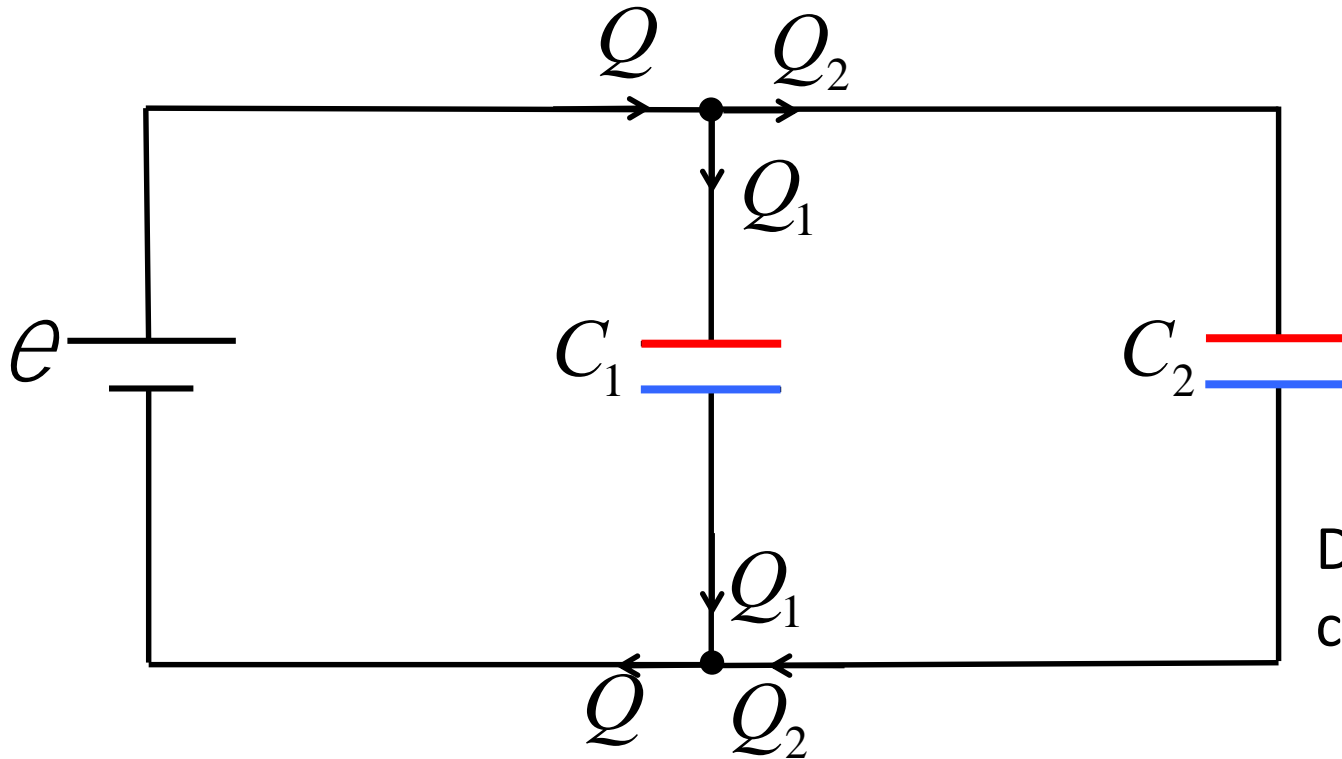

$$Q = Q_1 + Q_2$$

$$Q_1 = \Delta V_{C_1} C_1$$

$$Q_2 = \Delta V_{C_2} C_2$$


Define an equivalent capacitance:

$$Q = \mathcal{E} C_{eq}$$

From conservation of charge:  $\mathcal{E} C_{eq} = \mathcal{E} C_1 + \mathcal{E} C_2$

For capacitors in parallel:  $C_{eq} = C_1 + C_2$

# Capacitors in Parallel

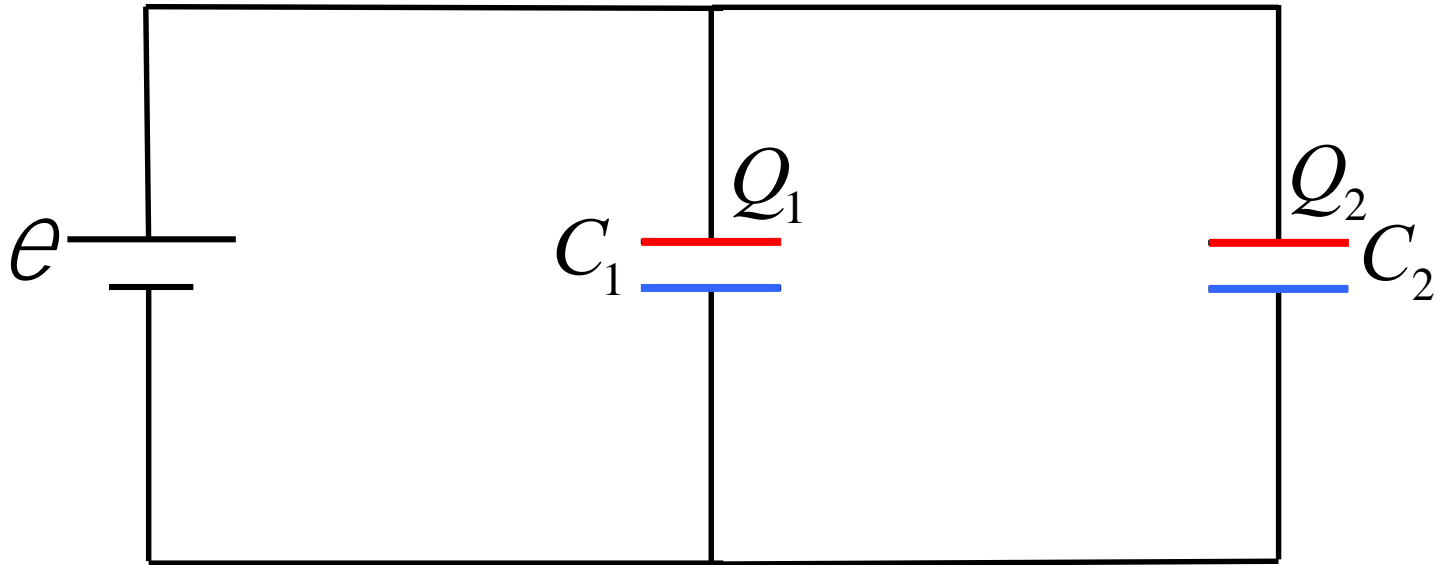

$$Q = Q_1 + Q_2$$

$$C_{eq} = C_1 + C_2$$

# Summary of Capacitors

Relation between charge and voltage across plates

$$\Delta V_C = \frac{Q}{C}$$


Capacitors in Series: store the same amount of charge

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}}$$

Capacitors in Parallel: have the same voltage across them

$$C_{eq} = C_1 + C_2 + \dots + C_N$$

# On document camera

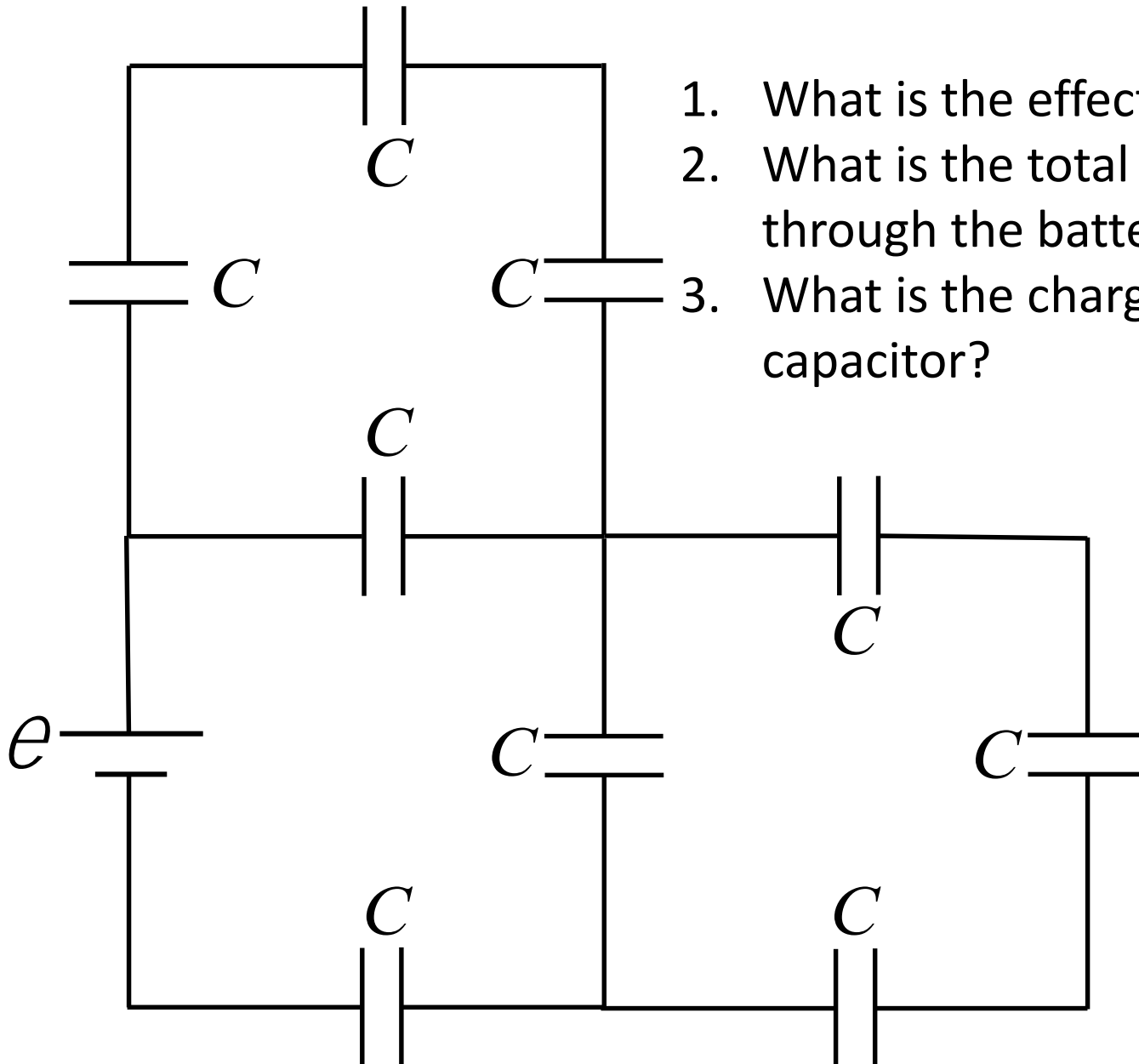

1. What is the effective capacitance?
2. What is the total charge moved through the battery?
3. What is the charge on each capacitor?

Wednesday March 8, 2017 class 2

## Last time:

- Energy stored in parallel plate, spherical, and cylindrical capacitors
- Potential energy stored in the electric field itself.
- Capacitors in electric circuits: how charges move
- Kirchhoff's loop rule with capacitors
- Capacitors in series and parallel
- More complicated capacitor circuit

## Today:

- Subtlety with capacitors: series or parallel?
- Linear dielectric materials: an atomic perspective
- Effect of dielectrics on capacitance
- Applications of dielectrics and capacitors

# Summary of Capacitors

Relation between charge and voltage across plates

$$\Delta V_C = \frac{Q}{C}$$

Capacitors in Series: store the same amount of charge


$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}}$$

Capacitors in Parallel: have the same voltage across them

$$C_{eq} = C_1 + C_2 + \dots + C_N$$



# On document camera

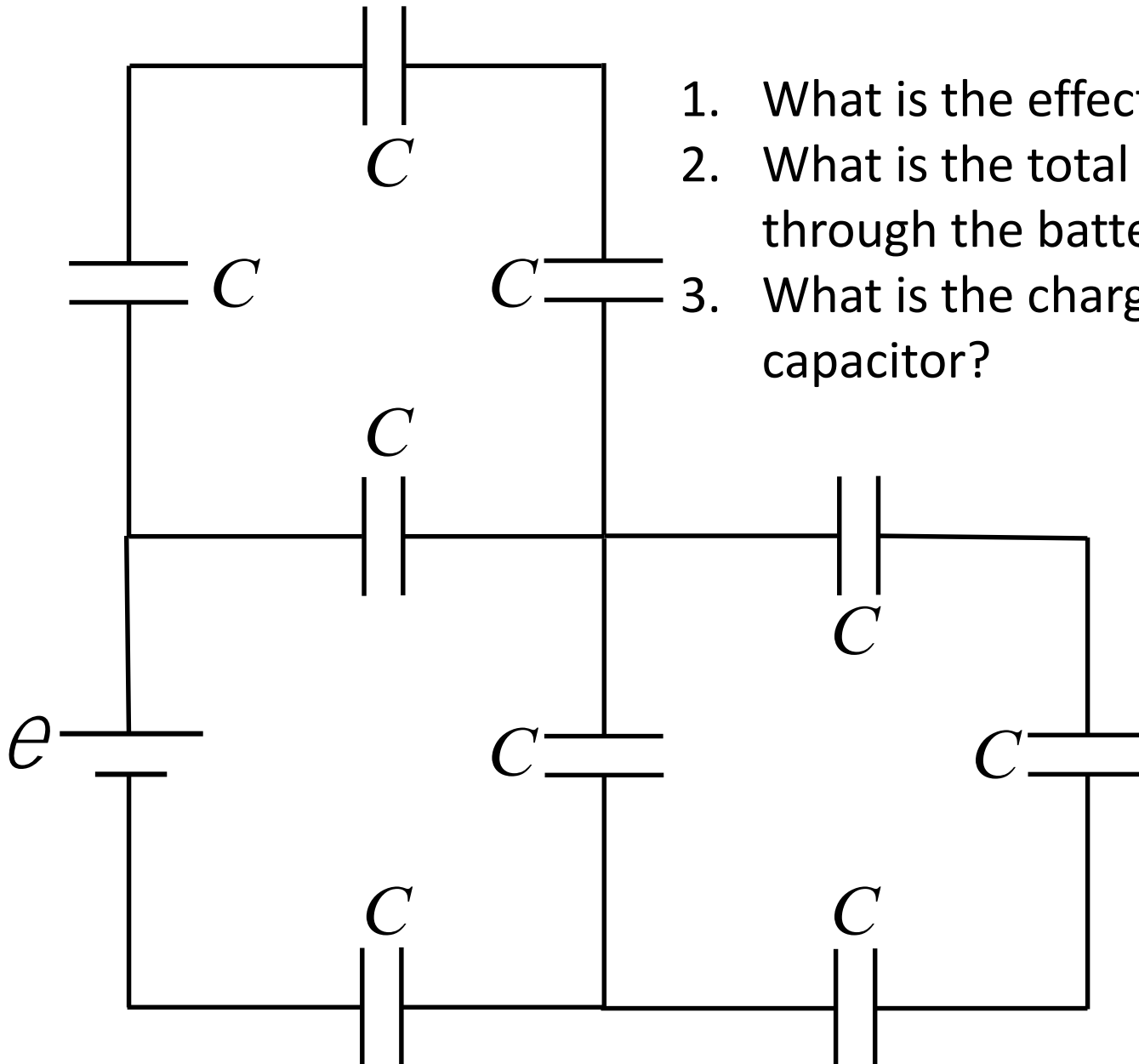

1. What is the effective capacitance?
2. What is the total charge moved through the battery?
3. What is the charge on each capacitor?

# Capacitor Subtlety


Are these capacitors in series or parallel?

The **plates** are **conductors**,  
and so are the **wires**.

The **top half** of the circuit  
is **electrically disconnected**  
from the **bottom half**.

**Top half** is at potential  $V_A$   
and the **bottom half** is at  
potential  $V_B$ .

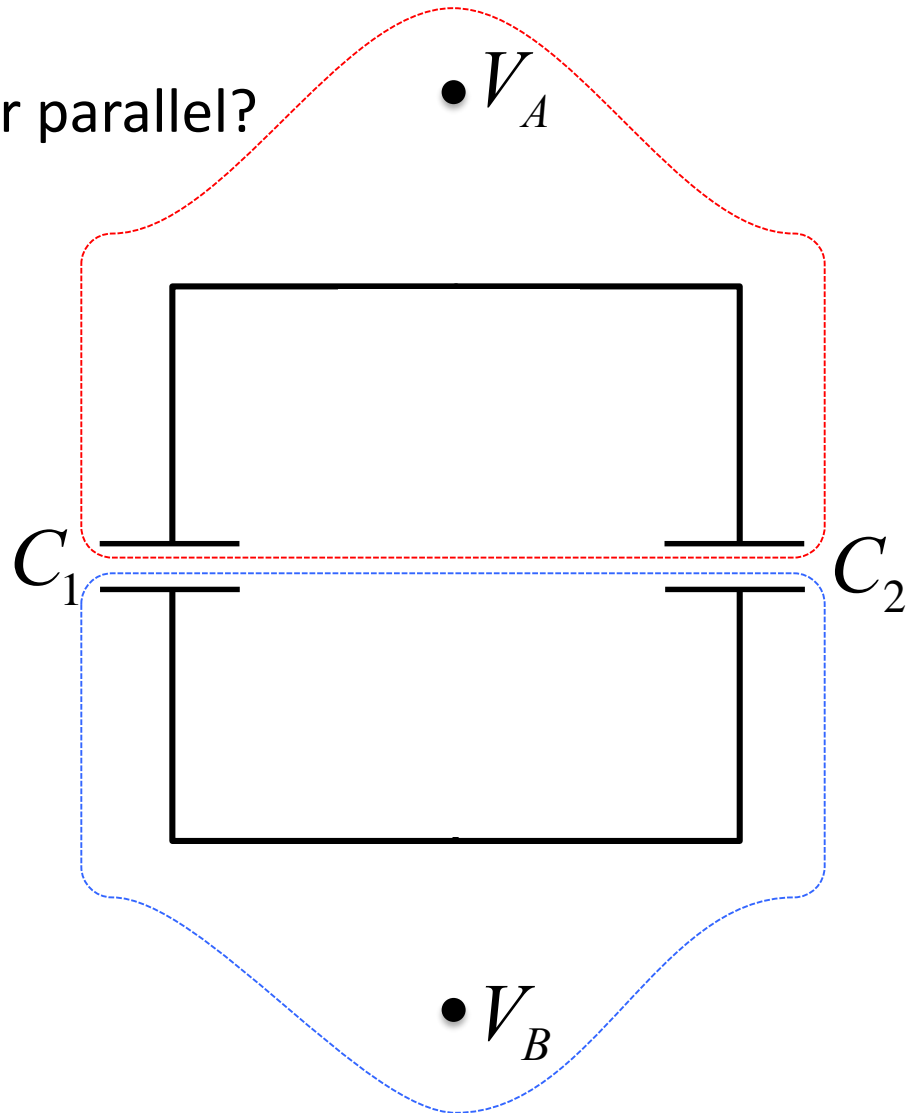
**These capacitors are in  
parallel! They have the  
same voltage across them**



$$Q = C_0 V_0$$

(a)  $V_0 = E_0 d$


Vacuum

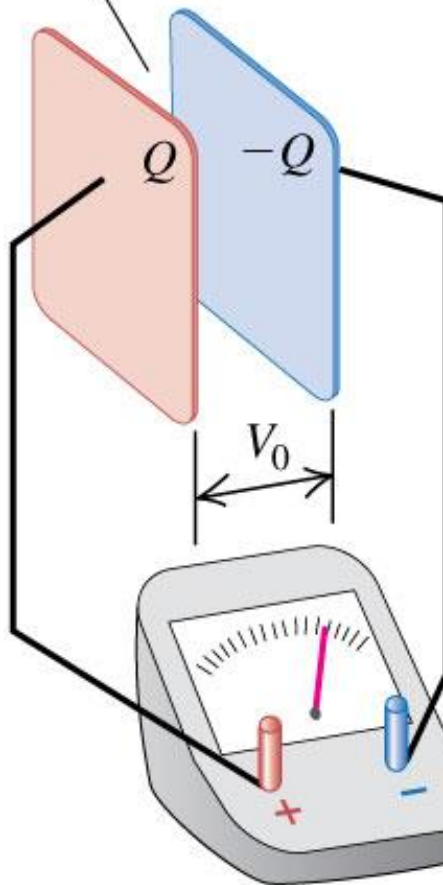

Electrometer  
(measures potential  
difference across  
plates)

(b)

Dielectric

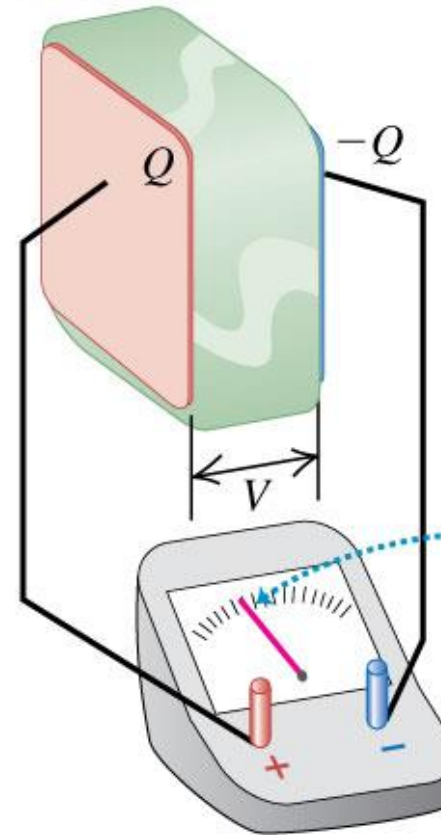

$$Q = CV$$

$$V < V_0$$

$$C > C_0$$


Adding the dielectric  
*reduces* the potential  
difference across the  
capacitor.

$$V = Ed$$

$$E < E_0$$

# non-polar molecules


(a)

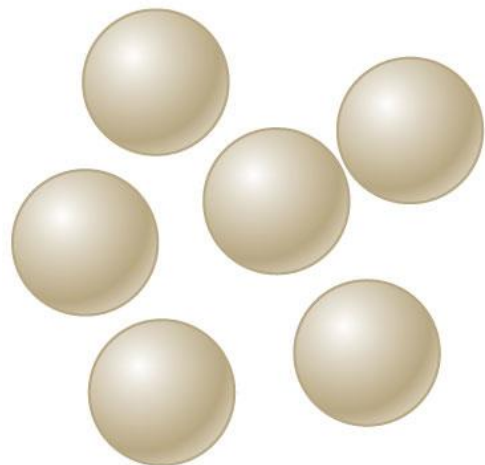

In the absence of an electric field, nonpolar molecules are not electric dipoles.


© 2012 Pearson Education, Inc.

(b)


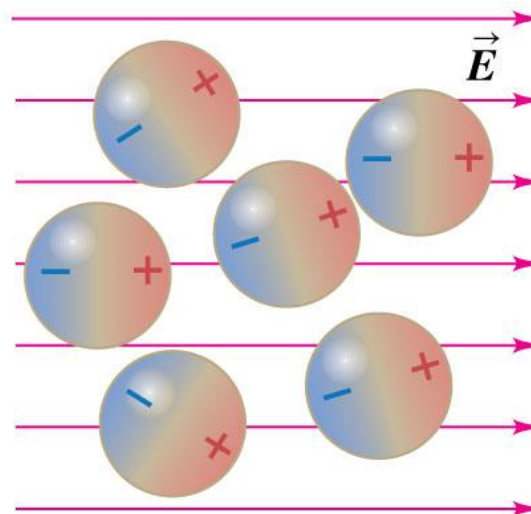


An electric field causes the molecules' positive and negative charges to separate slightly, making the molecule effectively polar.

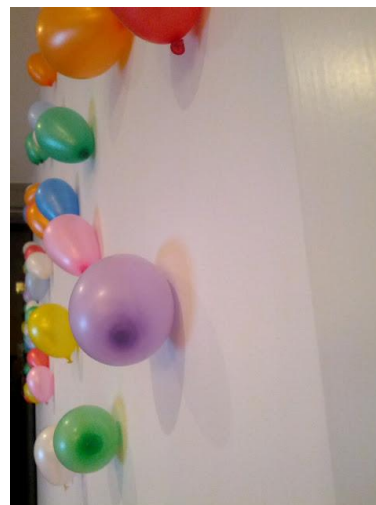
Recall the balloon on the wall example from week 1



# polar molecules

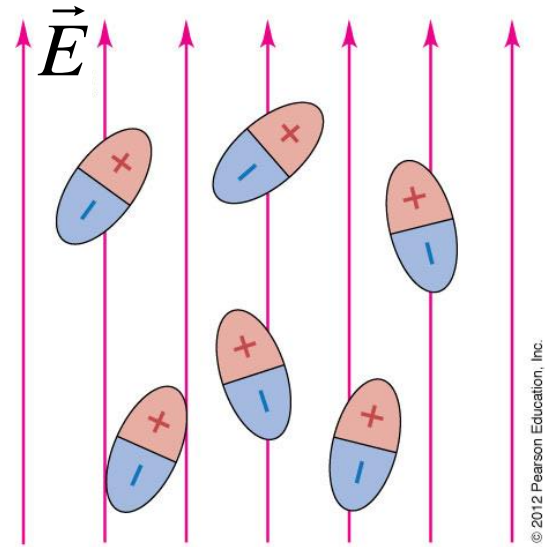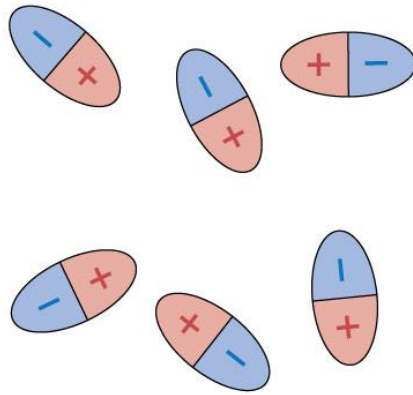


(a) No dielectric

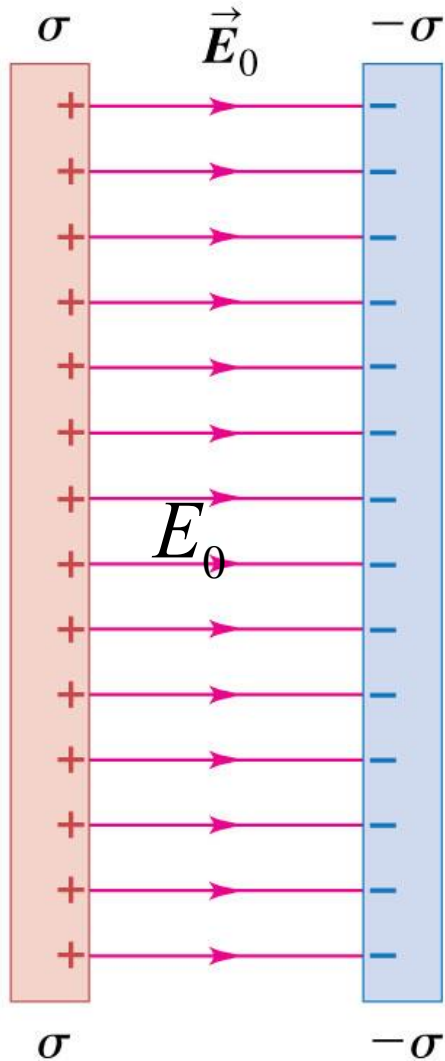


© 2012 Pearson Education, Inc.

(b) Dielectric just inserted

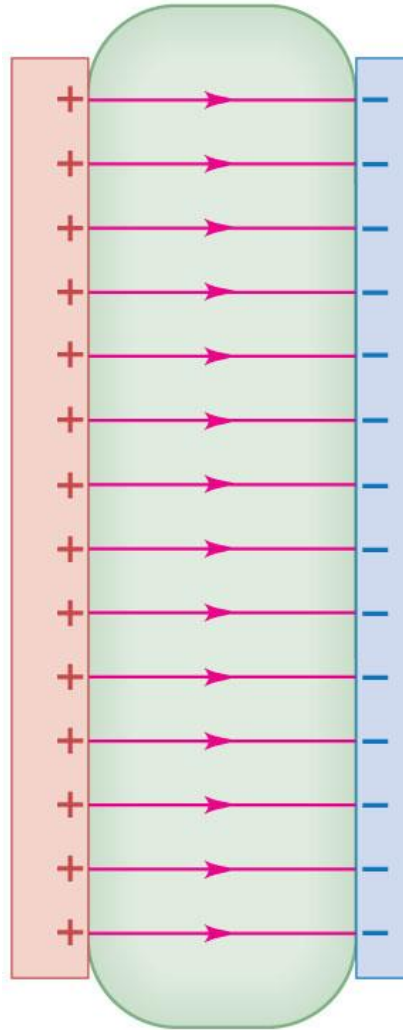

© 2012 Pearson Education, Inc.

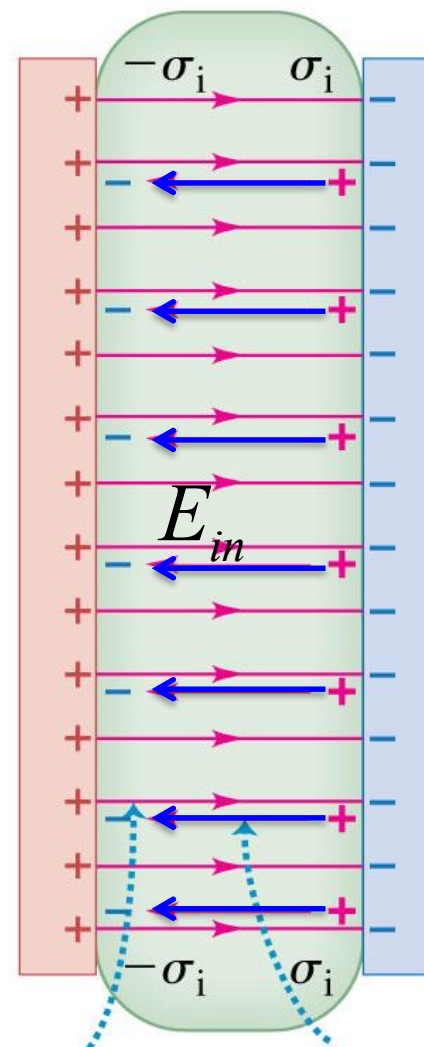(c) Induced charges create electric field



Original  
electric field

Weaker field in dielectric  
due to induced (bound) charges

$$E_{in} = E_0 - E_{diel}$$

$$E_{in} < E_0$$


$$E_{in} = \frac{E_0}{K}$$

© 2012 Pearson Education, Inc.


# Linear Dielectrics

Materials in which the induced polarization is proportional to the electric field are called **linear dielectrics**.

(a)

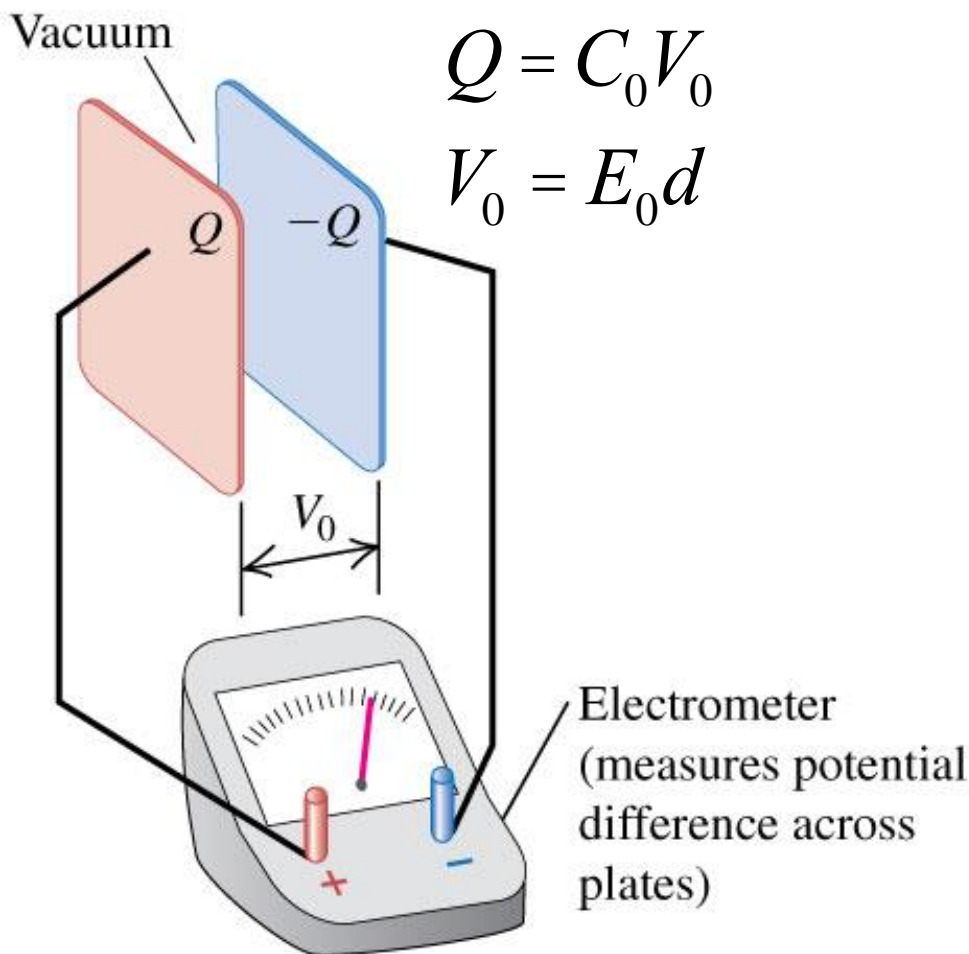

b)

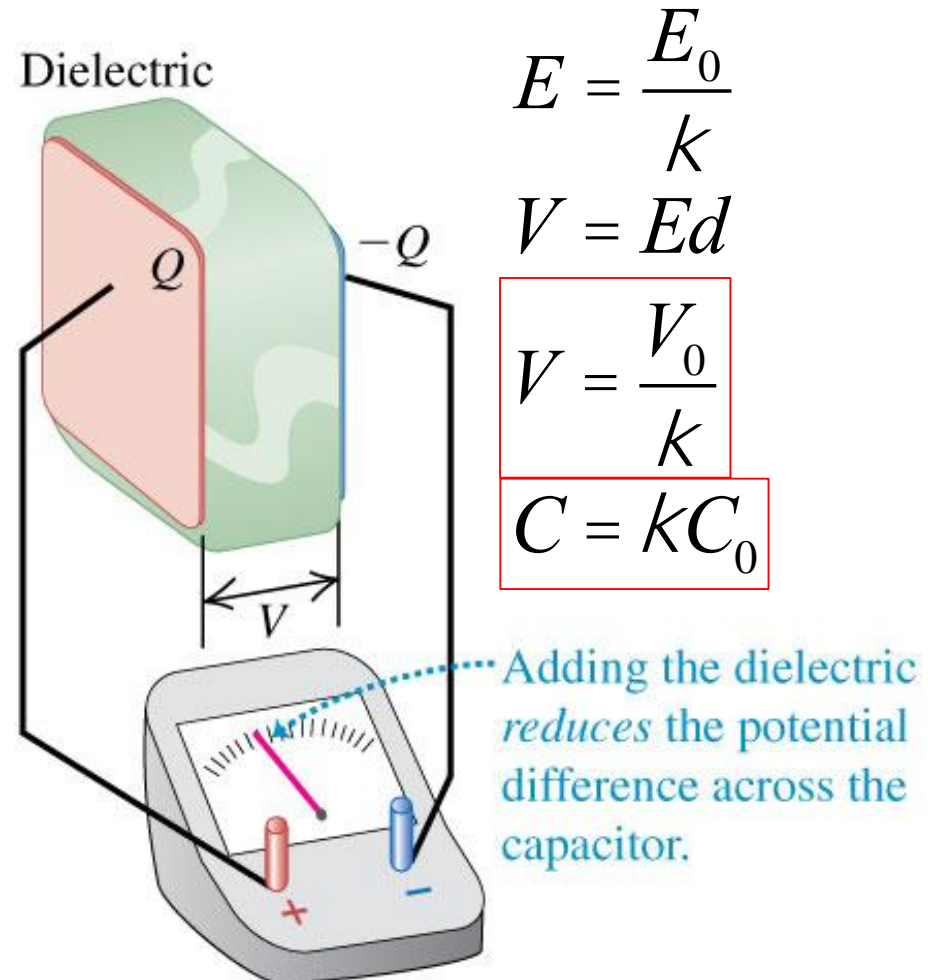

# Parallel Plate Capacitors With and Without Dielectrics

$$E_0 = \frac{S}{e_0}$$

$$E = \frac{E_0}{k} = \frac{S}{ke_0}$$

$$V_0 = E_0 d = \frac{Sd}{e_0}$$

$$V = \frac{V_0}{k} = \frac{Sd}{ke_0}$$

$$C_0 = \frac{Q}{V_0} = \frac{SA}{Sd} e_0 = \frac{Ae_0}{d}$$

$$C = kC_0 = \frac{Ake_0}{d}$$

Conclusion: for a linear dielectric, all the regular electrostatic equations hold if  $e_0 \rightarrow e \equiv ke_0$

Now you see why  $e_0$  is called “permittivity of free space” (i.e. in vacuum)



# Gauss' law for dielectrics

- $\oiint \vec{E} \cdot d\vec{A} = \frac{q_{f, enc}}{\kappa \epsilon_0}$

# TopHat Question

A capacitor without a dielectric is charged up so that it stores potential energy  $U_0$ , and it is then disconnected so that **its charge remains the same**. A dielectric with constant  $\kappa = 2$  is then inserted between the plates. What is the new potential energy stored in the capacitor **with the dielectric**?

$$U_C = \frac{Q^2}{2C} = \frac{V_C^2 C}{2}$$

A.  $4U_0$

C.  $\frac{1}{2}U_0$


A.  $2U_0$

D.  $\frac{1}{4}U_0$

The **potential energy lowers** when the dielectric is added, so it will feel a **force sucking it into the gap** between the plates.

Can find the force using  $F_x = -dU/dx$  and
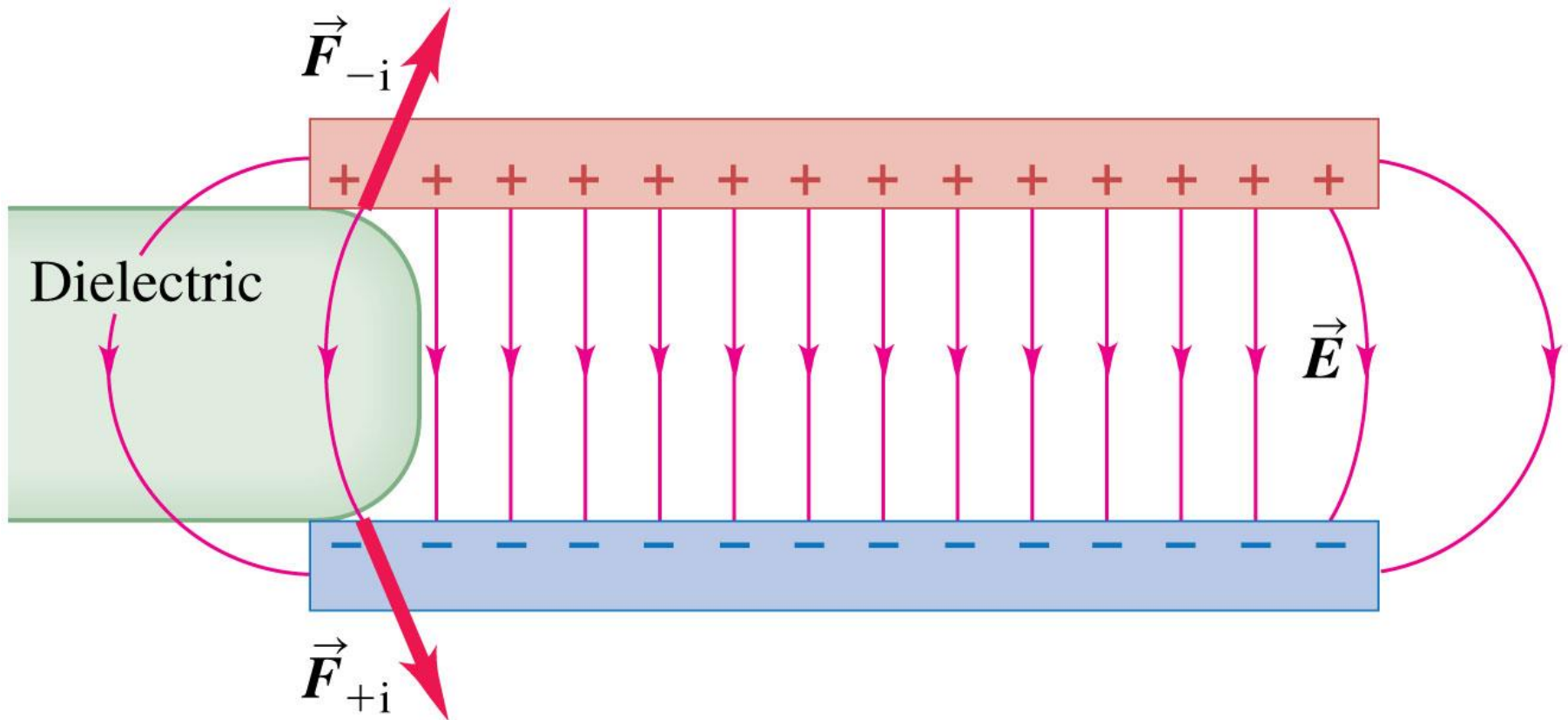
$$W = \int dq \left( \frac{q}{C} \right) = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} C V^2$$



© 2012 Pearson Education, Inc.

Fringe Electric Field pulls the dielectric into the gap

# TopHat Question

A capacitor without a dielectric is charged up so that it stores potential energy  $U_0$ , and is kept connected **at constant voltage**. A dielectric with constant  $\kappa = 2$  is then inserted between the plates. What is the new potential energy stored in the capacitor **with the dielectric**?

$$U_C = \frac{Q^2}{2C} = \frac{V_C^2 C}{2}$$

A.  $4U_0$

C.  $\frac{1}{2}U_0$


A.  $2U_0$

D.  $\frac{1}{4}U_0$


The **potential energy raises** when the dielectric is added, so it will feel a **force pushing it out of the gap** between the plates.

# Application: Capacitive Touch Screen

Row and column stack up layers

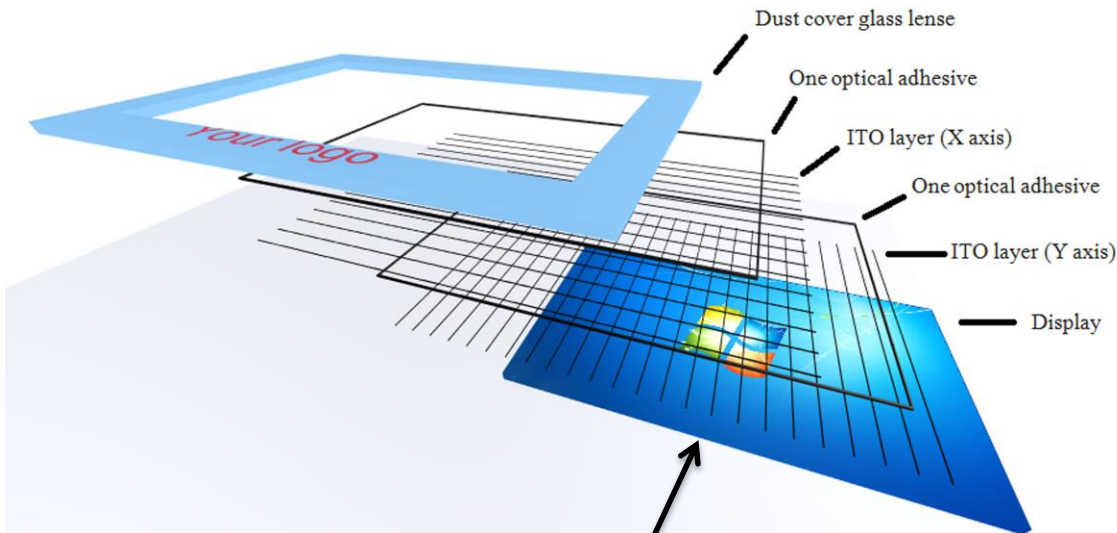


Should be 

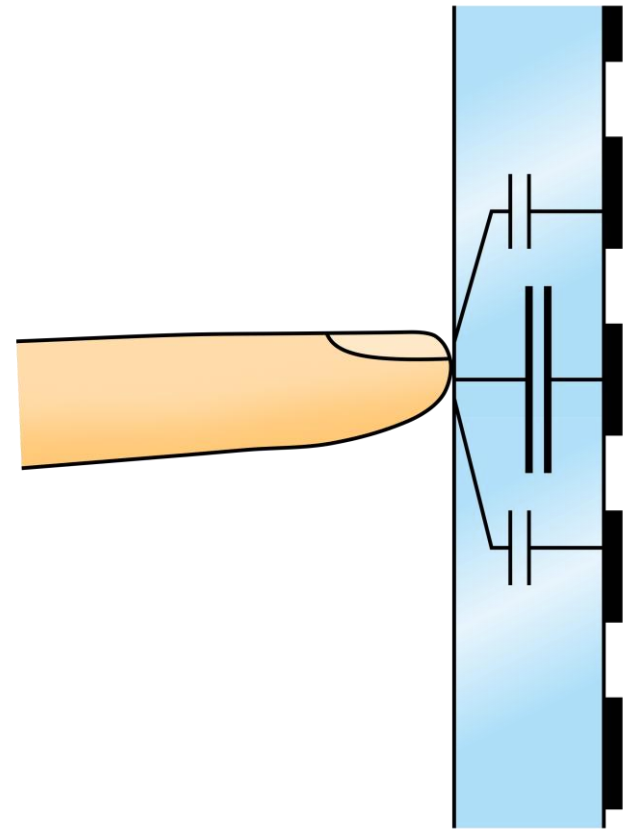

<https://www.youtube.com/watch?v=qBbxSEp3-6o>

# Application: Capacitive Fuel Gauge

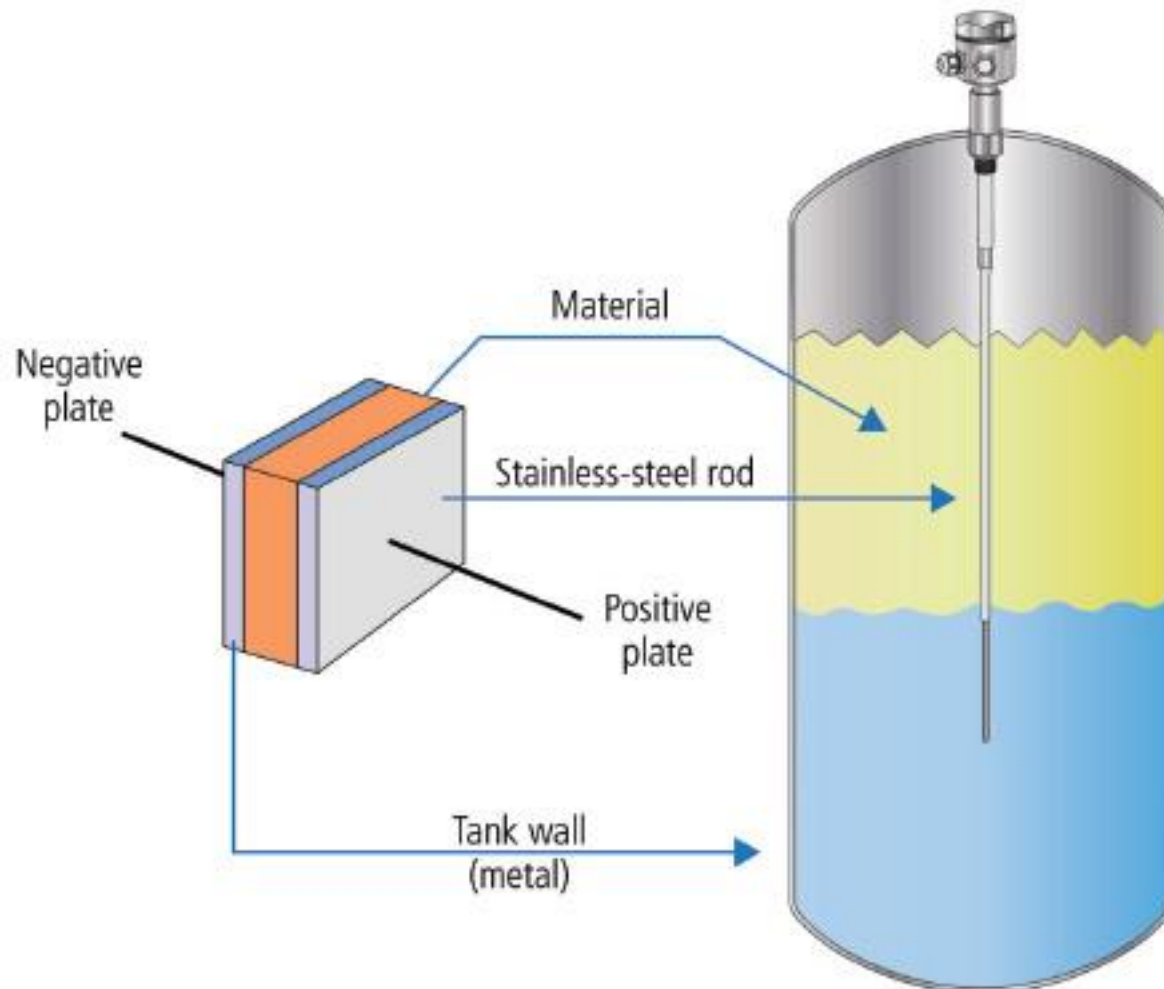

<https://www.youtube.com/watch?v=0du-QU1Q0T4>