

Electricity and Magnetism

- Physics 259 – L02
 - Lecture 35



UNIVERSITY OF
CALGARY

Chapter 27



Last time

- Chapters 26 and 27

This time




- Solve some examples


27 Circuits: continue of last section




Resistivity and temperature

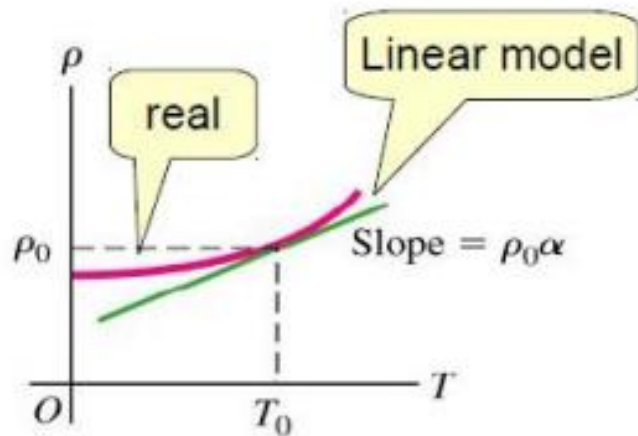

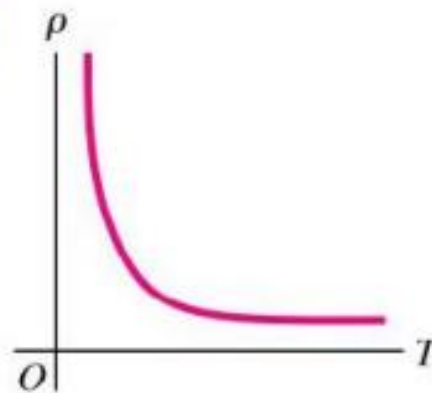(a) Metal:
 ρ increases
with increasing T



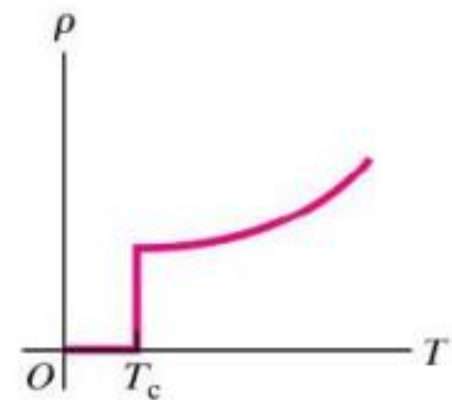
(b) Semiconductor:
 ρ decreases
with increasing T



(c) Superconductor:
 $\rho = 0$ for $T < T_c$


<https://www.youtube.com/watch?v=hTT6nktJQBE>

Case 1: Charging a capacitor

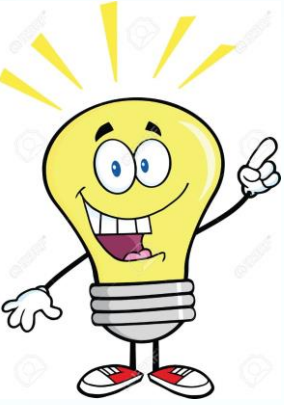


$$i = i_0 e^{-t/RC}$$
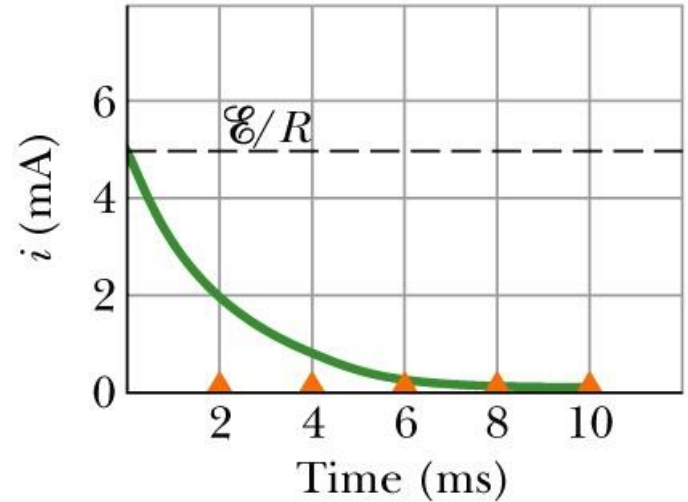
$$q = \varepsilon C (1 - e^{-t/RC}) = Q_f (1 - e^{-t/RC})$$



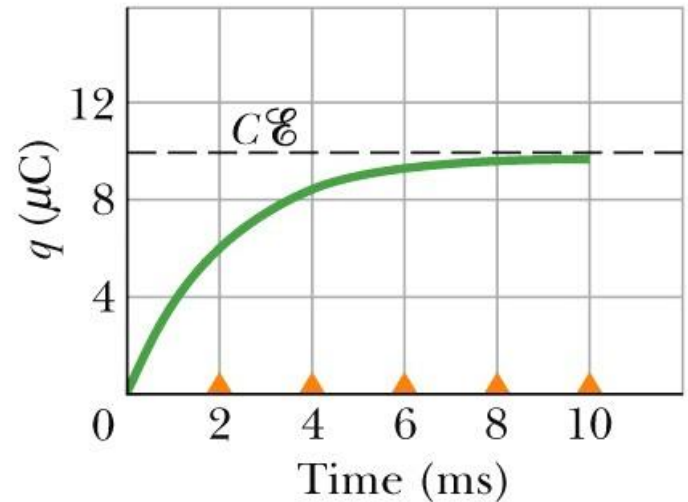
Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.


Case 2: Discharging a capacitor

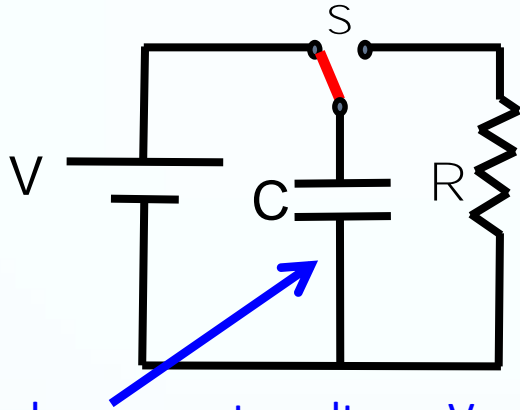Switch is connected to the left for a long time until $t=0^-$



Capacitor charges up to voltage V

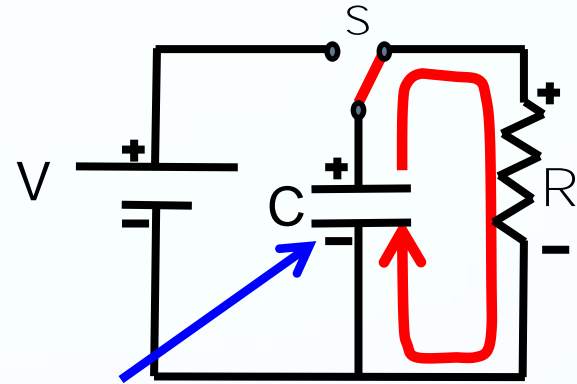Switch is suddenly flipped to the right at $t=0^+$




Capacitor discharges

$$q(t) = q_0 e^{-t/RC}$$

$$i(t) = i_0 e^{-t/RC}$$



$$q_0 = CV$$

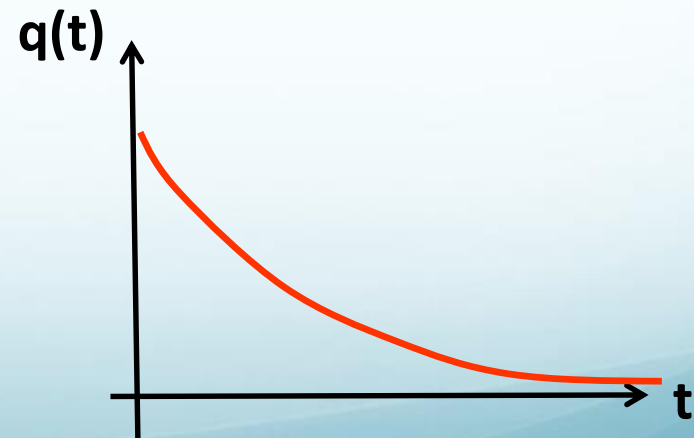

Charging/Discharging Capacitors



Charging: $q(t) = Q_f \left(1 - e^{-\frac{t}{RC}} \right)$

$$i(t) = i_0 e^{-\frac{t}{RC}}$$

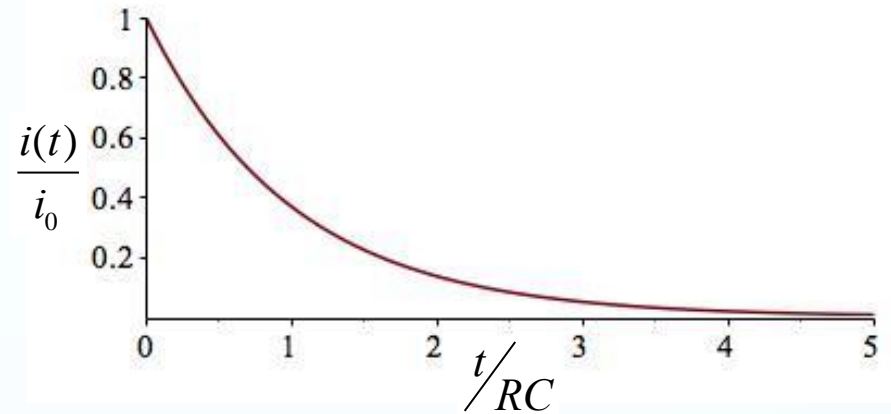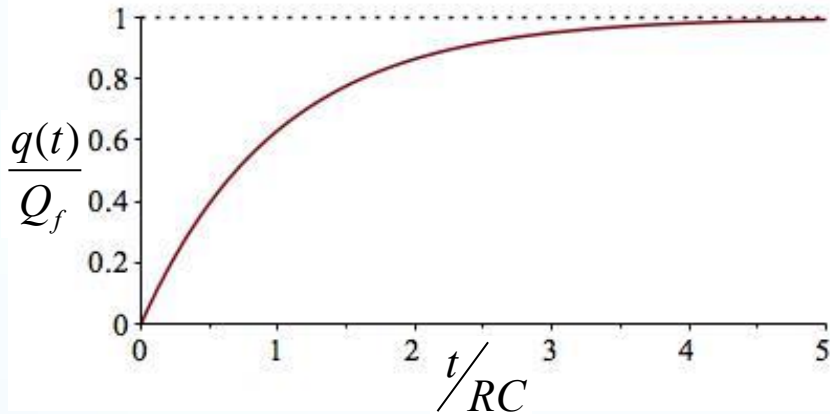

Discharging: $q(t) = Q_0 e^{-\frac{t}{RC}}$

$$i(t) = i_0 e^{-\frac{t}{RC}}$$

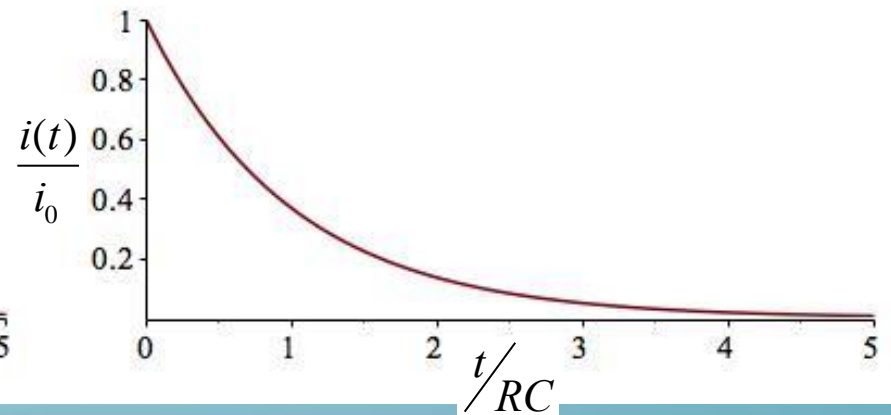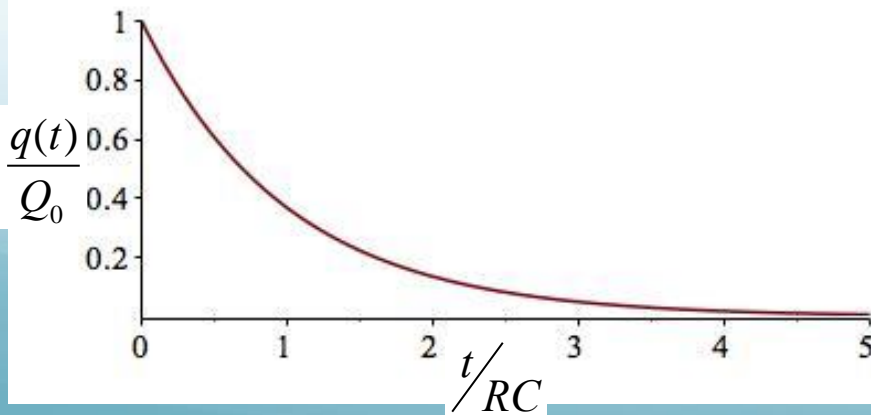

The RC time constant

The constant RC pops up in the exponential factor for both charging and discharging capacitors. What does it represent?

The units of RC is seconds: $[RC] = \frac{V}{A} \frac{C}{V} = \frac{C}{C/s} = s$

We call RC the “**RC time constant**” and it tells us how quickly a capacitor can charge or discharge.

$$RC \propto t$$


After a time τ , the charge on a discharging capacitor is reduced by a factor of $1/e$. After a time $N\tau$, it is reduced by a factor of $1/e^N$

$$q(t) = Q_0 e^{-\frac{t}{\tau}}$$


Sample question

An RC circuit is shown below. Initially the switch is open and the capacitor is uncharged. At time $t = 0$ s, the switch is thrown to the left, connecting the capacitor to the battery. At time $t = 15$ ms the switch is thrown to the right, connecting the capacitor to the resistor.

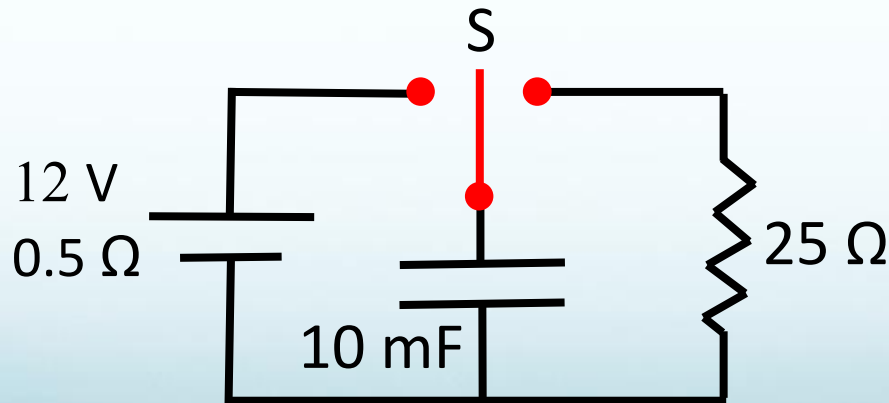- 1) How much charge builds up on the capacitor while it is connected to the battery?
- 2) What is the voltage across the resistor as a function of time as the capacitor discharges?
- 3) What is the ratio of the charging time to discharging time?



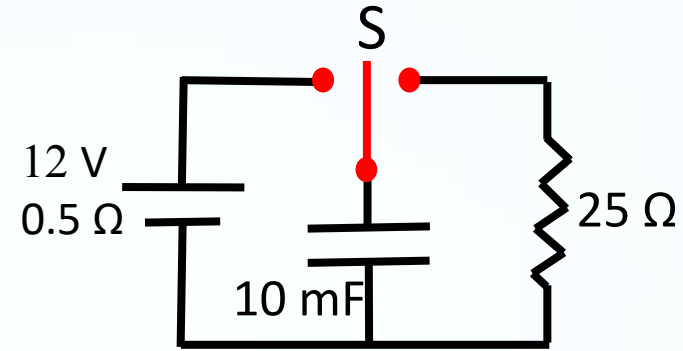
Initially the switch is open and the capacitor is uncharged. At time $t = 0$ s, the switch is thrown to the left, connecting the capacitor to the battery. At time $t = 15$ ms the switch is thrown to the right, connecting the capacitor to the resistor.



- 1) How much charge builds up on the capacitor while it is connected to the battery?


Initially the switch is open and the capacitor is uncharged. At time $t = 0$ s, the switch is thrown to the left, connecting the capacitor to the battery. At time $t = 15$ ms the switch is thrown to the right, connecting the capacitor to the resistor.

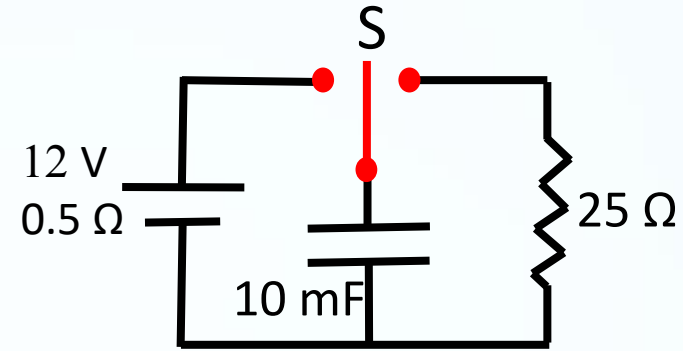2) What is the voltage across the resistor as a function of time as the capacitor discharges?



Initially the switch is open and the capacitor is uncharged. At time $t = 0$ s, the switch is thrown to the left, connecting the capacitor to the battery. At time $t = 15$ ms the switch is thrown to the right, connecting the capacitor to the resistor.

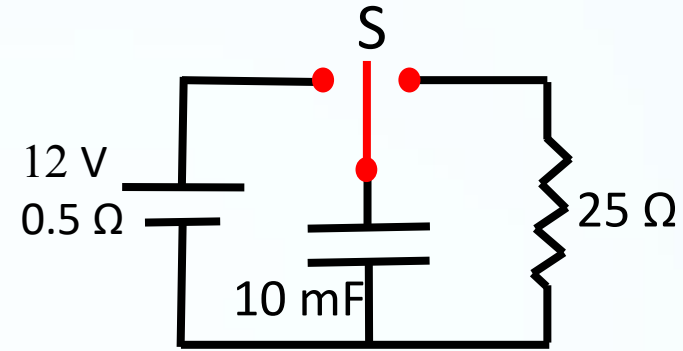3) What is the ratio of the charging time to discharging time?



This section we talked about:

Chapter 27

See you on Friday

